

**Logic Design**  
**Lab Experiments**  
**Dr. Manal Tantawi**

	<b>Experiment Title</b>
1	Logic gates
2	combination circuit I
3	Combination circuit II
4	Implementing functions using NAND only
5	Implementing functions using NOR only
6	Full adder
7	Full adder using decoder
8	Implementing functions using multiplexers
9	Sequential circuit
10	2 bit counter
11	Pseudo-random generator
12	Frequency division

# Lab 1 (logic gates)

**Objective:** introducing lab equipment and integrated circuits (ICs) to students.

**Task to do in lab:** verify truth table of logic gates.

**OR gate (IC:7432)**

X	Y	$X+Y$
0	0	0
0	1	1
1	0	1
1	1	1

**AND gate (IC:7408)**

X	Y	$X.Y$
0	0	0
0	1	0
1	0	0
1	1	1









**NOR gate (IC:7402)**

X	Y	$(X+Y)'$
0	0	1
0	1	0
1	0	0
1	1	0

**NAND gate (IC:7400)**

X	Y	$(X.Y)'$
0	0	1
0	1	1
1	0	1
1	1	0

# ICs for logic gates

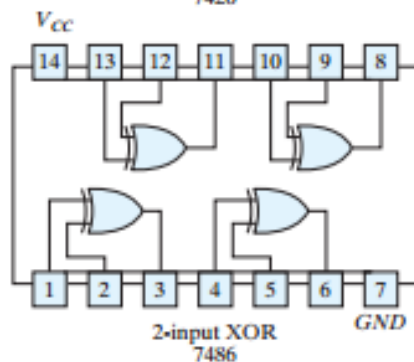 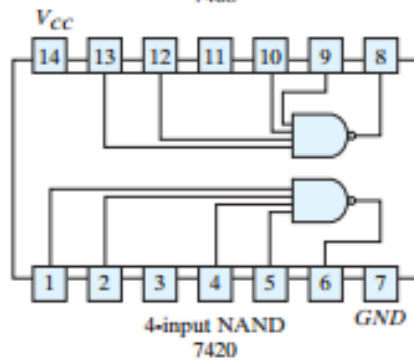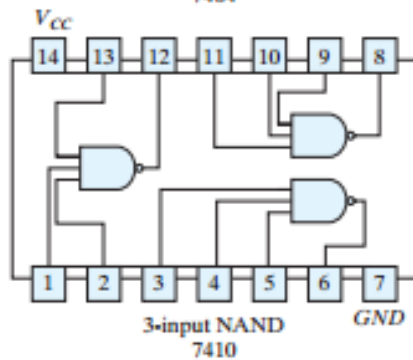 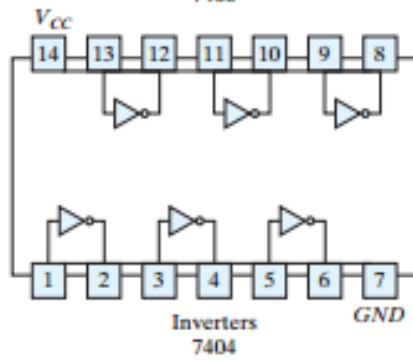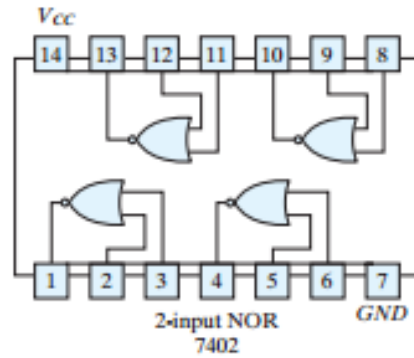 

# Lab 2 (combinational circuit I)


**Objective:** implementing simple combinational circuit.

**Task to do in lab:** implementing practically the following function

$$F(X, Y, Z) = XY' + Z$$

Truth table for F

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

 

# Lab 3 (combinational circuit II)


**Objective:** implementing combinational circuit (long expression)

**Task to do in lab:** implementing practically the following function

$$F(A, B, C, D) = A'(B + C'D) + BC$$

Truth table for F

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

 


# Lab 4 (NAND only)

**Objective:** implementing Functions using NAND only

**Task to do in lab:** implementing practically the following function using NAND only

$$F(A, B, C, D) = AB + ACD + AB'CD'$$

 


$$F(A, B, C, D) = \sum(10, 11, 12, 13, 14, 15)$$

# Lab 5 (NOR only)

**Objective:** implementing functions using NOR only.

 **Task to do in lab:** implementing practically the following function using NOR only.

$$F(W, X, Y, Z) = (Y' + Z')(W' + X' + Y)$$



$$F(W, X, Y, Z) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 10, 14)$$




# Lab 6 (Full adder)

**Objective:** implementing Full Adder.

**Task to do in lab:** implementing practically the Full Adder.

Truth table for Full Adder

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 



# Lab 8 (Multiplexers)

**Objective:** implementing functions using multiplexer.


**Task to do in lab:** implementing practically the Following function using multiplexer.

$$F(A, B, C, D) = \sum(0, 1, 3, 4, 8, 9, 15)$$


Truth table for F

A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

Implementation using multiplexer

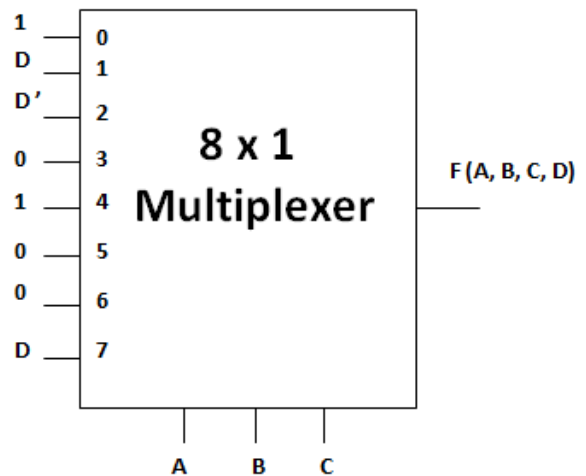

 Pin assignment for available multiplexer IC: 74151



Function table for IC: 74155


Function table

Strobe	Select			Output
<i>S</i>	<i>C</i>	<i>B</i>	<i>A</i>	<i>Y</i>
1	X	X	X	0
0	0	0	0	<i>D0</i>
0	0	0	1	<i>D1</i>
0	0	1	0	<i>D2</i>
0	0	1	1	<i>D3</i>
0	1	0	0	<i>D4</i>
0	1	0	1	<i>D5</i>
0	1	1	0	<i>D6</i>
0	1	1	1	<i>D7</i>

# Lab 9 (Sequential circuits)

**Objective:** implementing sequential circuits using different flip flops.

 
**Task to do in lab:** design and implement a sequential circuit that follows the following state diagram with one external output using T flip flops.




$A_n$	$B_n$	$A_{n+1}$	$B_{n+1}$	$T_A$	$T_B$	$Y$
0	0	0	1	0	1	1
0	1	0	0	0	1	1
1	0	1	1	0	1	0
1	1	0	0	1	1	0

$$T_A = AB \quad T_B = 1 \quad Y = A'$$



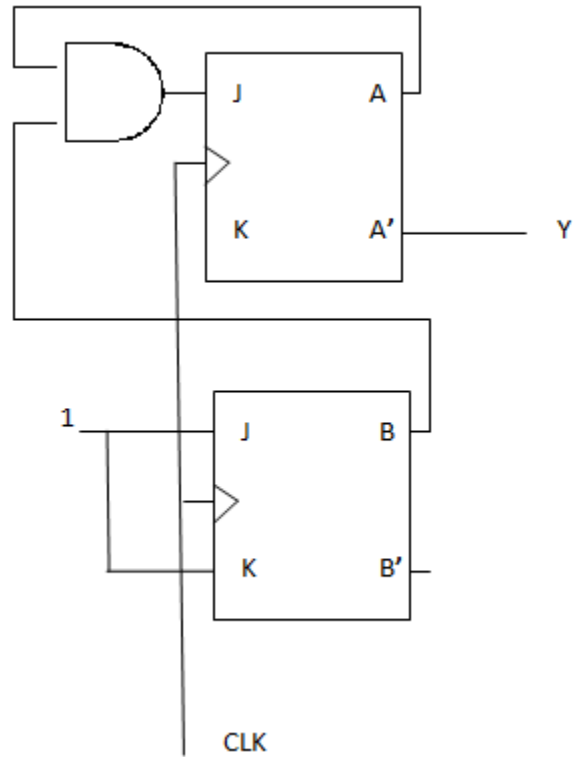

 Circuit Logic diagram using JK flip flops (j and k are connected to form T flip flop)



Pin assignment for available JK flip flop IC: 7476



Function table

Inputs					Outputs	
Preset	Clear	Clock	$J$	$K$	$Q$	$Q'$
0	1	X	X	X	1	0
1	0	X	X	X	0	1
0	0	X	X	X	1	1
1	1		0	0	No change	
1	1		0	1	0	1
1	1		1	0	1	0
1	1		1	1	Toggle	

# Lab 10 (Counters)

**Objective:** implementing counter circuits using different flip flops.


**Task to do in lab:** design and implement a two bit counter using JK flipflops

$A_n$	$B_n$	$A_{n+1}$	$B_{n+1}$	$J_A$	$K_B$	$J_B$	$K_B$
0	0	0	1	0	x	1	x
0	1	1	0	1	x	x	1
1	0	1	1	x	0	1	x
1	1	0	0	x	1	x	1

$$J_A = K_A = B$$


$$J_B = K_B = 1$$

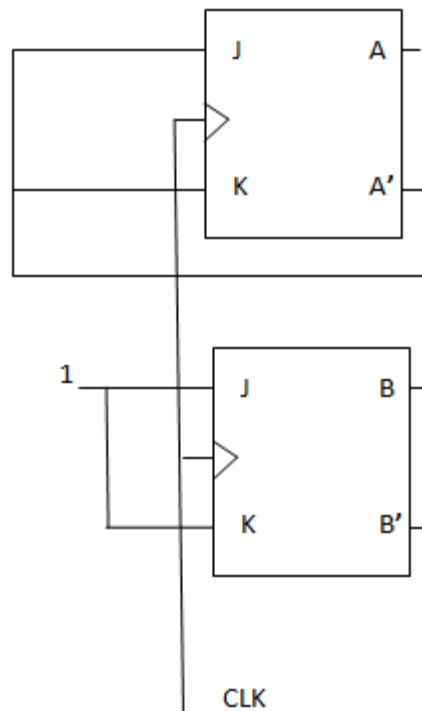Circuit Logic diagram using JK flip flops







 

Pin assignment for available JK flip flop IC: 7476




Function table

Inputs					Outputs	
Preset	Clear	Clock	$J$	$K$	$Q$	$Q'$
0	1	X	X	X	1	0
1	0	X	X	X	0	1
0	0	X	X	X	1	1
1	1		0	0	No change	
1	1		0	1	0	1
1	1		1	0	1	0
1	1		1	1	Toggle	

# Lab 11 (Registers)

**Objective:** implementing pseudorandom generator using 4 bit shift register.

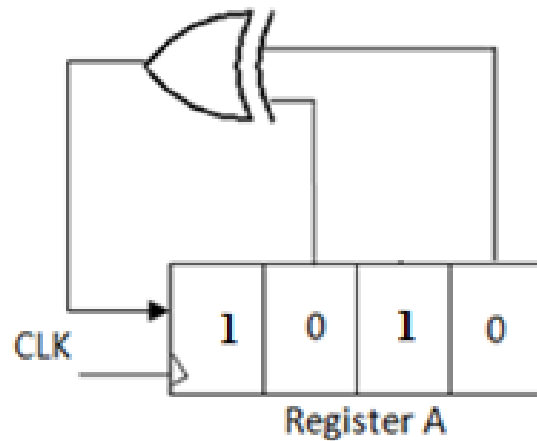
**Task to do in lab:** use 4 bit shift register with XOR to generate random numbers.



Serial input (SI)	Register Content
0	1010
0	0101
0	0010
1	0001
0	1000
1	0100
	1010

Cycle length = 6
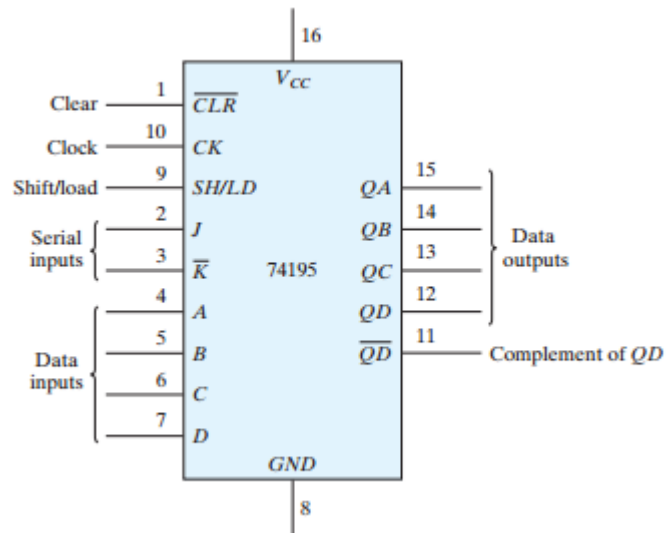
## Pin assignment for available 4 bit shift register IC: 74195




Function table

Clear	Shift/ load	Clock	$J$	$\overline{K}$	Serial input	Function
0	X	X	X	X	X	Asynchronous clear
1	X	0	X	X	X	No change in output
1	0	↑	X	X	X	Load input data
1	1	↑	0	0	0	Shift from $QA$ toward $QD$ , $QA = 0$
1	1	↑	1	1	1	Shift from $QA$ toward $QD$ , $QA = 1$


# Lab 12 (Programmable counters)

**Objective:** implementing frequency divider.

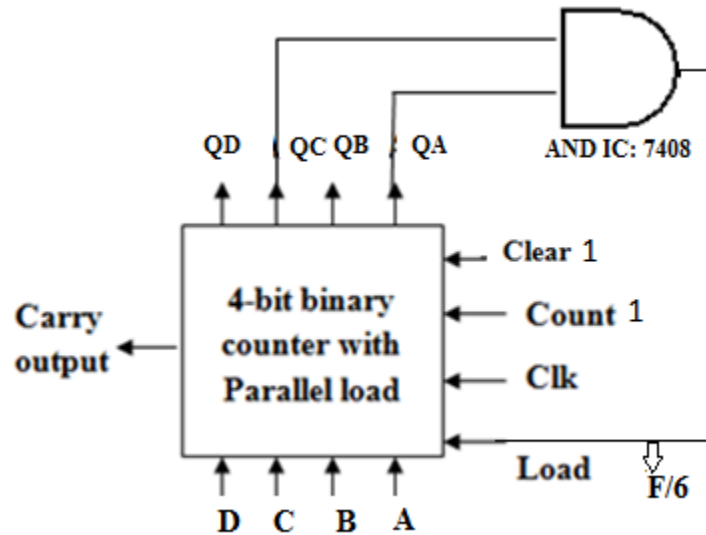**Task to do in lab:** implement frequency divider using 4 bit programmable counter. Ex: F/6



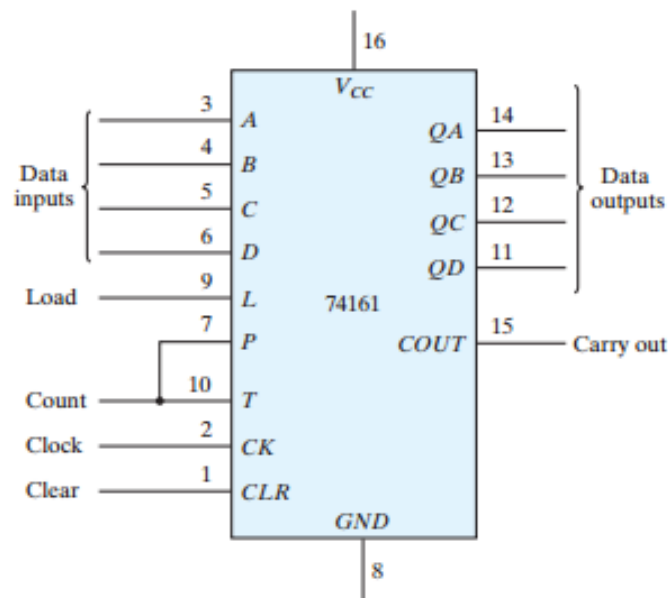Pin assignment for available 4 bit programmable counter IC: 74161



Function table

Clear	Clock	Load	Count	Function
0	X	X	X	Clear outputs to 0
1	↑	0	X	Load input data
1	↑	1	1	Count to next binary value
1	↑	1	0	No change in output