



Tutorial 3

- 1) Simplify the following Boolean expressions to a minimum number of literals:
 - a. $(A + B)' (A' + B)'$
 - b. $A'BC + ABC' + ABC + A'BC'$
- 2) Simplify the following Boolean expressions to a minimum number of literals and Draw logic diagrams of the circuits that implement the original and simplified expressions
 - a. $(A+B')(A+B)$
 - b. $A' B (D' + C' D) + B (A + A' C D)$
- 3) Obtain the truth table of the following functions, and express each function in sum-of-minterms and product-of-maxterms form:
 - a. $(B + CD)(C + BD)$
 - b. $(CD + B'C + BD')(B+D)$
- 4) Express the following functions in sum-of-product and product-of-sum forms
 - a. $F(X, Y, Z) = \sum(1, 3, 7)$
 - b. $F(A, B, C) = \pi(0, 1, 2, 3, 4, 6)$
- 5) Given that $F(A, B, C) = B'C + AC' + ABC$ then
 - a. Express F in terms of Sum of its minterms as $F(A, B, C) = \sum(\dots)$
 - b. Express F in terms of product of its maxterms as $F(A, B, C) = \pi(\dots)$
 - c. Express F' in terms of Sum of its minterms as $F'(A, B, C) = \sum(\dots)$
 - d. Express F' in terms of product of its maxterms as $F'(A, B, C) = \pi(\dots)$
- 6) Repeat question 5 Given that $F(A, B, C) = (A+B+C)(A+B')(B+C')$.
- 7) Express the **complement** of the following functions in sum of minterms and product of maxterm
 - a. $F(A, B, C, D) = \sum(0, 2, 6, 11, 13, 14)$
 - b. $F(A, B, C, D) = \sum(2, 4, 7, 10, 12, 14)$
 - c. $F(X, Y, Z) = \pi(0, 3, 6, 7)$
 - d. $F(X, Y, Z) = \pi(3, 5, 7)$
- 8) Convert each of the following functions to its canonical form:
 - a. $F(x, y, z) = \sum(1, 3, 5)$
 - b. $F(A, B, C, D) = \pi(3, 5, 8, 11)$