



Tutorial 5

- 1) How the three-input NAND can be expanded using two-input NAND?
- 2) Simplify the following Function and then implement it using 2-Level NAND gates only?
 - a. $F(A, B, C, D) = (5, 6, 7, 8, 13, 14, 15)$
- 3) Draw the multiple-level NAND circuit for the following expression:
 - a. $F(w,x,y,z) = w(x + y + z) + xyz$
- 4) How the 3-inputs NOR can be expanded using two-input NOR?
- 5) Simplify the following Function and then implement it using 2-Level NOR Gates only?
 - a. $F(W, X, Y, Z) = (0, 2, 4, 5, 8, 9, 10, 14)$, $d(W, X, Y, Z) = (1, 6, 13)$
- 6) Draw the multiple-level NOR circuit for the following expression:
 - a. $F(A,B,C,D) = CD(B + C)A + (BC' + DE')$
- 7) Design an odd Parity generator \ parity checker circuits.