



Answer the following Three questions:

(The total marks: 50)

**It is forbidden to change the name of variables or their order**

1<sup>st</sup> Question

marks: 22

Choose the correct answer

- 1) The representation of decimal number 9 in (8,4,-2,-1) is ? marks: 1

|         |                         |
|---------|-------------------------|
| a) 1001 | b) 1111                 |
| c) 1100 | d) None of the previous |

- 2) The result of the following subtraction  $(11100011)_2 - (11110000)_2$  is..... marks: 1

|             |              |
|-------------|--------------|
| a) 00010011 | b) 11110011  |
| c) 00001101 | d) -00001101 |

- 3) Which of the following is considered as an example of a number in base 13?

marks: 1

|         |         |
|---------|---------|
| a) FFFF | b) ABCD |
| c) 0101 | d) 876E |

- 4) Given that  $F(A, B, C) = (B'C)' + AC' + ABC$ , then the maxterms of F are .....

marks: 1

|                          |                   |
|--------------------------|-------------------|
| a) $\Sigma(0,2,3,4,6,7)$ | b) $\prod(1,5)$   |
| c) $\Sigma(3,4,5,6,7)$   | d) $\prod(0,2,3)$ |

- 5) The simplest (optimal) form of  $F(x, y, z) = x'(y' + z') + yz + z + xz'$  is .....

marks: 2

|              |               |
|--------------|---------------|
| a) 1         | b) $z + x'$   |
| c) $xz + y'$ | d) $z + y'z'$ |

- 6) If the complement of the function F is expressed as  $F'(A, B, C, D) = \Sigma(2, 4, 5, 6, 8, 9, 11, 12)$ , Then F could be expressed as: marks: 2

|                                     |                                 |
|-------------------------------------|---------------------------------|
| a) $\Sigma(0,1,3,7,10,11,13,14,15)$ | b) $\prod(2,4,5,6,8,9,10,12)$   |
| c) $\Sigma(0,1,3,7,10,13,14,15)$    | d) $\prod(2,4,5,6,7,8,9,11,12)$ |

- 7) The circuit that takes an input  $X = X_2 X_1 X_0$  and calculate the output as follow:


$$Y = \begin{cases} 0 & 1 \leq X < 3 \\ 1 & 4 \leq X < 7 \end{cases}$$

The circuit could be expressed as

marks: 2

|                              |                             |
|------------------------------|-----------------------------|
| a) $\sum(4, 5, 6)$           | b) $\sum(4, 5, 6), d(0, 3)$ |
| c) $\prod(1, 2), d(0, 3, 7)$ | d) $\prod(0, 1, 2, 3, 7)$   |

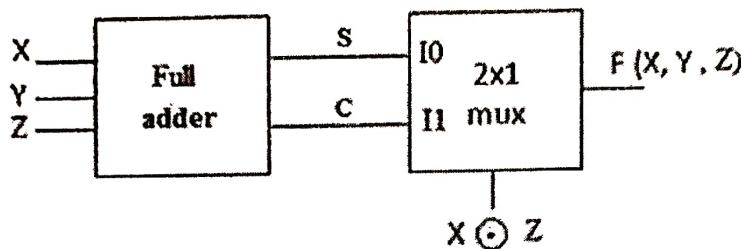Questions 8 and 9, For the following Function  $F(X, Y, Z)$ ,



- 8) When  $X, Y$  and  $Z$  equal 1, 0 and 1 respectively, then  $F$  equals ..... marks: 2

|      |      |
|------|------|
| a) 0 | b) 1 |
|------|------|


- 9) When  $X, Y$  and  $Z$  equal 1, 1 and 0 respectively, then  $F$  equals ..... marks: 2

|      |      |
|------|------|
| a) 0 | b) 1 |
|------|------|


- 10) If the function  $F(A, B, C) = \sum(0, 4, 6, 7)$  is implemented using  $4 \times 1$  mux with  $A$  and  $C$  on selections then the inputs from  $I_0$  to  $I_3$  will be equal to ..... respectively. marks: 2

|                   |                   |
|-------------------|-------------------|
| a) $B', 0, B', 1$ | b) $0, 1, 0, 1$   |
| c) $B', 0, 1, B$  | d) $B', B, B', B$ |

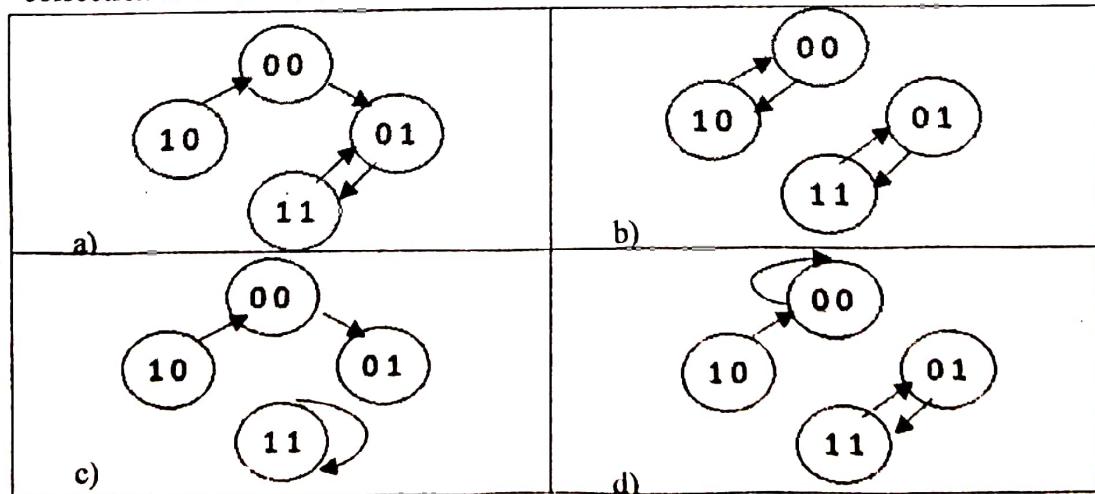- 11) From these state diagrams, the one that can be a state diagram for a self-correction counter is ..... marks: 2




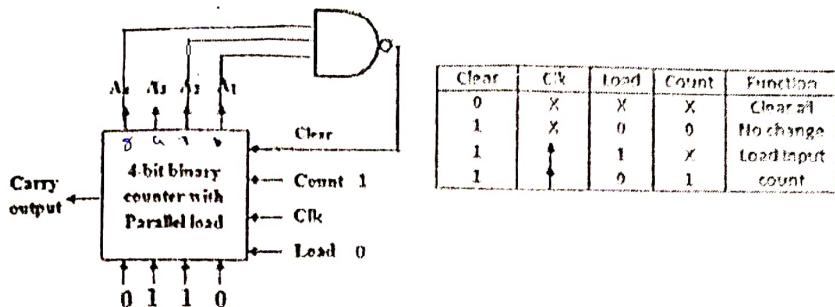✓ 12) Using the following 4 bit programmable counter with the given function table, It will count..... marks: 2



- |            |            |
|------------|------------|
| a) 0 to 6  | b) 0 to 11 |
| c) 6 to 11 | d) 6 to 10 |

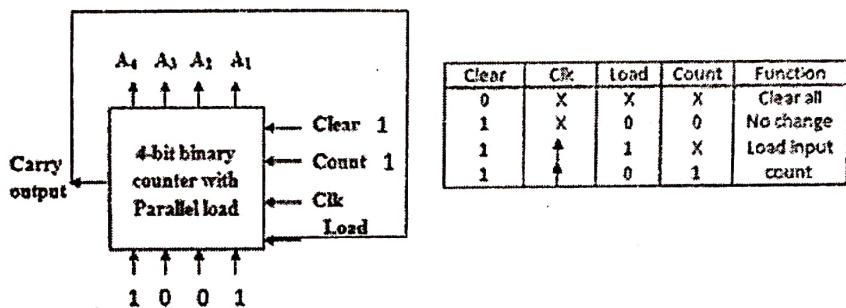
~ 13) Using the following 4 bit programmable counter with the given function table, we can get ..... marks: 2




- |        |         |
|--------|---------|
| a) F/7 | b) F/9  |
| c) F/8 | d) F/10 |

**2<sup>nd</sup> Question** marks: 16

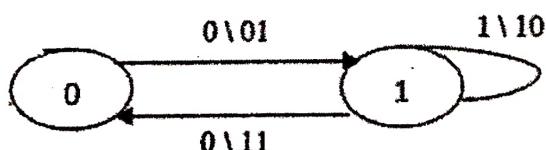A) Design a sequential circuit using JK flipflops according to the following state diagram. marks: 10



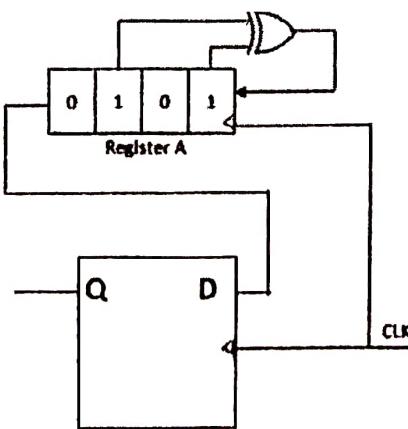
B) Find the content for the 4 bit shift registers and the value of Q during 4 clocks. The initial value for Q is Zero. marks: 6




3<sup>rd</sup> Question

marks: 12

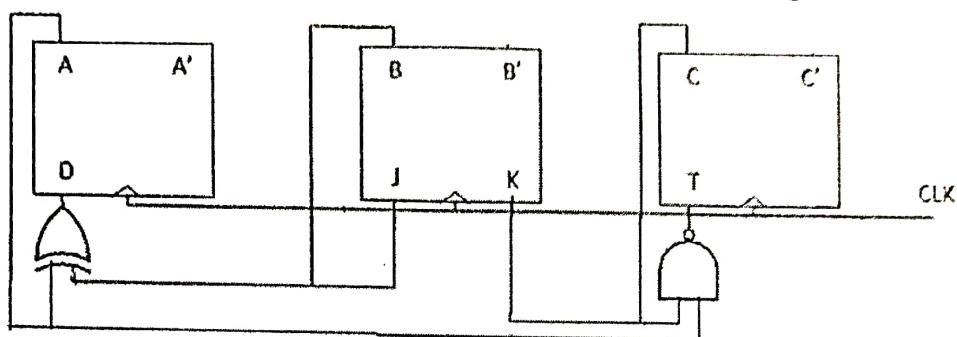- A) Analyze the following circuit then find its state table and state diagram marks: 8



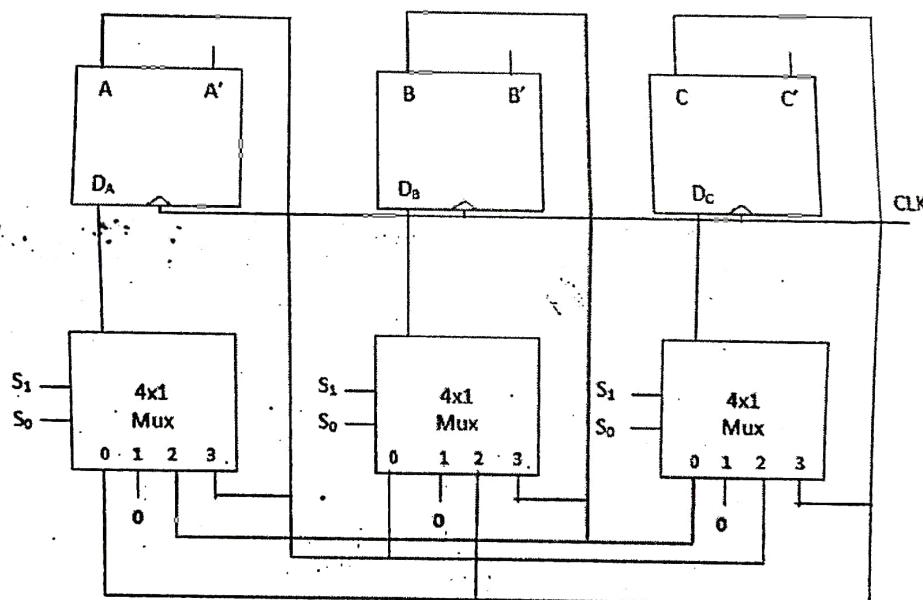- B) Follow the circuits connections, then find the function table of the given universal shift register of 4 different functions (All muxs have the same selection control). marks: 4



*With My Best Regards.*

*Assoc. Prof. Manal Tantawi*

*Dr. Merwat El-Zutty*