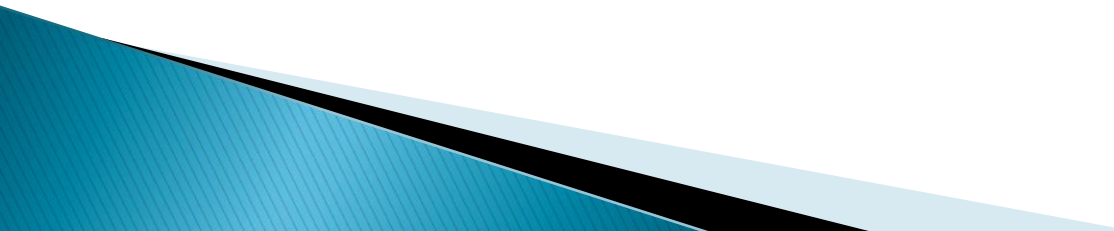


# Digital Design


Lecture of week 11

Dr Manal Tantawi

# Analysis of Sequential Circuits

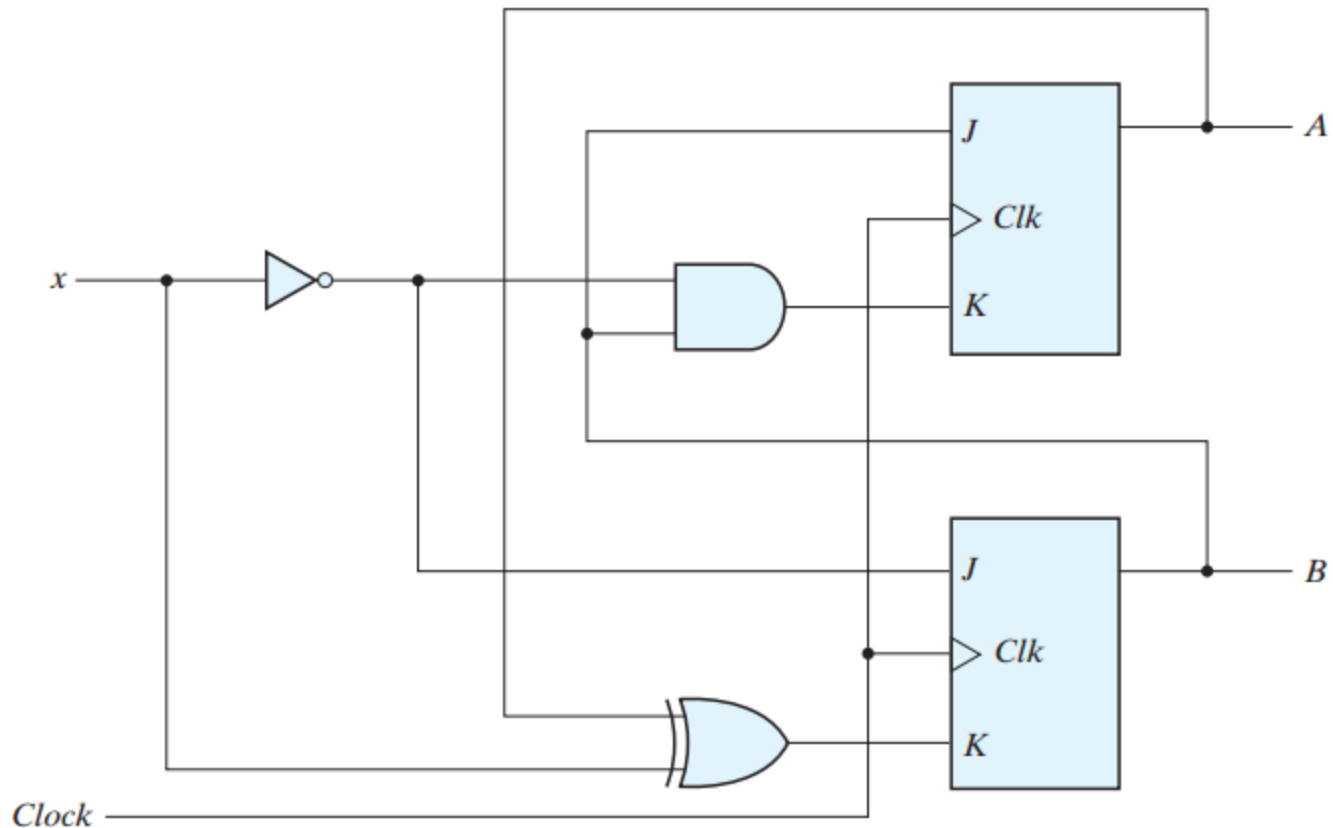- 1) Logic Diagram
  - 2) Expressions for external outputs (if exist) and inputs of flipflops
  - 3) State Table
  - 4) State Diagram
- 


Analyze the following circuit and then derive its state table and diagram



- ▶ One external input
- ▶ No external output
- ▶ Two J K flip flops

$$J_A = B \quad K_A = Bx'$$
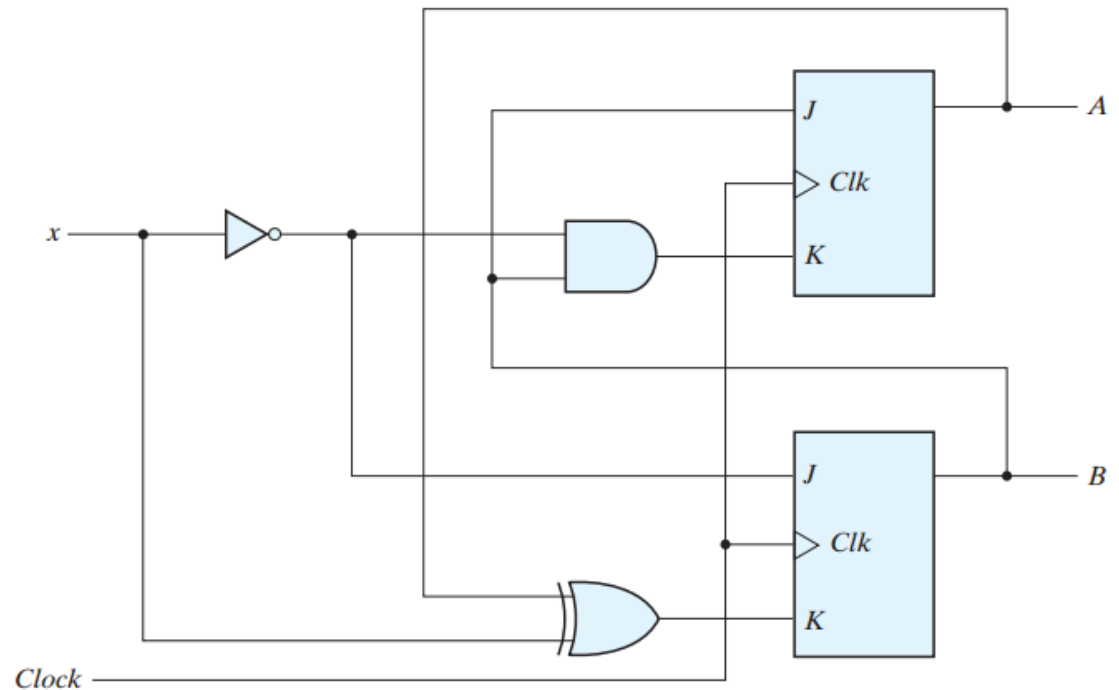
$$J_B = x' \quad K_B = A'x + Ax' = A \oplus x$$



$$J_A = B \quad K_A = Bx'$$

$$J_B = x' \quad K_B = A'x + Ax' = A \oplus x$$

*State Table for Sequential Circuit with JK Flip-Flops*

Present State		Input	Flip-Flop Inputs				Next State	
A	B		$J_A$	$K_A$	$J_B$	$K_B$	A	B
0	0	0	0	0	1	0		
0	0	1	0	0	0	1		
0	1	0	1	1	1	0		
0	1	1	1	0	0	1		
1	0	0	0	0	1	1		
1	0	1	0	0	0	0		
1	1	0	1	1	1	1		
1	1	1	1	0	0	0		

<b>JK Flip-Flop</b>			
<b>J</b>	<b>K</b>	<b>Q(n + 1)</b>	
0	0	Q(n)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(n)	Complement

### State Table for Sequential Circuit with JK Flip-Flops

<b>Present State</b>		<b>Input</b>	<b>Flip-Flop Inputs</b>				<b>Next state</b>	
<b>A</b>	<b>B</b>		<b>J<sub>A</sub></b>	<b>K<sub>A</sub></b>	<b>J<sub>B</sub></b>	<b>K<sub>B</sub></b>	<b>A</b>	<b>B</b>
0	0	0	0	0	1	0	0	0
0	0	1	0	0	0	1	0	0
0	1	0	1	1	1	0	1	1
0	1	1	1	0	0	1	1	1
1	0	0	0	0	1	1	1	1
1	0	1	0	0	0	0	0	1
1	1	0	1	1	1	1	1	0
1	1	1	1	0	0	0	0	1


<b>JK Flip-Flop</b>			
<b>J</b>	<b>K</b>	<b>Q(n + 1)</b>	
0	0	Q(n)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(n)	Complement

*State Table for Sequential Circuit with JK Flip-Flops*

<b>Present Stat</b>		<b>Input</b>	<b>Flip-Flop Inputs</b>				<b>Next Stat</b>	
<b>A</b>	<b>B</b>		<b>J<sub>A</sub></b>	<b>K<sub>A</sub></b>	<b>J<sub>B</sub></b>	<b>K<sub>B</sub></b>	<b>A</b>	<b>B</b>
0	0	0	0	0	1	0	0	1
0	0	1	0	0	0	1	0	0
0	1	0	1	1	1	0	1	1
0	1	1	1	0	0	1	1	0
1	0	0	0	0	1	1	1	1
1	0	1	0	0	0	0	1	0
1	1	0	1	1	1	1	0	0
1	1	1	1	0	0	0	1	1

## State Diagram

Present State		Input $x$	Next State	
$A$	$B$		$A$	$B$
0	0	0	0	1
0	0	1	0	0
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1

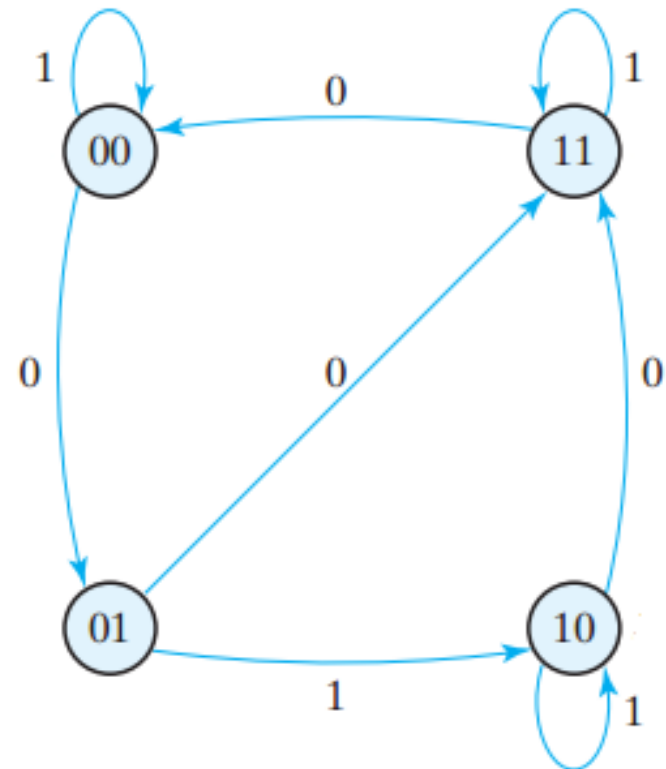




# Analyze the following circuit and then derive its state table and diagram

One external input  
One external output  
Two T flip flops

$$T_A = Bx$$

$$T_B = x$$

$$y = AB$$

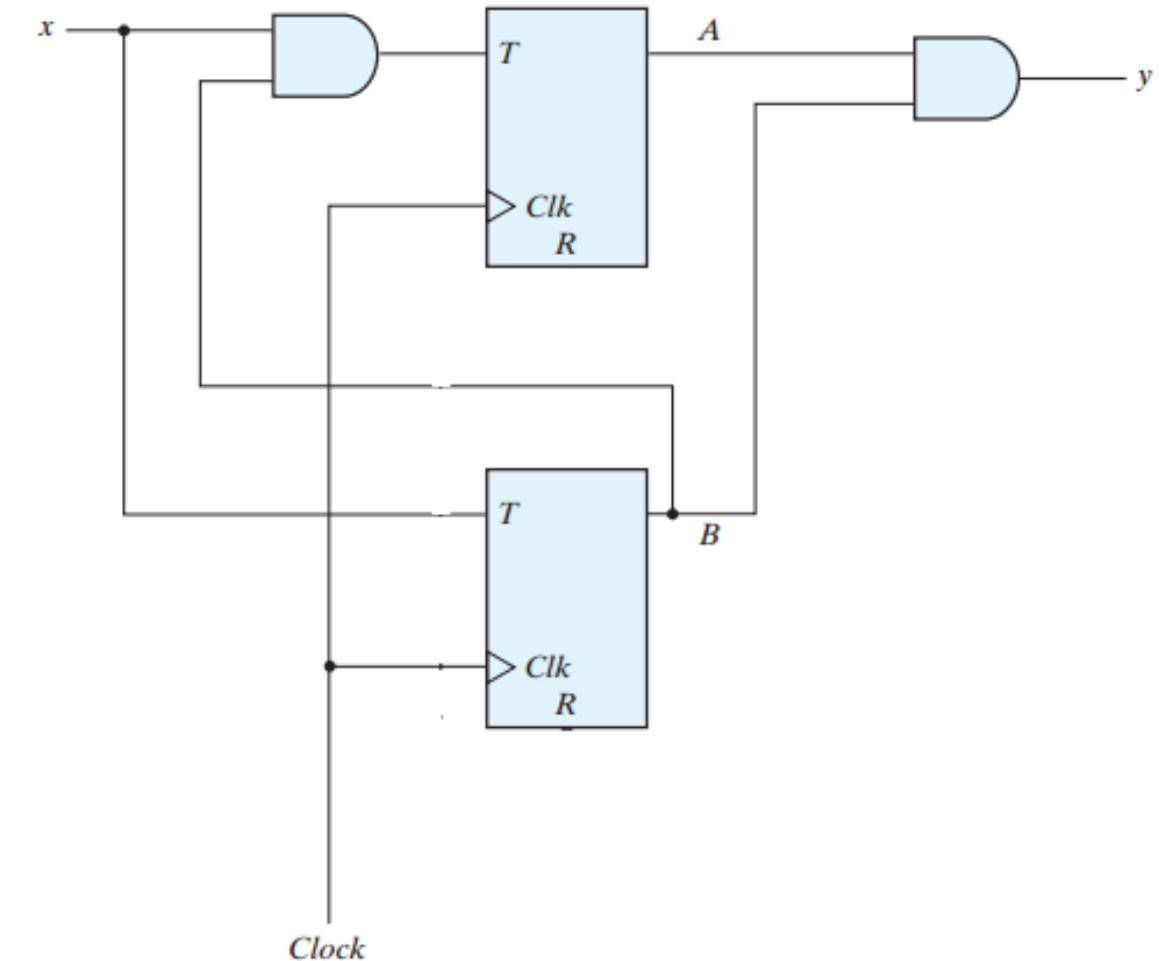

$$T_A = Bx$$

$$T_B = x$$

$$y = AB$$

---

<b>Present State</b>		<b>Input</b>		
<b>A</b>	<b>B</b>	<b>x</b>		<b>y</b>
0	0	0		0
0	0	1		0
0	1	0		0
0	1	1		0
1	0	0		0
1	0	1		0
1	1	0		1
1	1	1		1

---

$$T_A = Bx$$

$$T_B = x$$

$$y = AB$$

---

<b>Present State</b>		<b>Input</b>				
<b>A</b>	<b>B</b>	<b>x</b>	Ta	Tb		y
0	0	0	0	0		0
0	0	1	0	1		0
0	1	0	0	0		0
0	1	1	1	1		0
1	0	0	0	0		0
1	0	1	0	1		0
1	1	0	0	0		1
1	1	1	1	1		1

---

$$T_A = Bx$$

$$T_B = x$$

$$y = AB$$

**T Flip-Flop**

T	Q(n + 1)	
0	Q(n)	No change
1	Q'(n)	Complement

Present State ↓		Input		Next State ↓		
A	B	x	Ta	Tb	A	y
0	0	0	0	0	0	0
0	0	1	0	1	0	0
0	1	0	0	0	0	0
0	1	1	1	1	1	0
1	0	0	0	0	1	0
1	0	1	0	1	1	0
1	1	0	0	0	1	1
1	1	1	1	1	0	1

$$T_A = Bx$$

$$T_B = x$$


$$y = AB$$

### T Flip-Flop


T	Q(n + 1)	
0	Q(n)	No change
1	Q'(n)	Complement

Present State		Input	Ta	Tb	Next State		y
A	B				A	B	
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	0	0	0	1	0
0	1	1	1	1	1	0	0
1	0	0	0	0	1	0	0
1	0	1	0	1	1	1	0
1	1	0	0	0	1	1	1
1	1	1	1	1	0	0	1

Present State		Input		Next State			
A	B	x	Ta	Tb	A	B	y
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	0	0	0	1	0
0	1	1	1	1	1	0	0
1	0	0	0	0	1	0	0
1	0	1	0	1	1	1	0
1	1	0	0	0	1	1	1
1	1	1	1	1	0	0	1

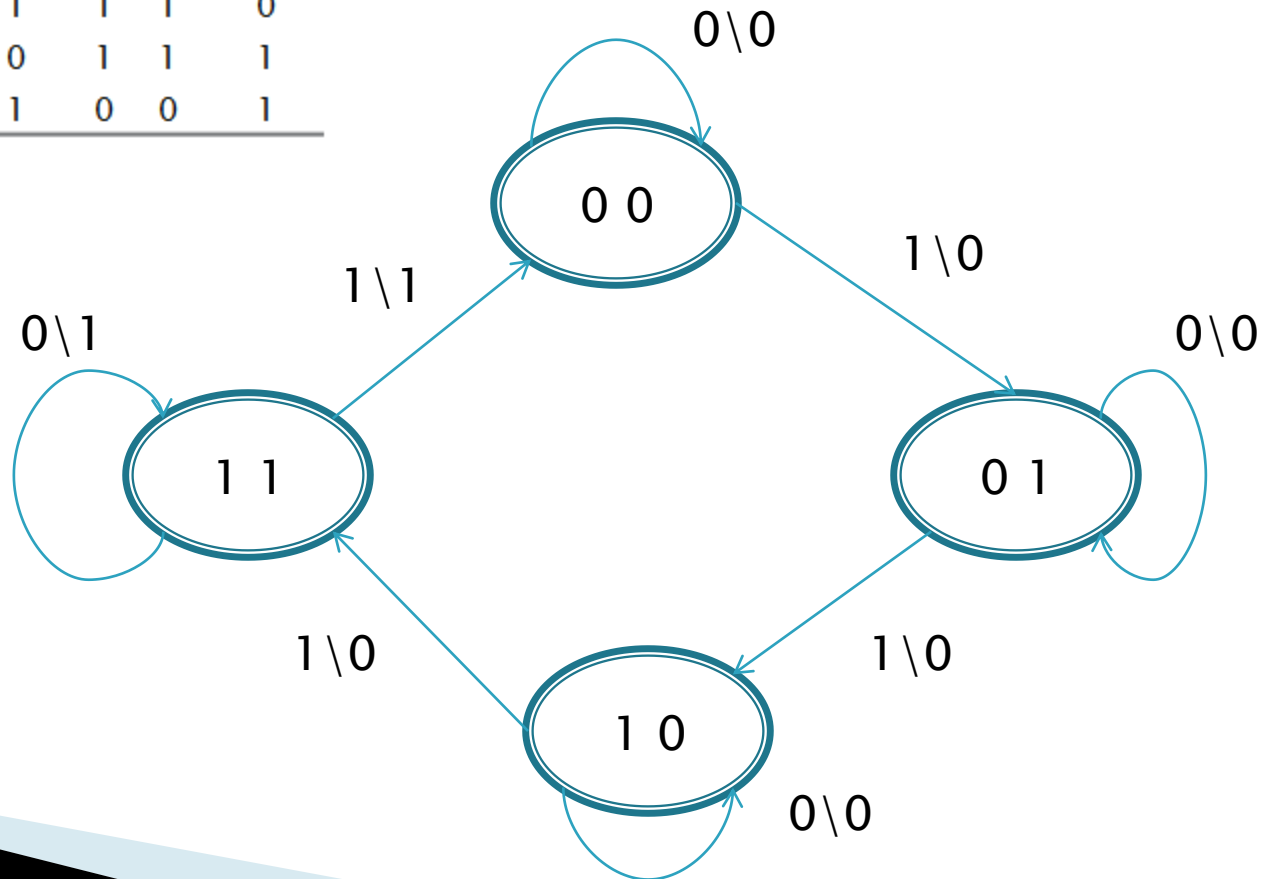

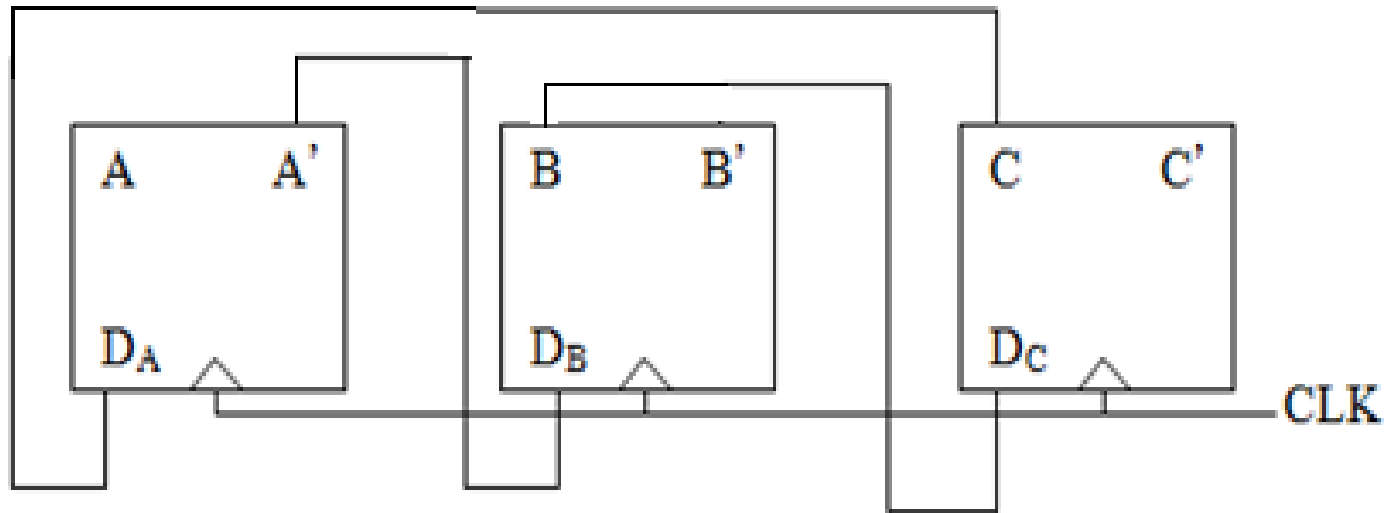Analyze the following sequential circuit, find state table, state diagram and the repeated sequence if exists. is it self correcting ? why ?



$$\begin{aligned} D_a &= C_n \\ D_b &= A_n' \\ D_c &= B_n \end{aligned}$$


$A_n$	$B_n$	$C_n$	$D_a$	$D_b$	$D_c$	$A_{n+1}$	$B_{n+1}$	$C_{n+1}$
0	0	0	0	1	0			
0	0	1	1	1	0			
0	1	0	0	1	1			
0	1	1	1	1	1			
1	0	0	0	0	0			
1	0	1	1	0	0			
1	1	0	0	0	1			
1	1	1	1	0	1			



$D_a = C_n$   
 $D_b = A_n'$   
 $D_c = B_n$

$A_n$	$B_n$	$C_n$	$D_a$	$D_b$	$D_c$	$A_{n+1}$	$B_{n+1}$	$C_{n+1}$
0	0	0	0	1	0	0	1	0
0	0	1	1	1	0	1	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0	0
1	0	1	1	0	0	1	0	0
1	1	0	0	0	1	0	0	1
1	1	1	1	0	1	1	0	1


$A_n$	$B_n$	$C_n$	$D_a$	$D_b$	$D_c$	$A_{n+1}$	$B_{n+1}$	$C_{n+1}$
0	0	0	0	1	0	0	1	0
0	0	1	1	1	0	1	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0	0
1	0	1	1	0	0	1	0	0
1	1	0	0	0	1	0	0	1
1	1	1	1	0	1	1	0	1

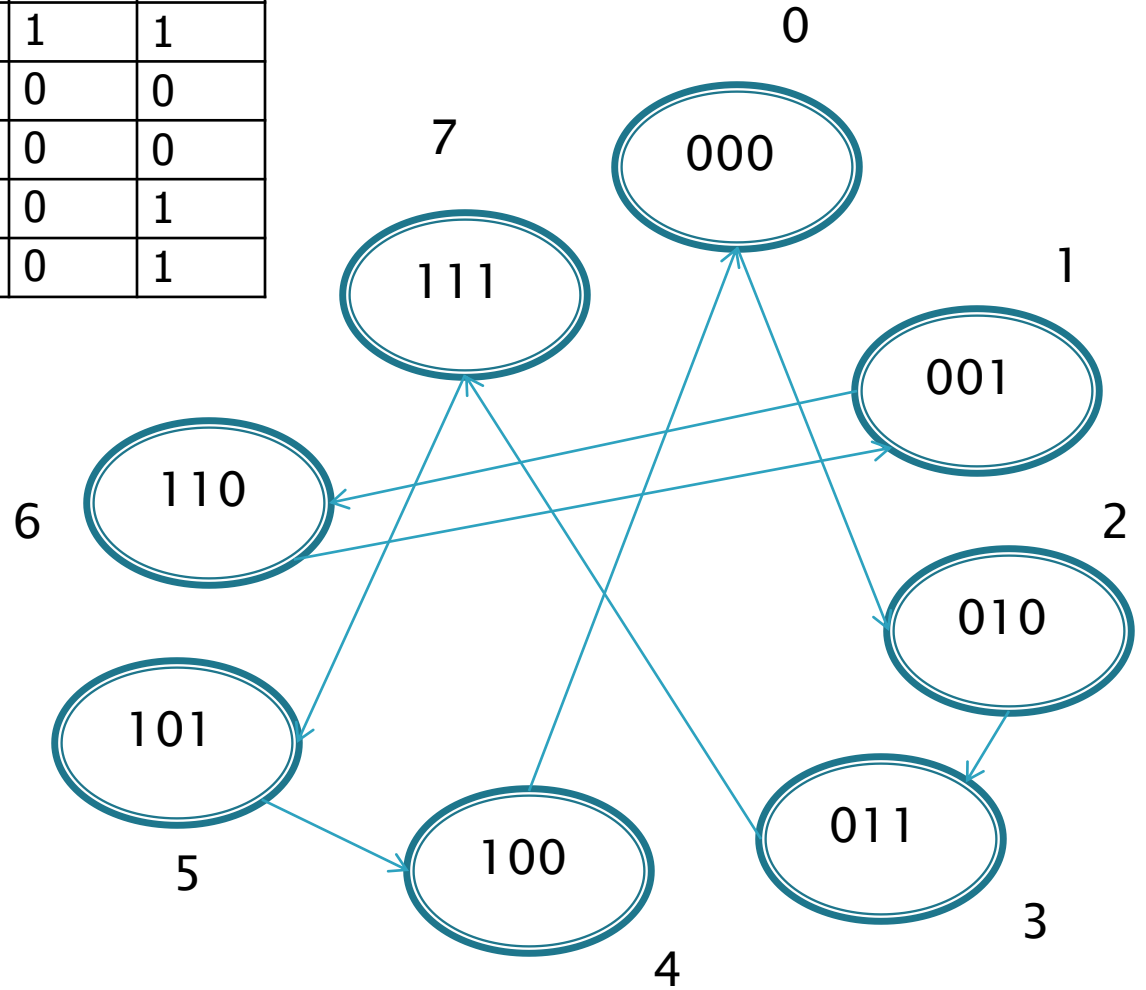

Two existing loops

1) 1 and 6

2) 7, 5, 4, 0, 2, 3

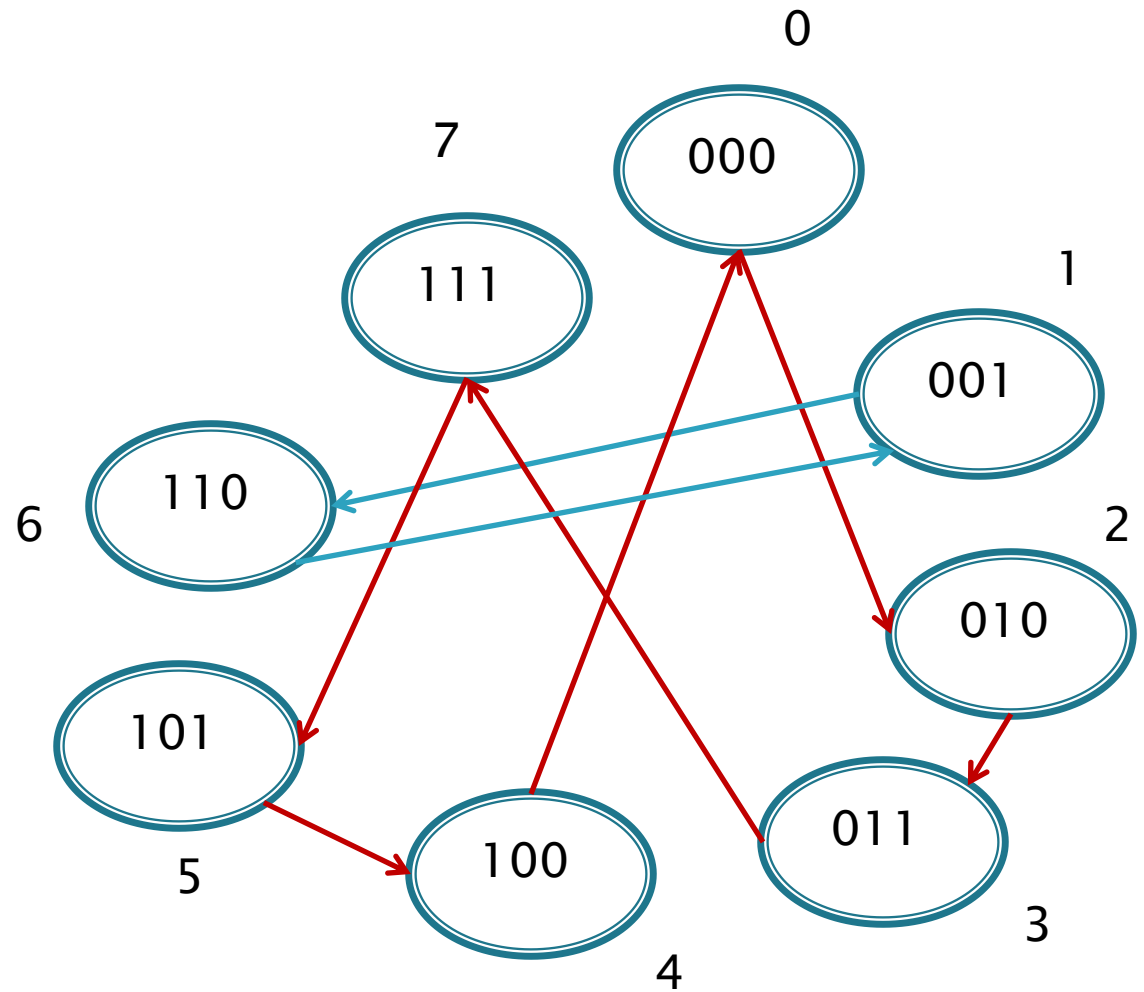


Not self-correcting counter


Two existing loops

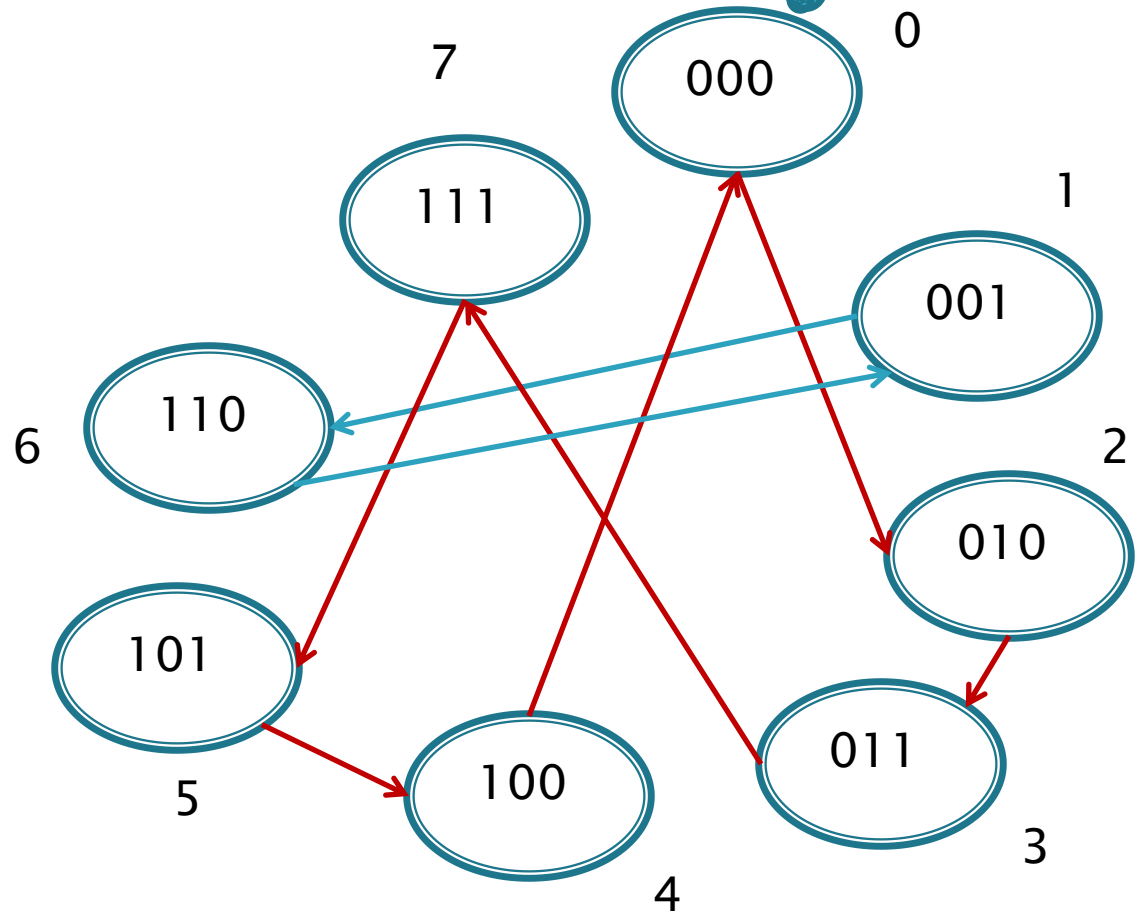- 1) 1 and 6
- 2) 7, 5, 4, 0, 2, 3

Self correcting counter contains only one loop




# Programmable counters

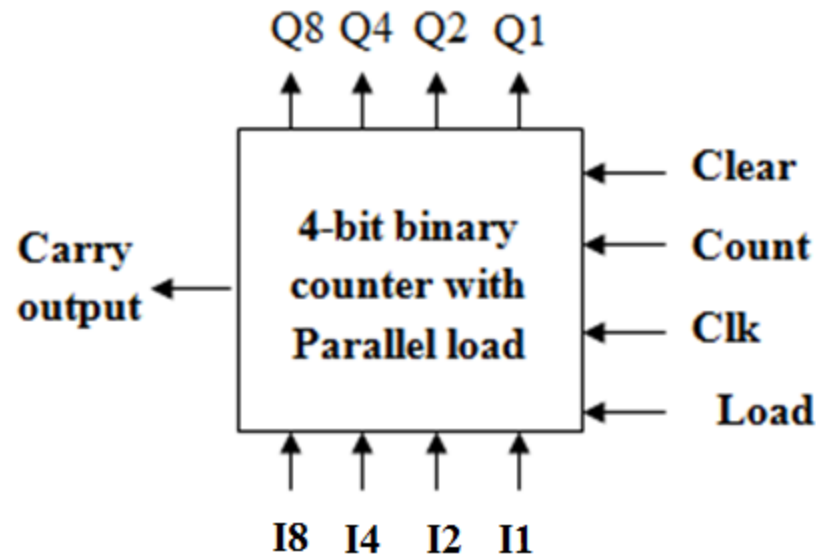


Clear	Clk	Load	Count	Function
0	X	X	X	Clear all
1	↑	1	X	Load input
1	↑	0	1	count
1	↑	0	0	No change


# Programmable counters

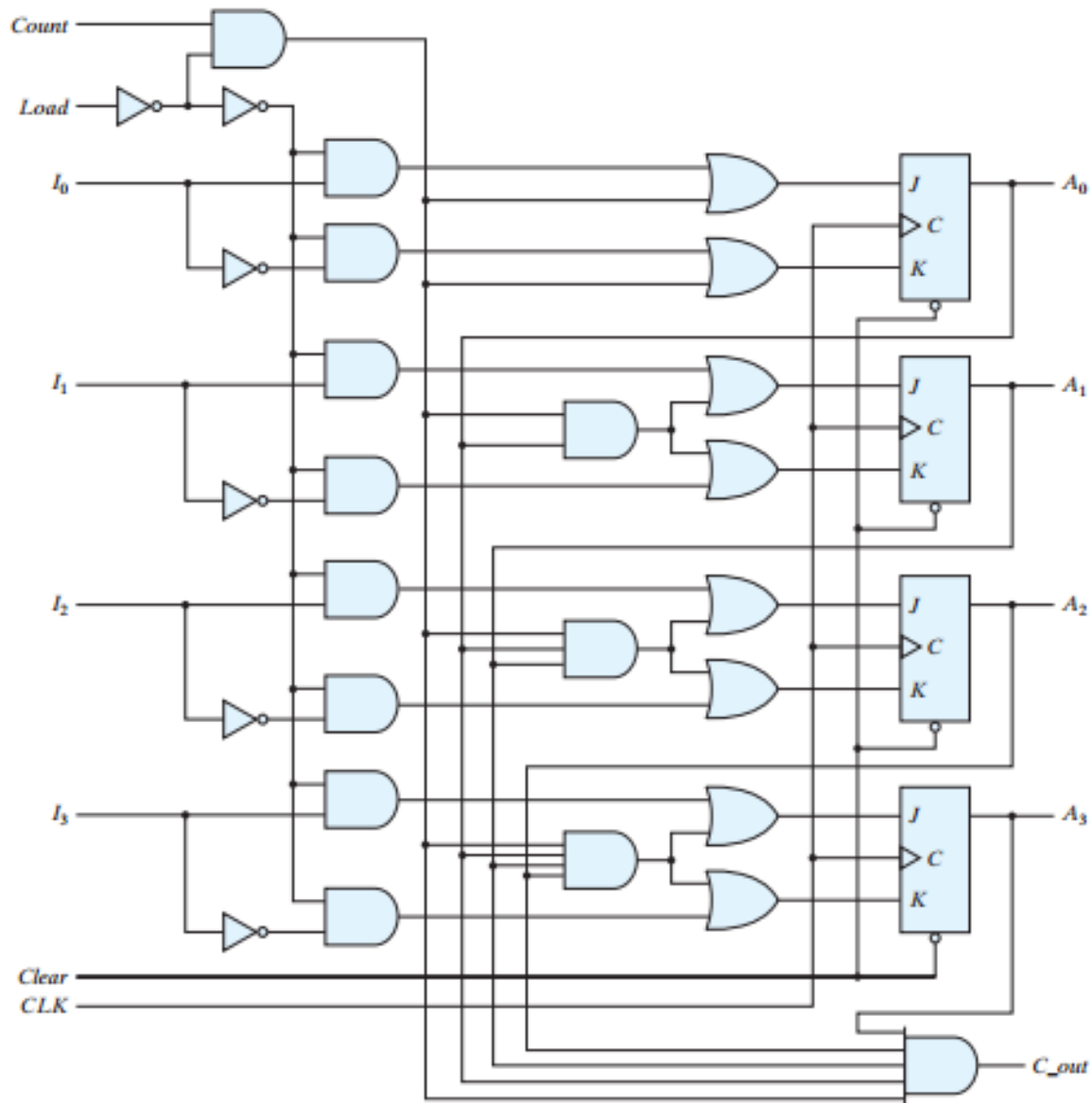

# Frequency division ( $F/n$ )

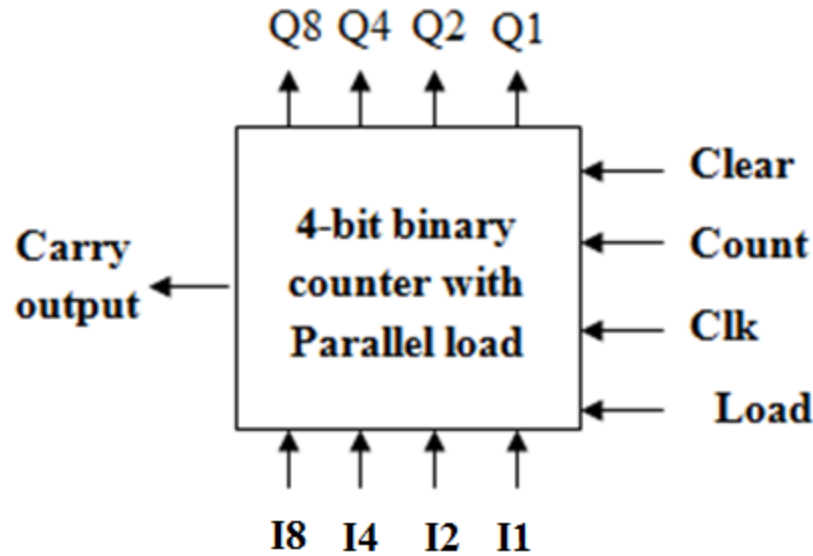

# Frequency division (power of 2)

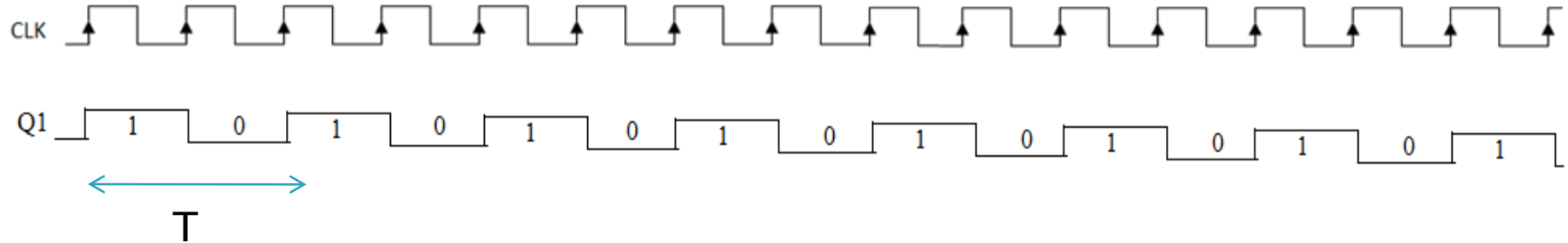


$$T_{Q1} = 2 T_{clk}$$

$$F_{Q1} = 1 / 2 T_{clk}$$

$$F_{Q1} = F_{clk} / 2$$



# Frequency division (power of 2)

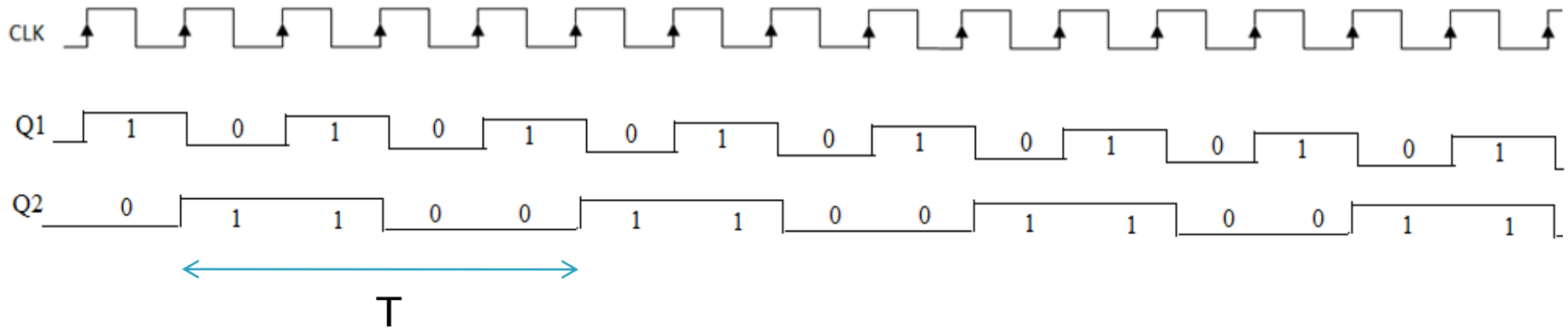


$$T_{Q2} = 4 T_{clk}$$

$$F_{Q2} = 1 / 4 T_{clk}$$

$$F_{Q2} = F_{clk} / 4$$

# Frequency division (power of 2)

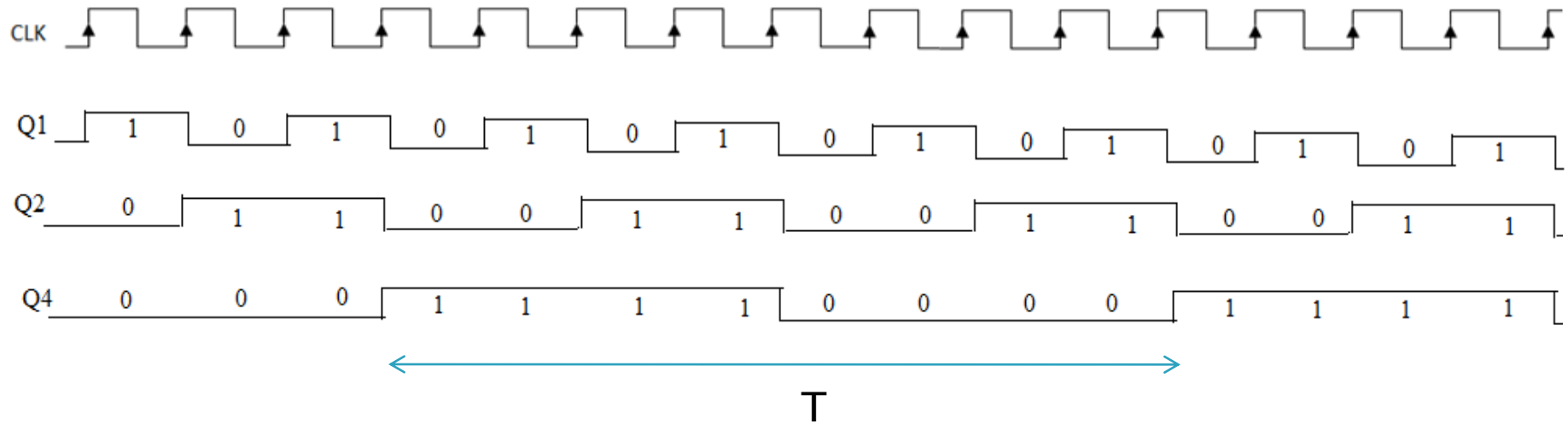


$$T_{Q4} = 8 T_{clk}$$

$$F_{Q4} = 1 / 8 T_{clk}$$

$$F_{Q4} = F_{clk} / 8$$

# Frequency division (power of 2)

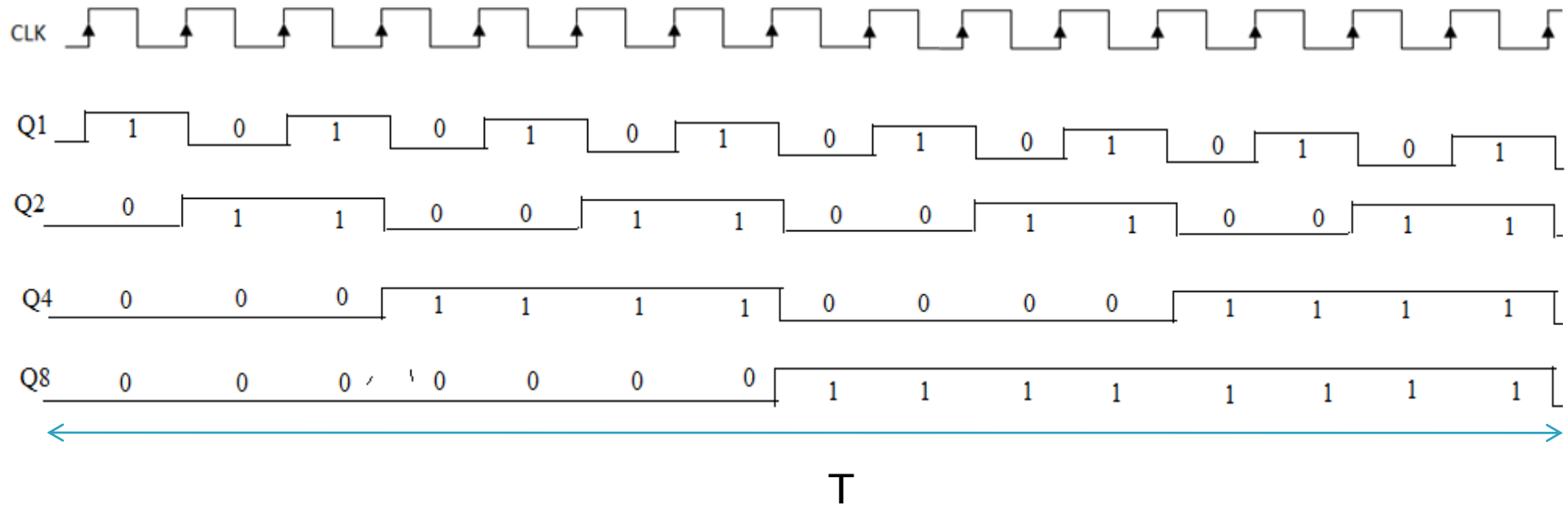


$$T_{Q8} = 16 T_{clk}$$

$$F_{Q8} = 1 / 16 T_{clk}$$

$$F_{Q8} = F_{clk} / 16$$

# Frequency division (power of 2)

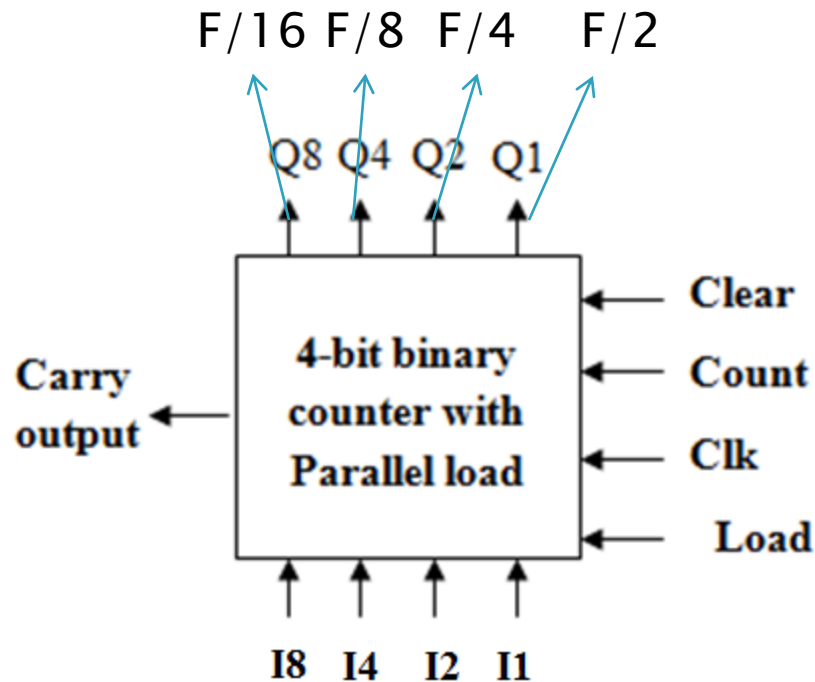

# Frequency division (F/n)

- ▶ Counter mod n
- ▶ Ex: n= 6 to get f/6

From the beginning ( using load)


Q8	Q4	Q2	Q1	load
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1

# Frequency division (F/n)

- ▶ Counter mod n
- ▶ Ex: n= 6 to get f/6



From the beginning ( using load)

Q8	Q4	Q2	Q1	load
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1

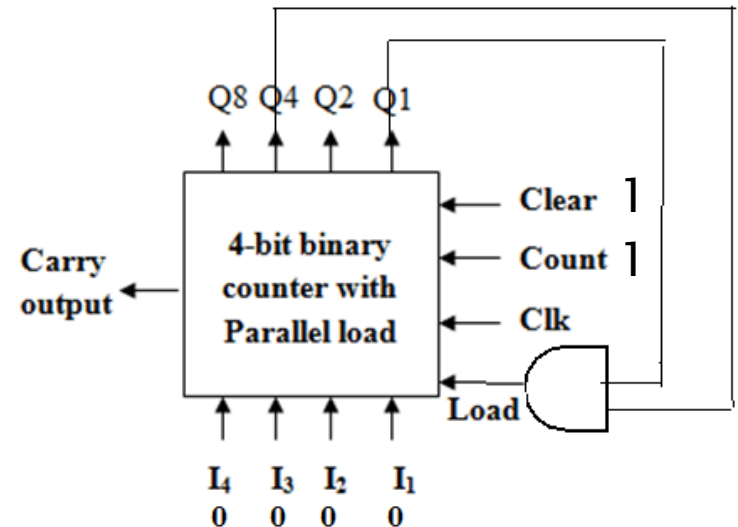

# Frequency division (F/6)

Q8	Q4	Q2	Q1	load
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1

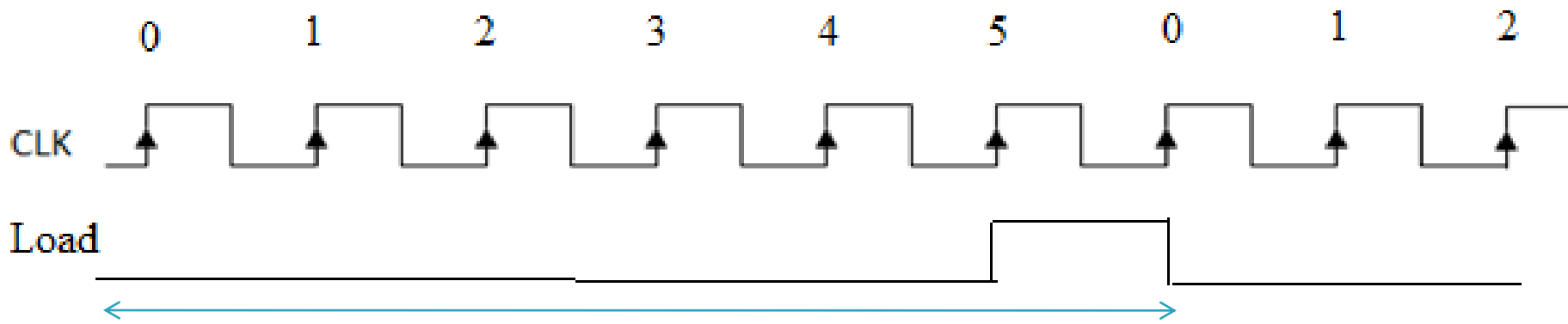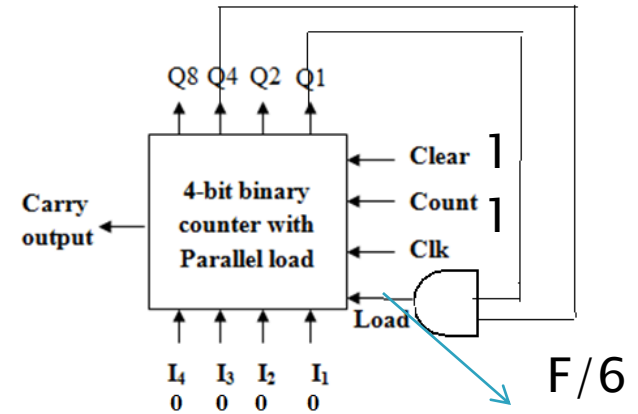

$T_{load}$

$$T_{load} = 6 T_{clk}$$

$$F_{load} = 1 / 6 T_{clk}$$

$$F_{load} = F_{clk} / 6$$

# Frequency division (F/n)

- ▶ Counter mod n
- ▶ Ex: n= 6 to get f/6

From the beginning ( using clear)

Q8	Q4	Q2	Q1	clear
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0




# Frequency division (F/n)

- ▶ Counter mod n
- ▶ Ex: n= 6 to get f/6

From the beginning ( using clear)

Q8	Q4	Q2	Q1	clear
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0

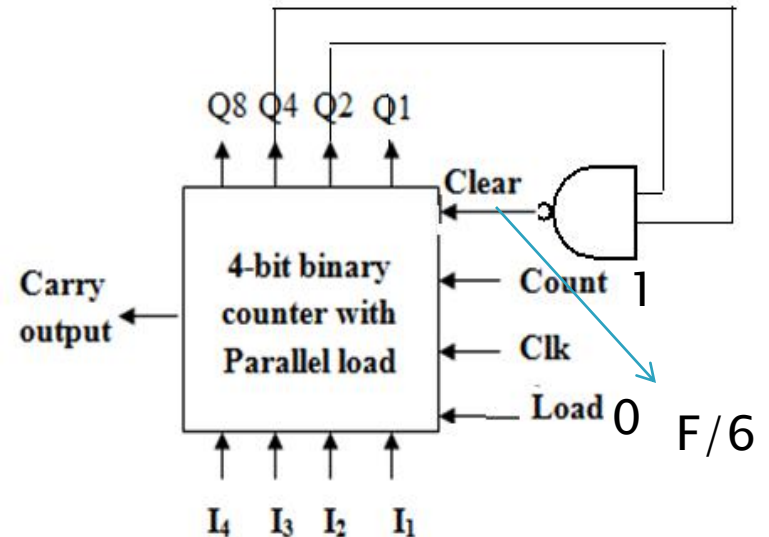

# Frequency division (F/n)

- ▶ Counter mod n
- ▶ Ex:  $n = 6$  to get  $f/6$

From the middle


Q8	Q4	Q2	Q1	load
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1

# Frequency division (F/n)

- ▶ Counter mod n
- ▶ Ex:  $n = 6$  to get  $f/6$

From the middle

Q8	Q4	Q2	Q1	load
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1

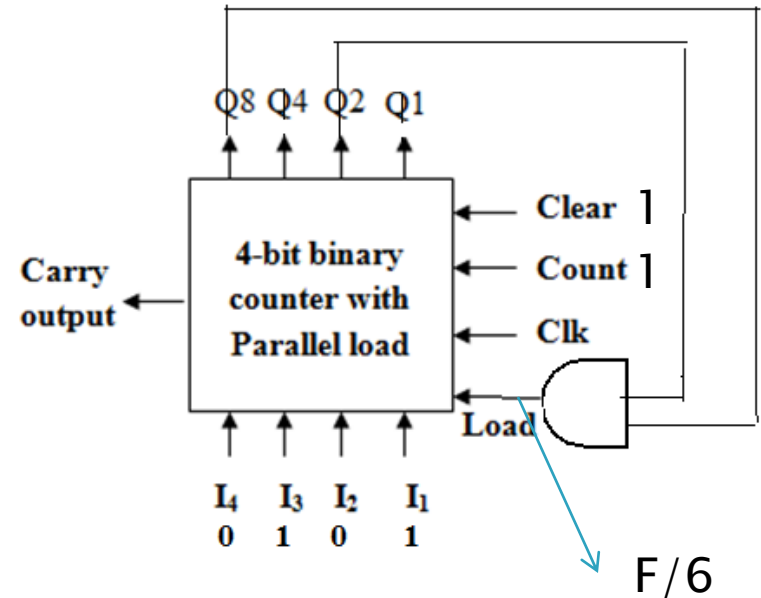

# Frequency division (F/n)

- ▶ Counter mod n
- ▶ Ex: n= 6 to get f/6

From the end


Q8	Q4	Q2	Q1	load
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

# Frequency division (F/n)

- ▶ Counter mod n
- ▶ Ex: n= 6 to get f/6

From the end

Q8	Q4	Q2	Q1	load
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

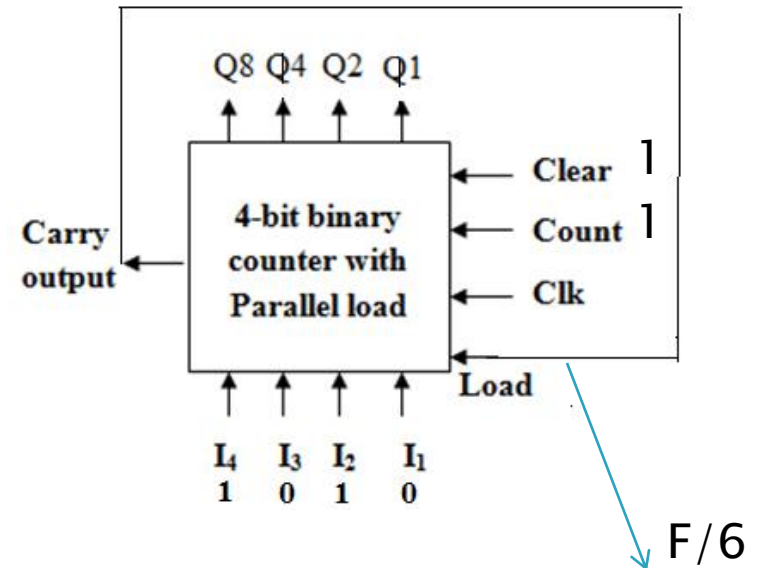

**Next Lecture we will explain  
Computer Memories  
Thank you**

