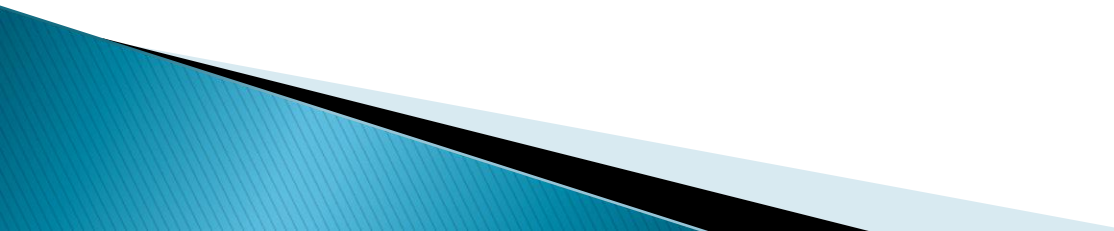


Digital Design

Lecture of week 11 part 2

Dr Manal Tantawi


Computer Memories

- 1) Registers ✓✓
 - 2) RAM (self read not included in final exam)
 - 3) ROM (self read not included in final exam)
- 

Registers


- ▶ 4 bit register with parallel load

 Only one clock is needed to upload an input




Registers

- ▶ 4 bit shift register (right or left)

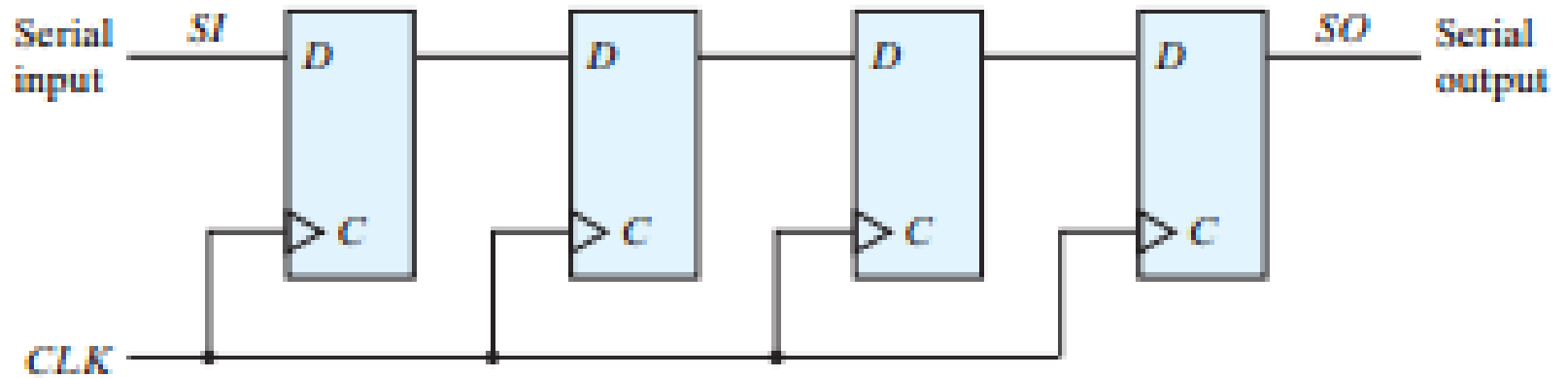

Registers

▶ 4 bit shift register (right)

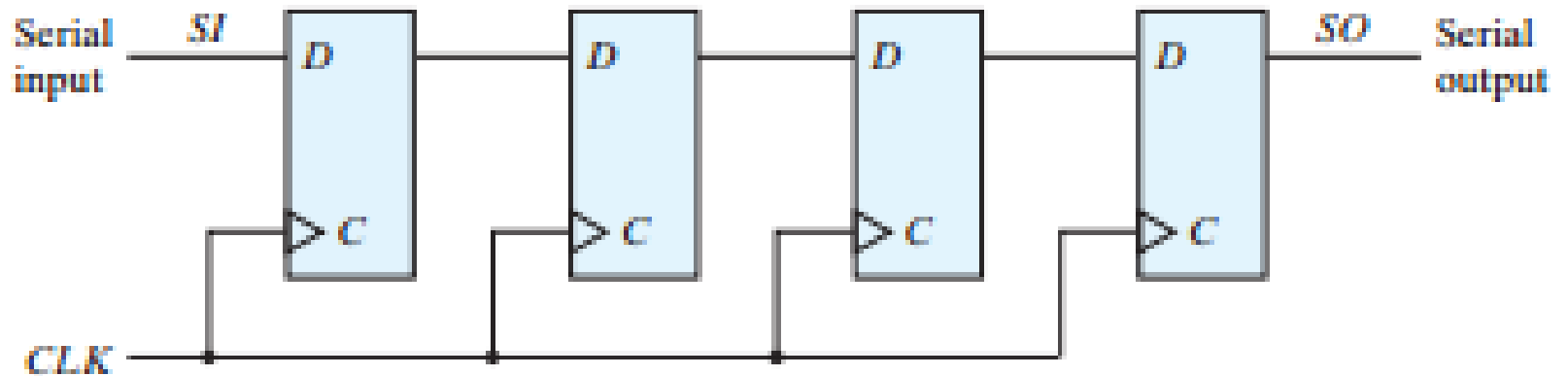


	1	0	1	0
CLK 1	0	1	0	1
CLK 2	0	0	1	0
CLK 3	0	0	0	1
CLK 4	0	0	0	0

4 clocks are needed



Shift register

- ▶ Serial transfer ($B = A$)

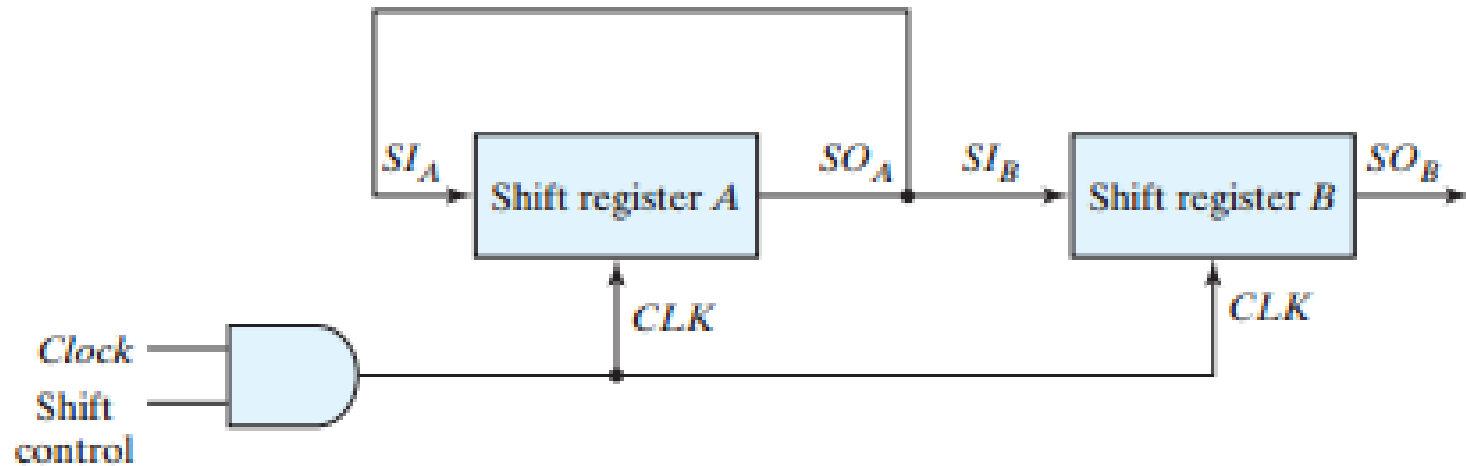

Shift register


- ▶ Serial transfer ($B = A$)

 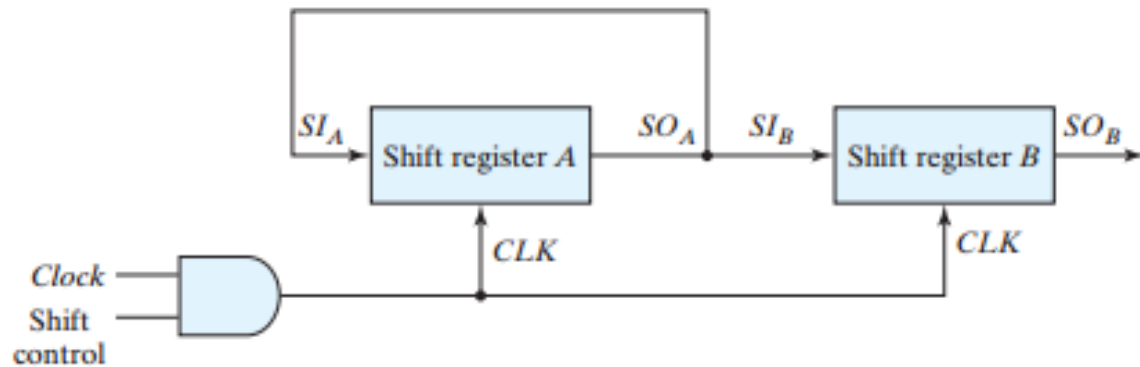

(b) Timing diagram


Shift register


- Serial transfer (B = A)

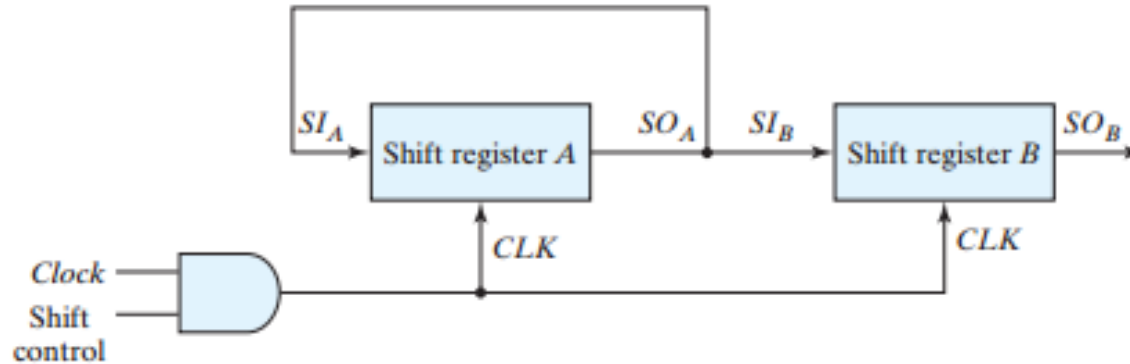


Timing Pulse	Shift Register A				Shift Register B			
Initial value	1	0	1	1	0	0	1	0
After T_1	1	1	0	1	1	0	0	1
After T_2	1	1	1	0	1	1	0	0
After T_3	0	1	1	1	0	1	1	0
After T_4	1	0	1	1	1	0	1	1

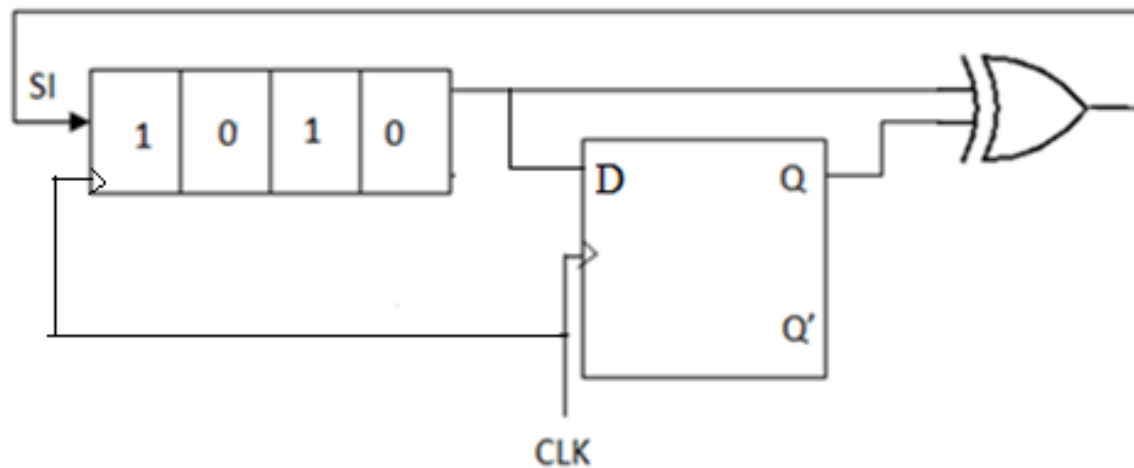Find the content of the register after 4 clocks (initial value for $Q = 0$)




 


clocks	SI Last bit \oplus Q	Register content	D =Last bit	Q
	0	1 0 1 <u>0</u>	0	<u>0</u>
CLK 1	1	0 1 0 <u>1</u>	1	<u>0</u>

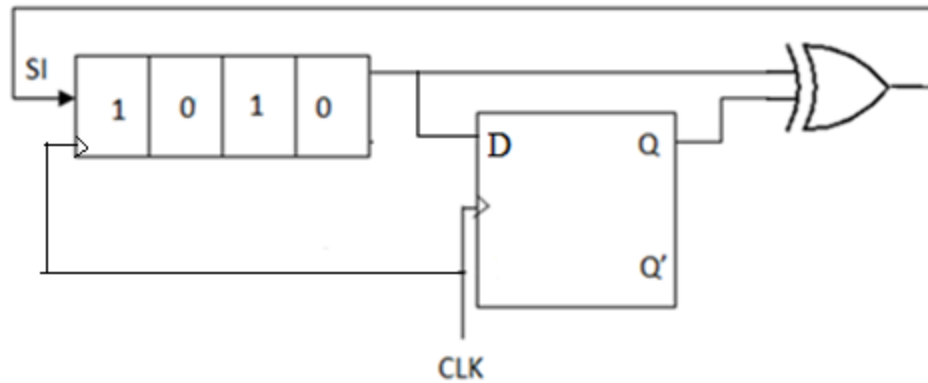

clocks	SI Last bit \oplus Q	Register content	D =Last bit	Q
	0	1 0 1 <u>0</u>	0	<u>0</u>
CLK 1	1	0 1 0 <u>1</u>	1	<u>0</u>
CLK 2	1	1 0 1 <u>0</u>	0	<u>1</u>

 

clocks	SI Last bit \oplus Q	Register content	D =Last bit	Q
	0	1 0 1 <u>0</u>	0	<u>0</u>
CLK 1	1	0 1 0 <u>1</u>	1	<u>0</u>
CLK 2	1	1 0 1 <u>0</u>	0	<u>1</u>
CLK 3	1	1 1 0 <u>1</u>	1	<u>0</u>

 

clocks	SI Last bit \oplus Q	Register content	D =Last bit	Q
	0	1 0 1 <u>0</u>	0	<u>0</u>
CLK 1	1	0 1 0 <u>1</u>	1	<u>0</u>
CLK 2	1	1 0 1 <u>0</u>	0	<u>1</u>
CLK 3	1	1 1 0 <u>1</u>	1	<u>0</u>
CLK 4		1 1 1 <u>0</u>		<u>1</u>

Serial Adder

$X + Y + Z + W$ (each of them is 4 bits)

Register A



X

Register A



$X + Y$

Register A



$X + Y + Z$

Register B



Y

Register B



Z

Register B



W

1


2

3

(4 clocks)

(4 clocks)

Serial Adder

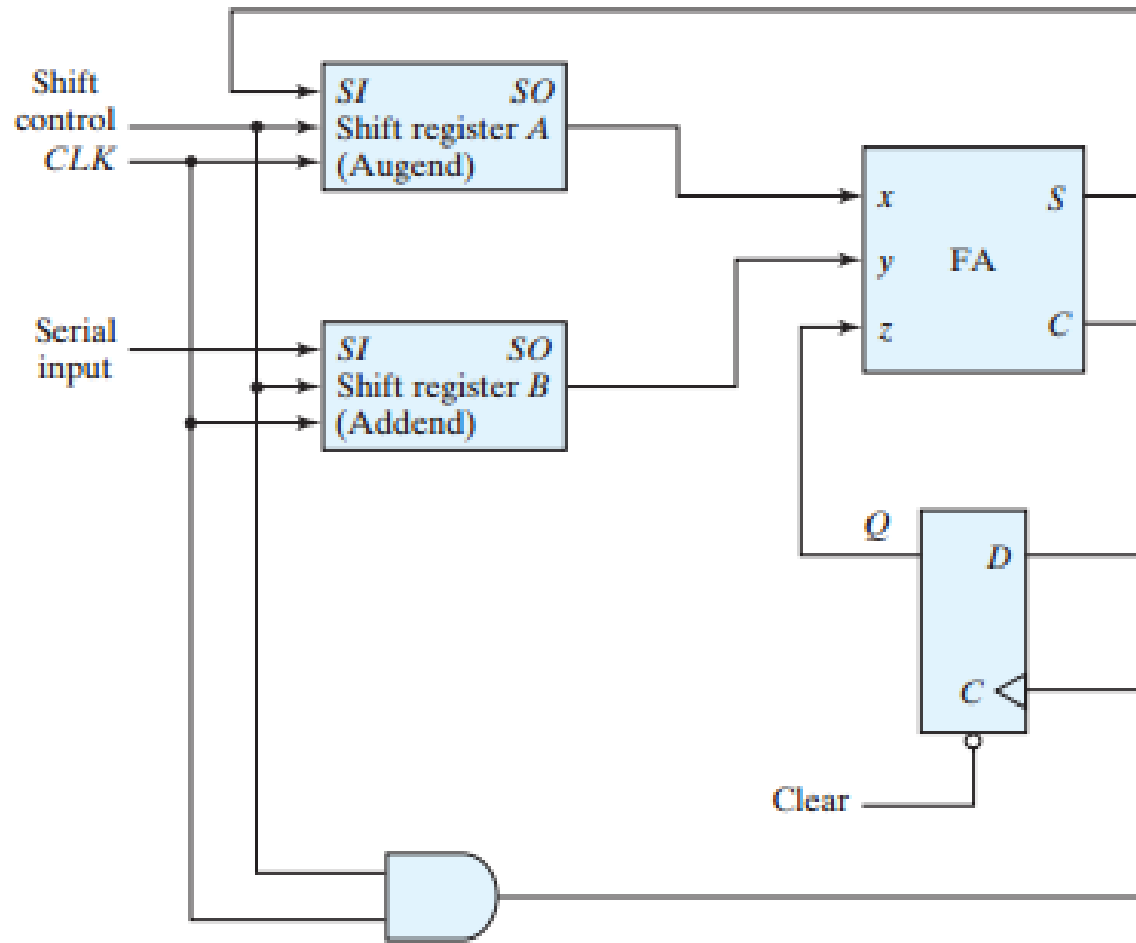

Serial Adder

X = 0 1 0 1

Register A

Y = 0 0 1 1

Register B

Z = 0 1 1 1

Clocks	Sl _A = S	Register A	Sl _B	Register B	D = C	Q	C	S
	0	0 1 0 <u>1</u>	1	0 0 1 <u>1</u>	1	<u>0</u>	1	0
CLK1	0	0 0 1 <u>0</u>	1	1 0 0 <u>1</u>	1	<u>1</u>	1	0
CLK2	0	0 0 0 <u>1</u>	1	1 1 0 <u>0</u>	1	<u>1</u>	1	0
CLK3	1	0 0 0 <u>0</u>	0	1 1 1 <u>0</u>	0	<u>1</u>	0	1
CLK4		1 0 0 <u>0</u>		0 1 1 <u>1</u>		<u>0</u>		





X + Y




Z

Selection circuit (remember)

  


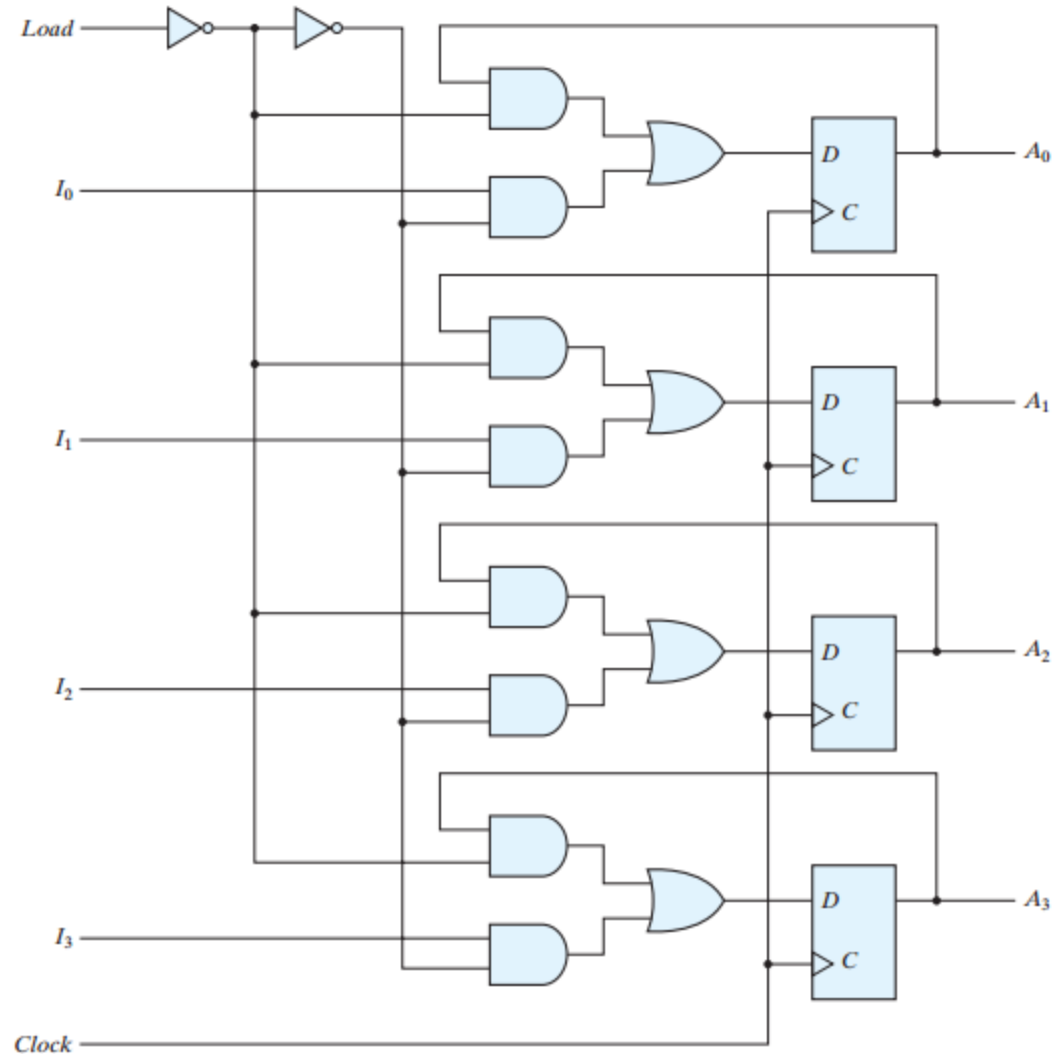4 bit register with parallel load \ no change




4 bit register with parallel load \ no change

Load = 0
no change

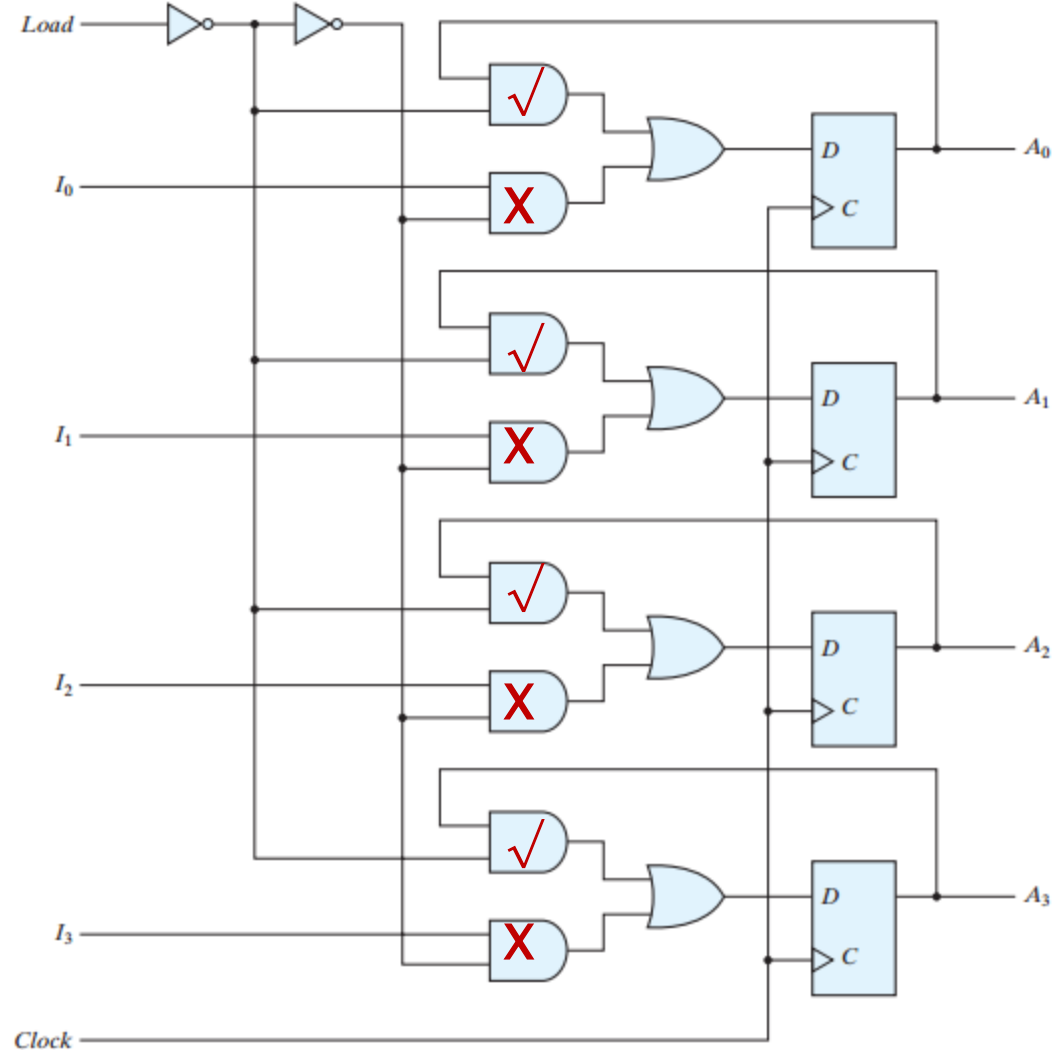


4 bit register with parallel load \ no change

Load = 1
Parallel load

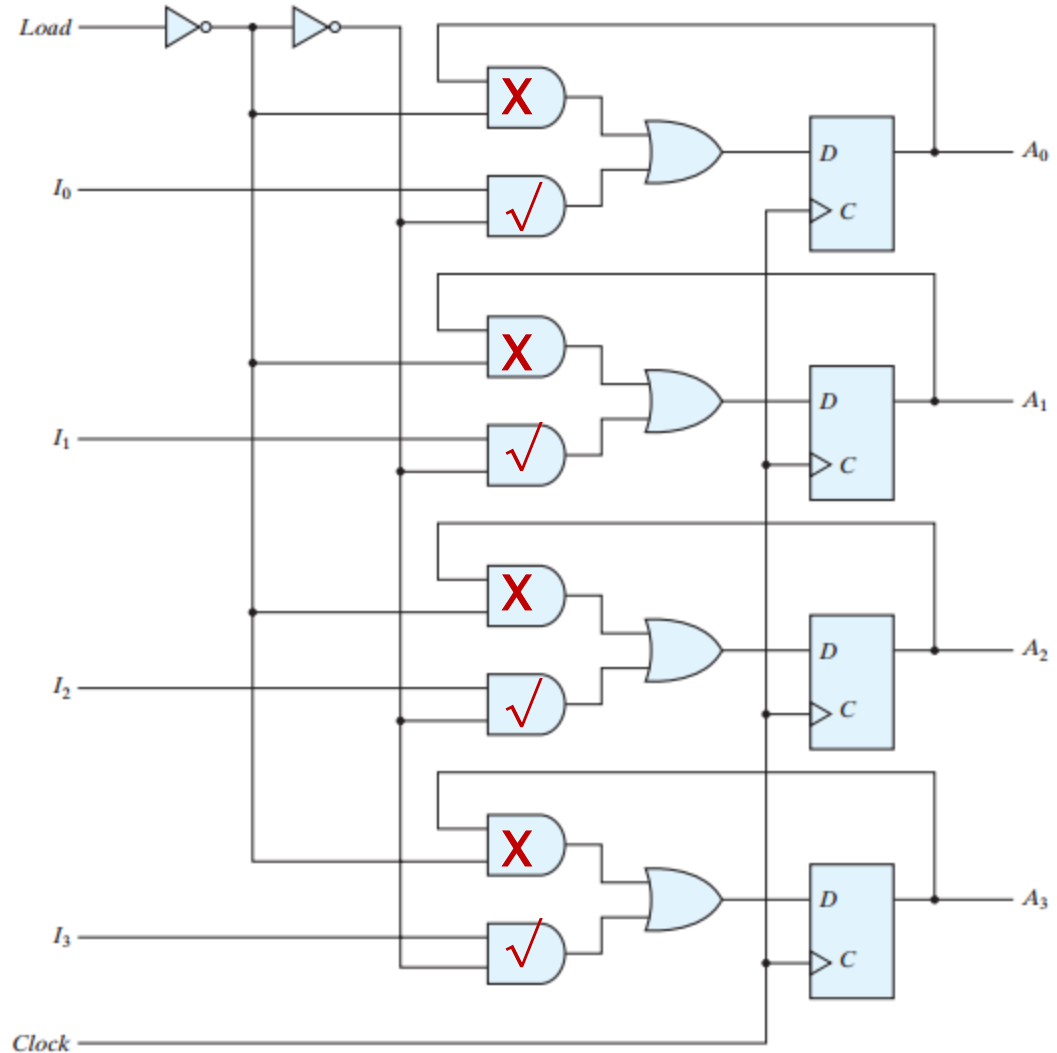

4 bit Universal Shift Register example 1

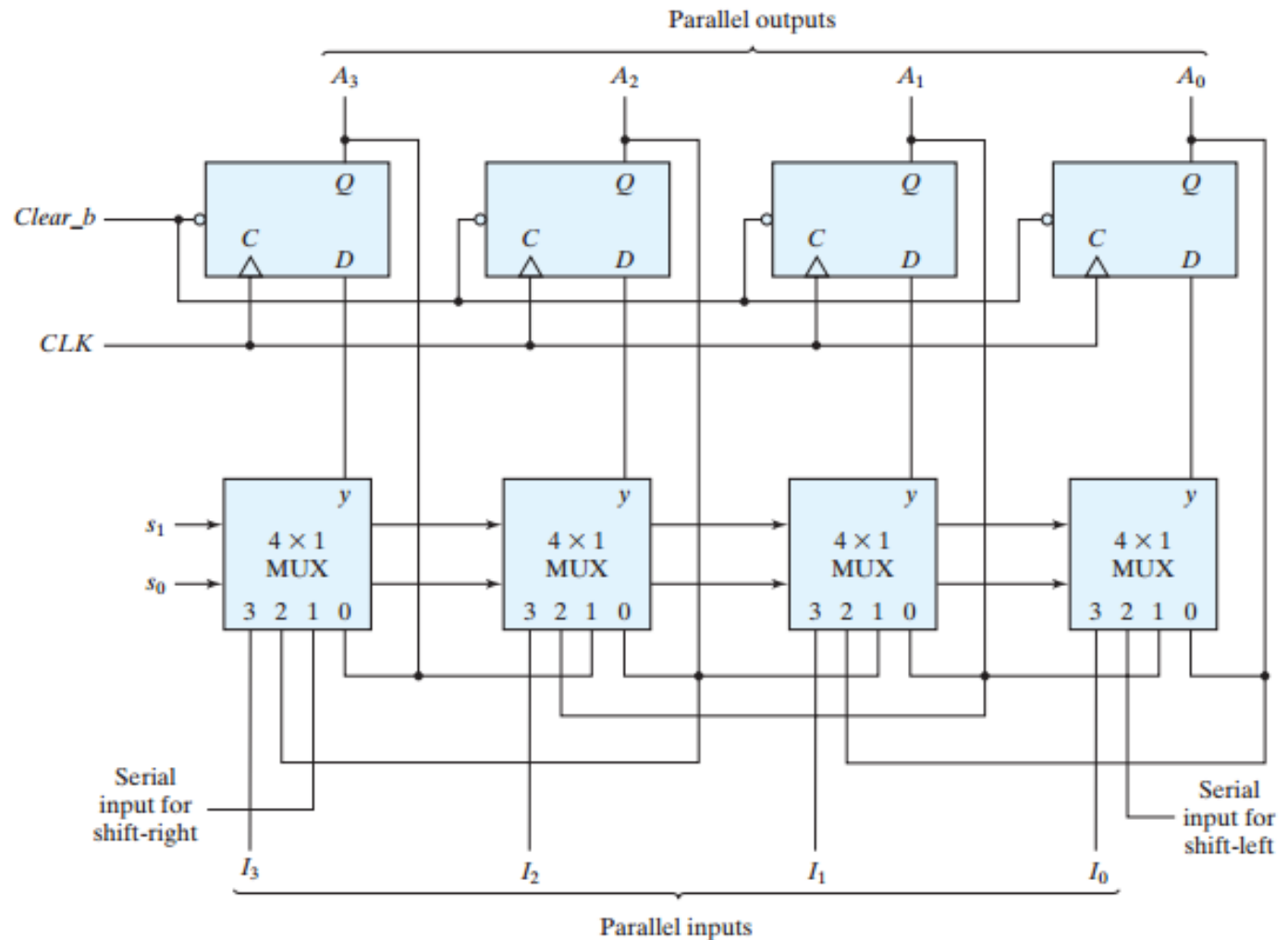


4 bit Universal Shift Register (cont.) example 1

Function table

Mode Control		Register Operation
s_1	s_0	
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load

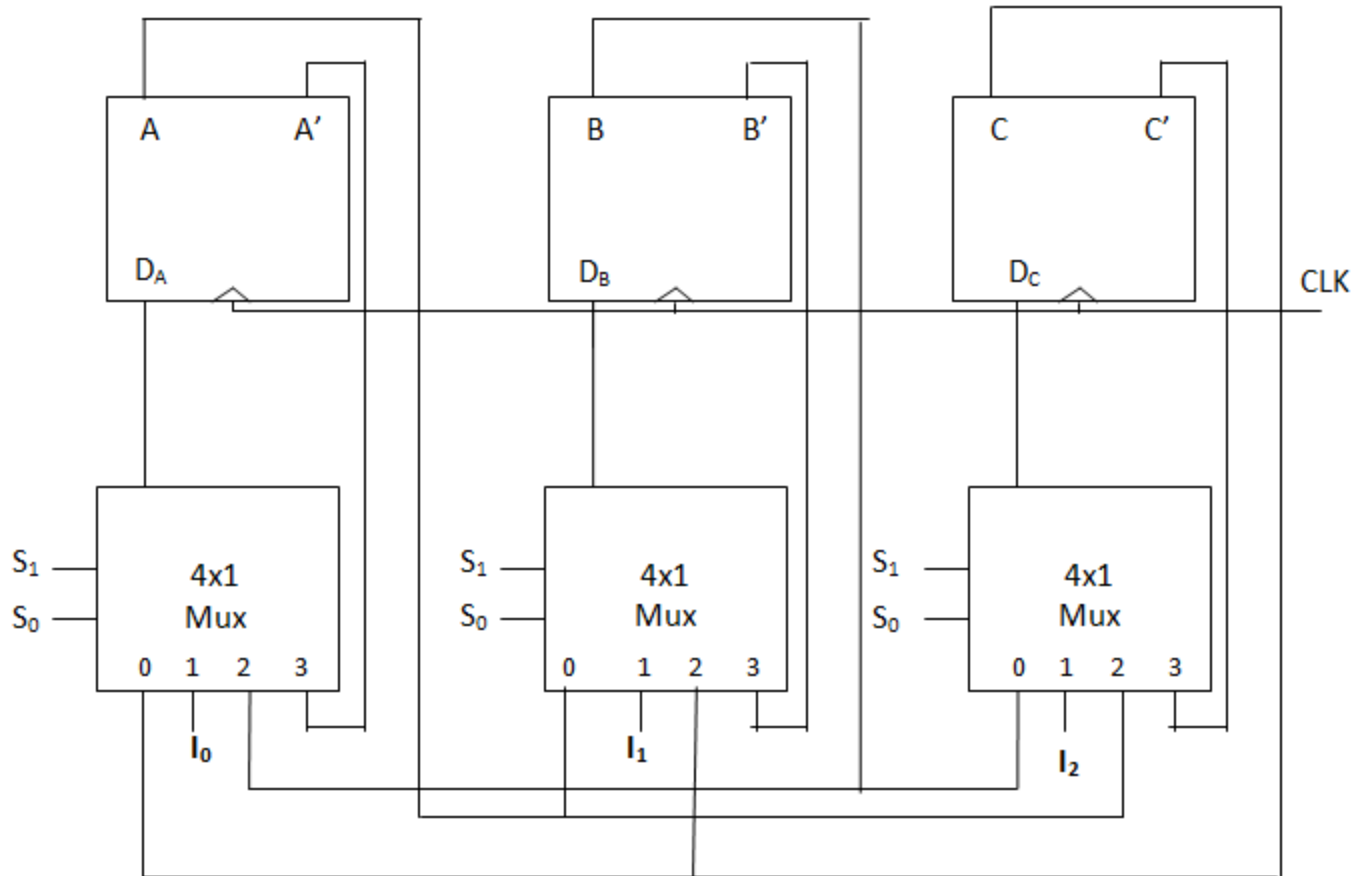3 bit Universal Shift Register(cont.) example 2




3 bit Universal Shift Register (cont.) example 2

Function table

S0	S1	Register operation
0	0	Circular shift right
0	1	Parallel Load
1	0	Circular shift left
1	1	complement

Random Access Memory (RAM)

Different representations for OR gate

 

(a) Conventional symbol




(b) Array logic symbol

Ex: $A + B + C$





(a) Conventional symbol

 


(b) Array logic symbol

Memory unit (RAM)

 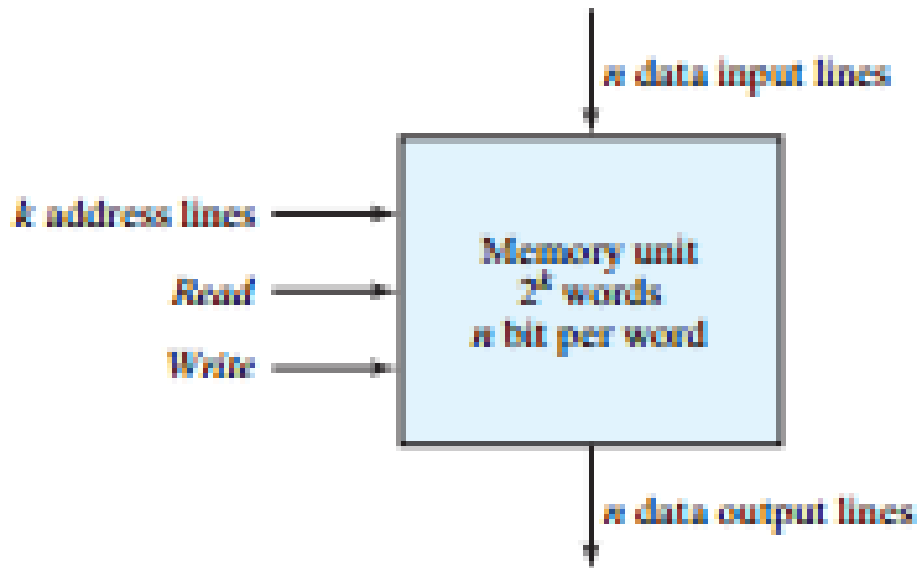

Memory unit (RAM)

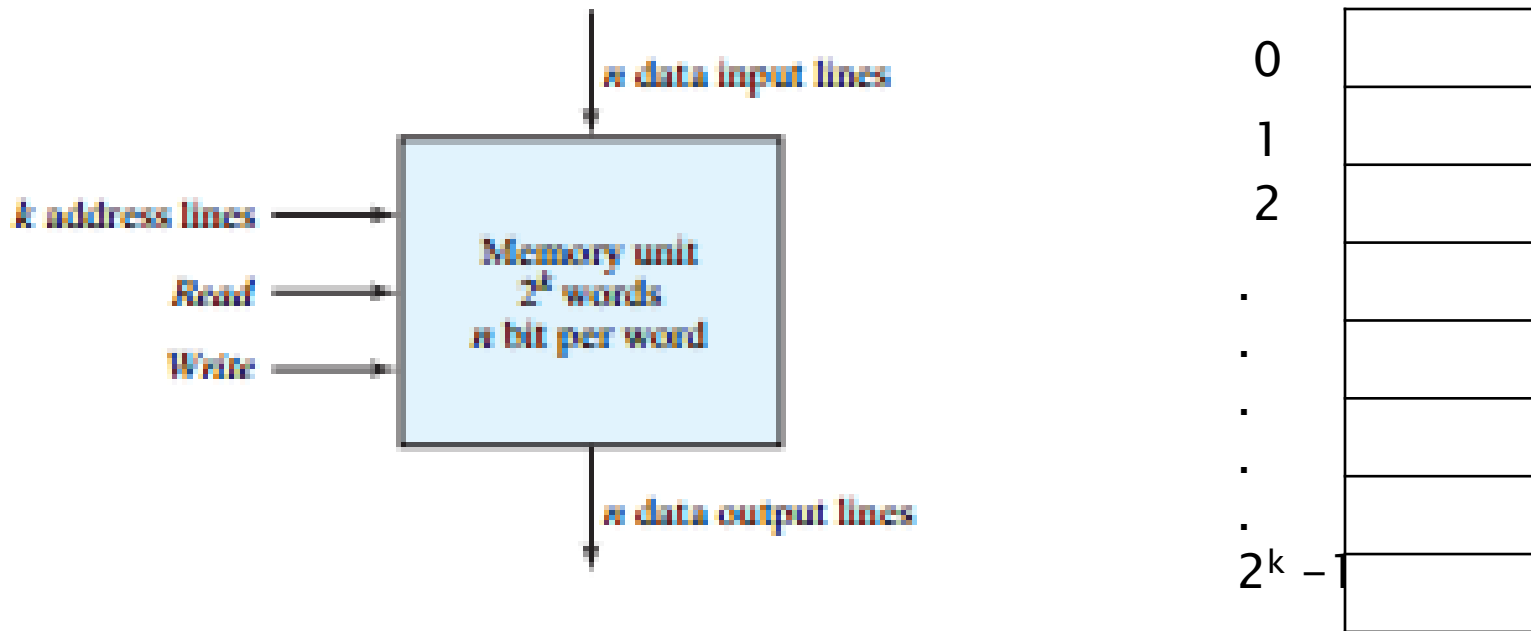

RAM size = # of words x word size

ex: 8 x 4 RAM

number of words = 8 = 2^3

Word size = number of inputs = number of outputs = 4

number of address lines = 3

A Binary Cell


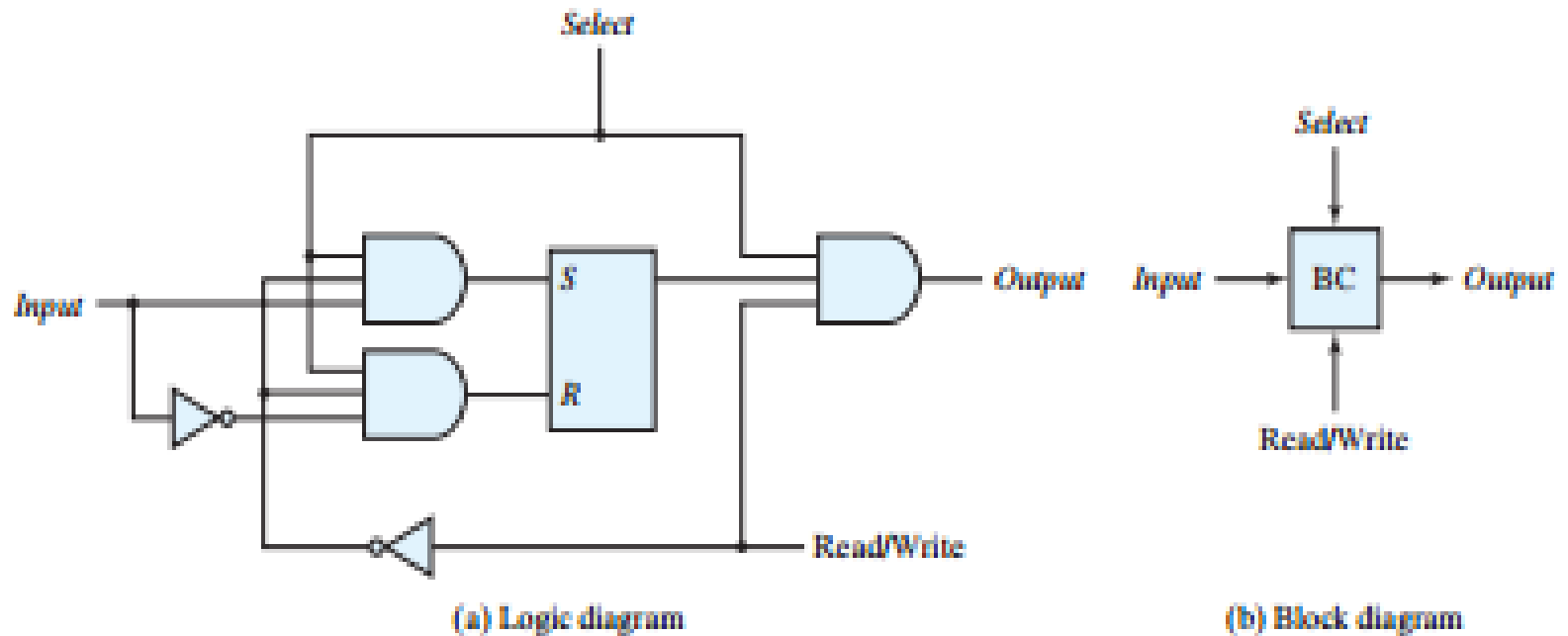


Diagram of a 4 x 4 RAM

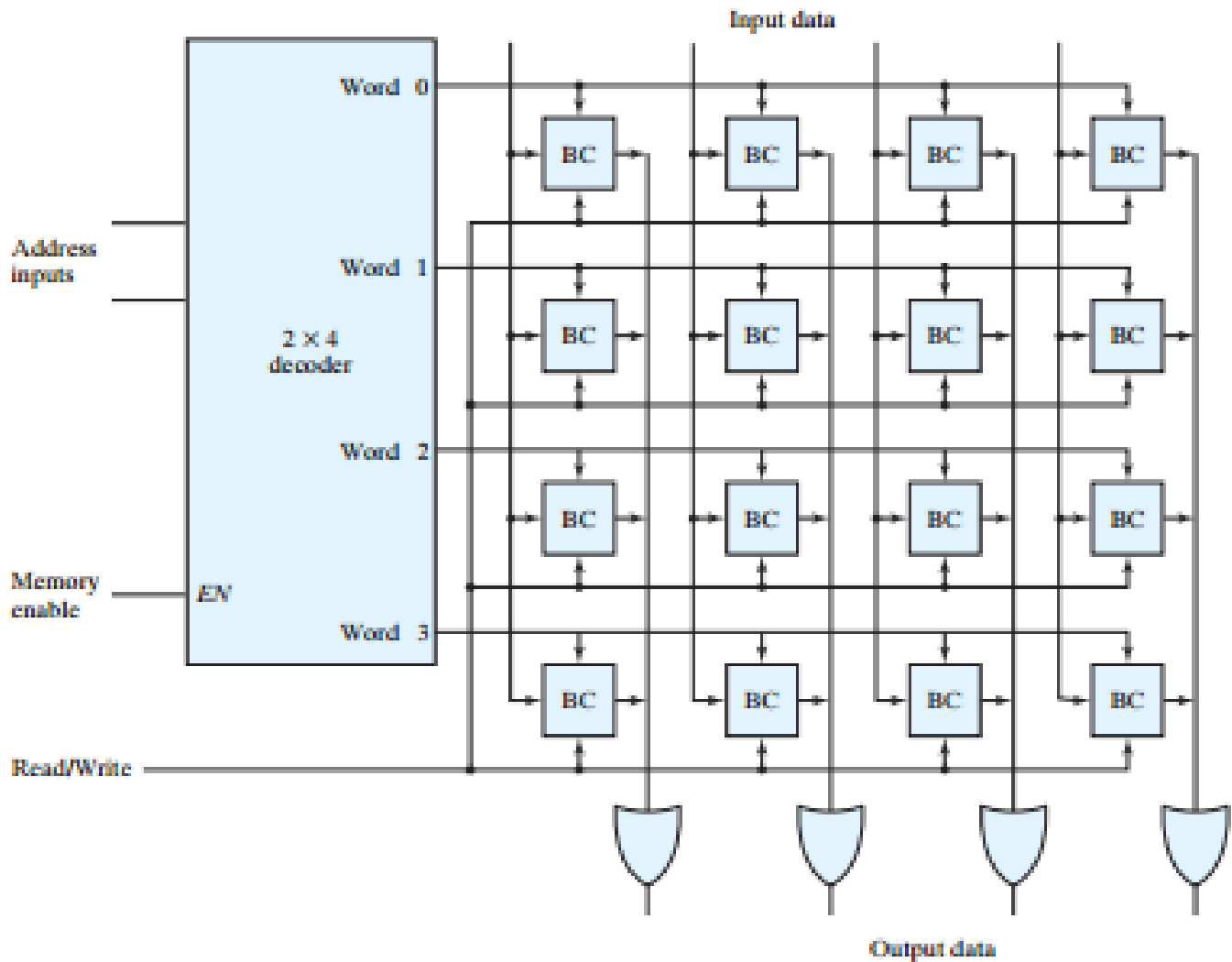

If we have 32M x 8 RAM then

▶ Kilobyte = 2^{10} Mega = 2^{20} Giga = 2^{30}

Number of words = $2^5 * 2^{20} = 2^{25}$

Word size = 8 bits


Number of inputs = 8

Number of outputs = 8


Number of address lines = 25

Decoder size = 25×2^{25}

Read-only Memory (ROM)

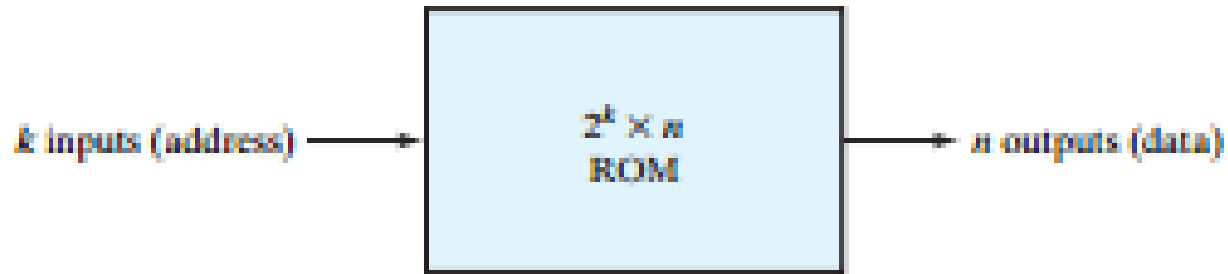

32 x 8 ROM

 

Example


ROM Truth Table (Partial)

Inputs					Outputs							
I_4	I_3	I_2	I_1	I_0	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
		⋮							⋮			
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

Programmed ROM

ROM Truth Table (Partial)

Inputs					Outputs							
I_4	I_3	I_2	I_1	I_0	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
		⋮							⋮			
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

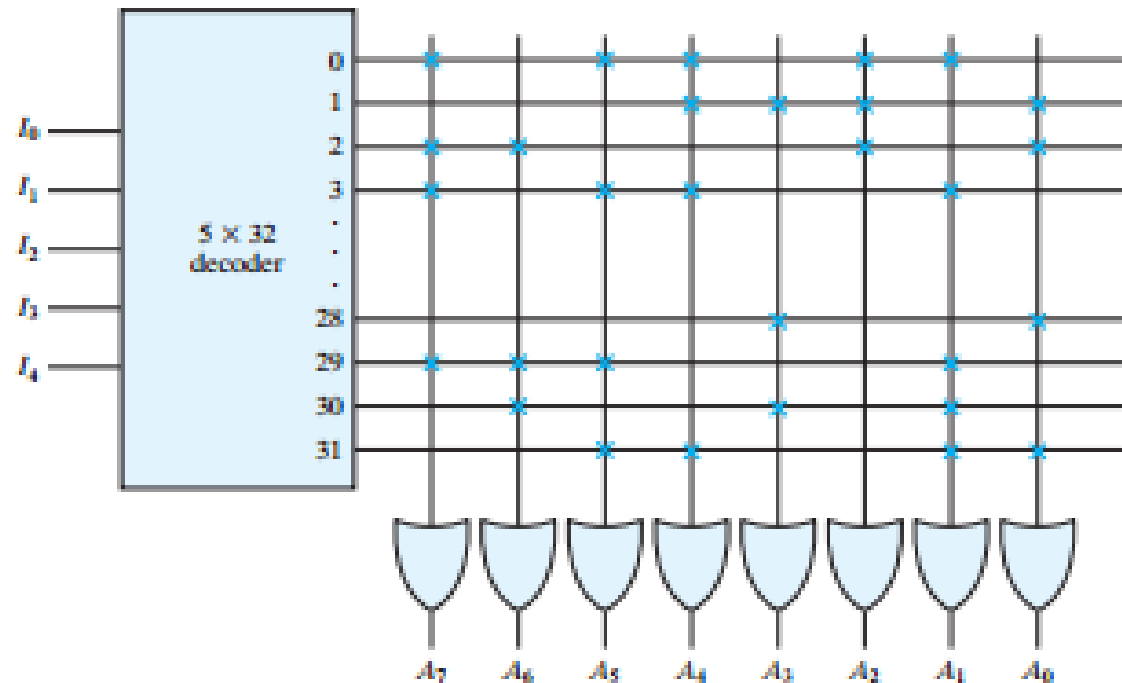

Thank you