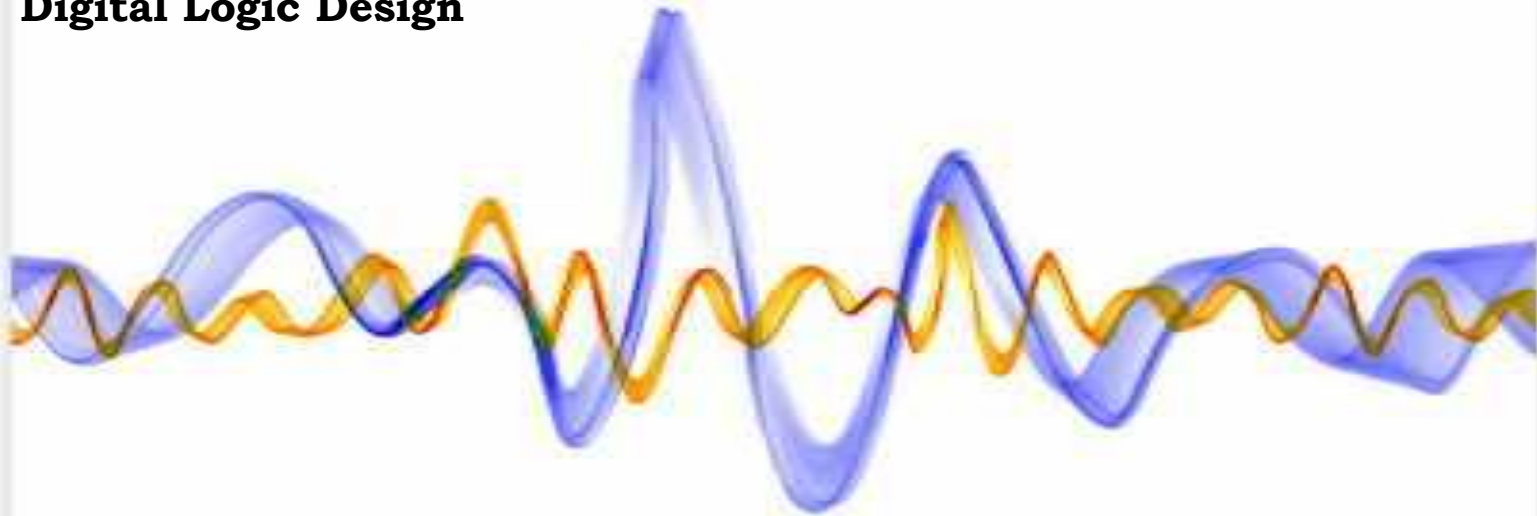


Digital Logic Design



Lecture 5:

Chapter 4: Combinational Logic

Mirvat Al-Qutt, Ph.D


Computer Systems Department , FCIS,
Ain Shams University



NAND-Only Implementation

- ▶ **NAND gate is a universal gate**
 - ▶ Can implement any digital system using NAND gate only

NAND

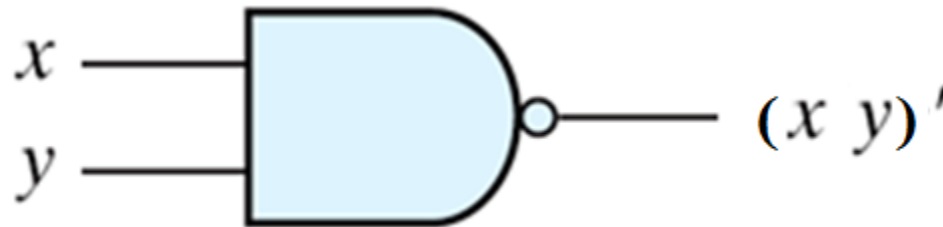


- ▶ **Universal gate** : we can implement all logic Operations with NAND Gates **ONLY**



NAND-Only Implementation

- ▶ **NAND gate is a universal gate**
 - ▶ Can implement any digital system using NAND gate only

AND

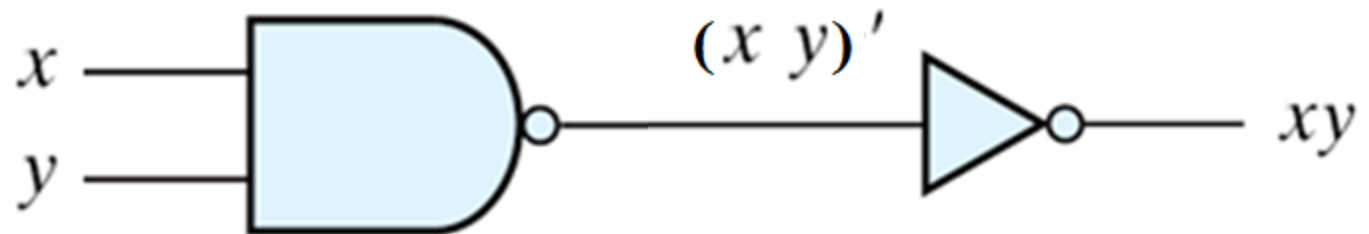


- ▶ **Universal gate** : we can implement all logic Operations with NAND Gates **ONLY**



NAND-Only Implementation

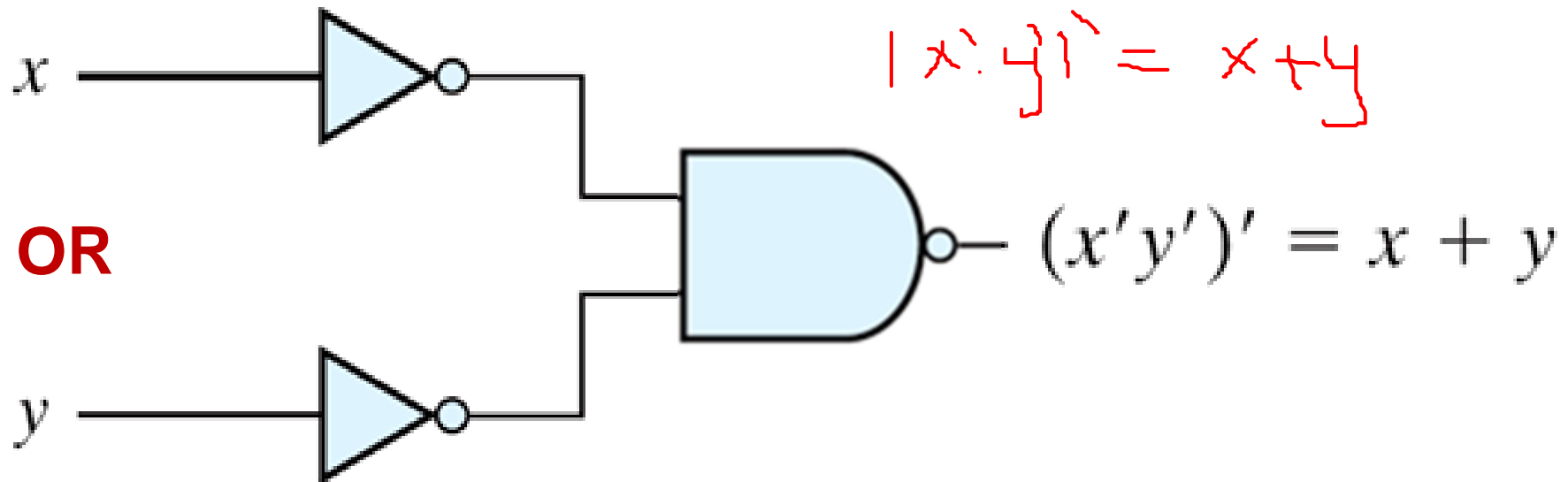- ▶ **NAND gate is a universal gate**
 - ▶ Can implement any digital system using NAND gate only




- ▶ **Universal gate** : we can implement all logic Operations with NAND Gates **ONLY**



NAND-Only Implementation

- ▶ **NAND gate is a universal gate**
 - ▶ Can implement any digital system using NAND gate only

Inverter

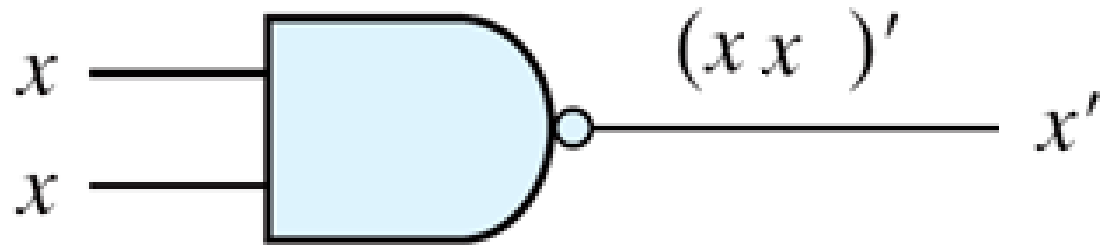

- ▶ **Universal gate** : we can implement all logic Operations with NAND Gates **ONLY**



NAND-Only Implementation

- ▶ **NAND gate is a universal gate**
 - ▶ Can implement any digital system


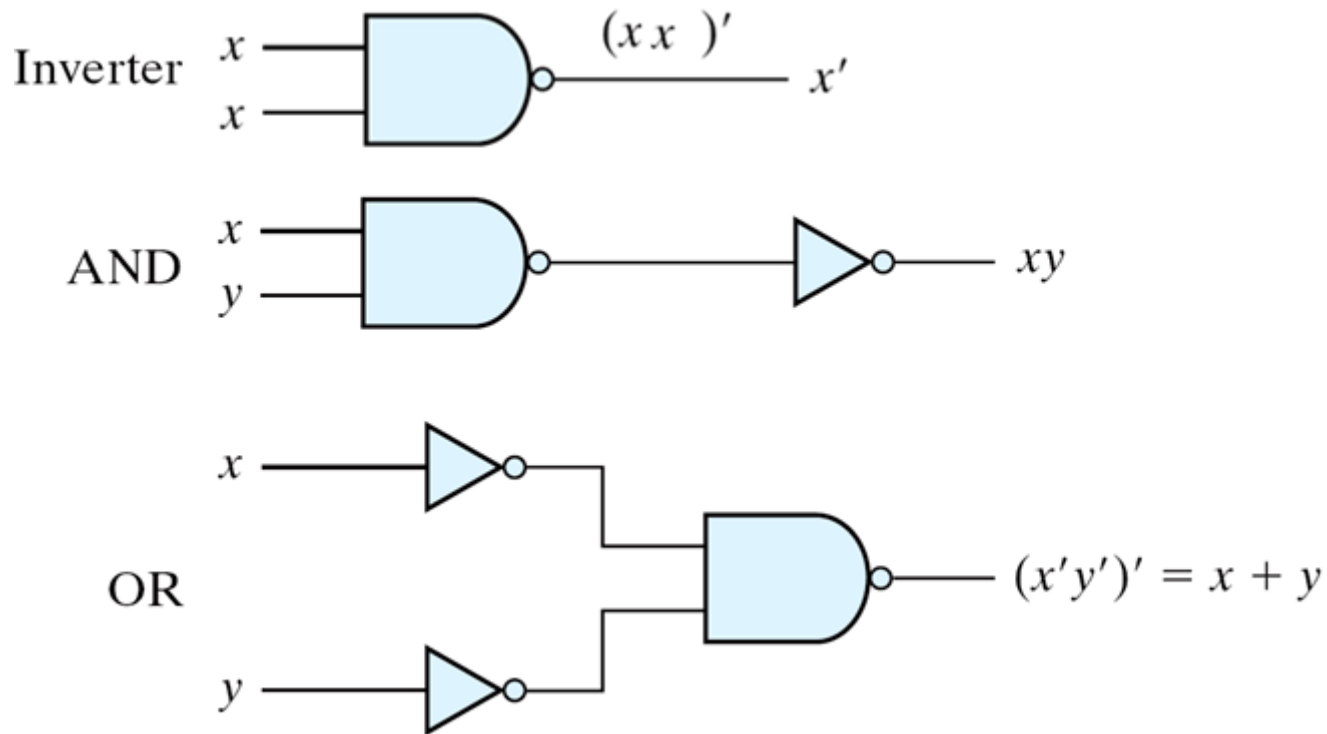


Figure 3.18 Logic Operations with NAND Gates

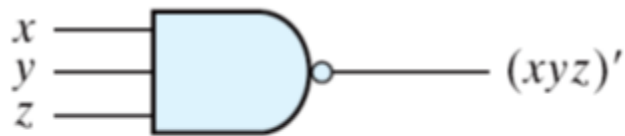

NAND Gate


- ▶ Two graphic symbols for a NAND gate



(a) AND-invert

$$(xyz)' = x' + y' + z'$$

By applying
DeMorgan's Theorem

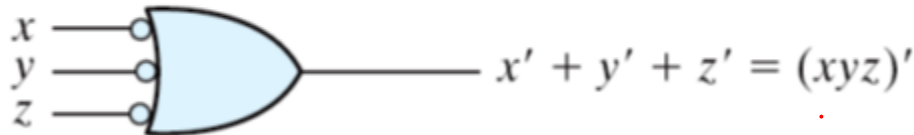

(b) Invert-OR






Two-level NAND-Only Implementation

- ▶ Two-level logic
 - ▶ NAND-NAND = sum of products
 - ▶ Example: $F = AB + CD$
 - ▶ $F = ((AB)' (CD)')' = AB + CD$


Three ways to implement $F = AB + CD$

NAND-Only Implementation

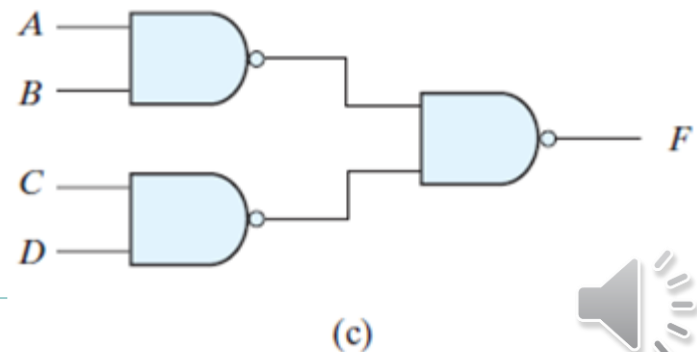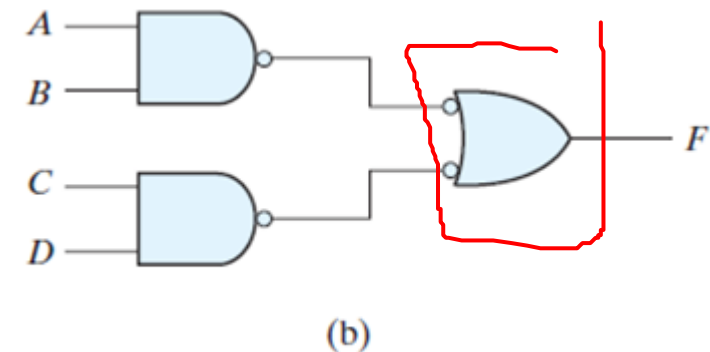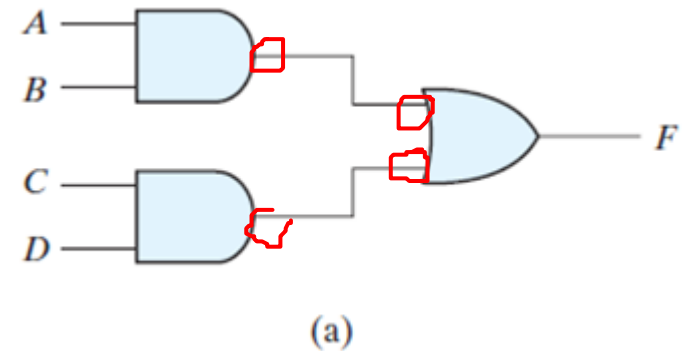



Two-level NAND-Only Implementation

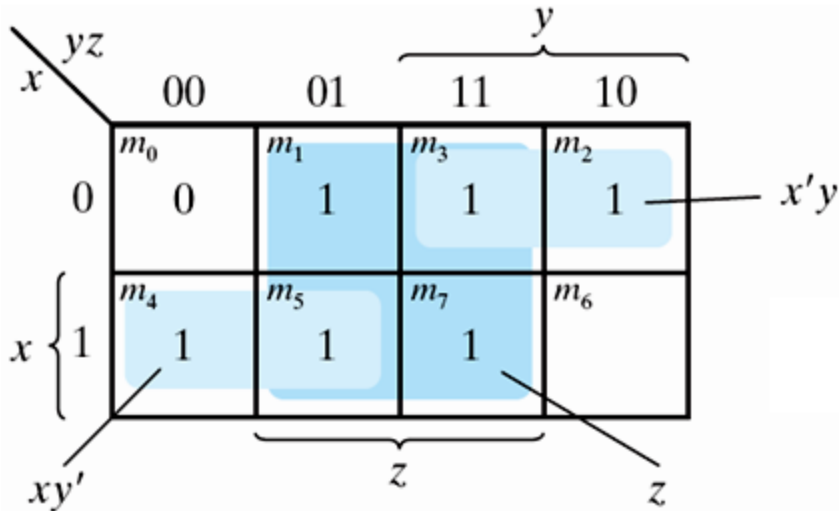- ▶ Example: implement $F(x, y, z) = \sum(1,2,3,4,5,7)$




(a)

$$F = xy' + x'y + z$$

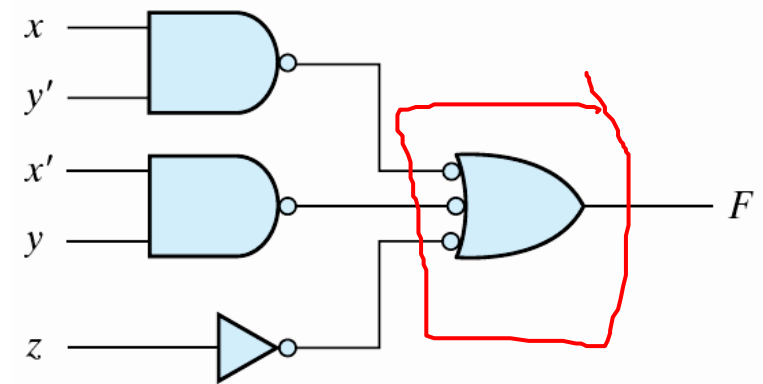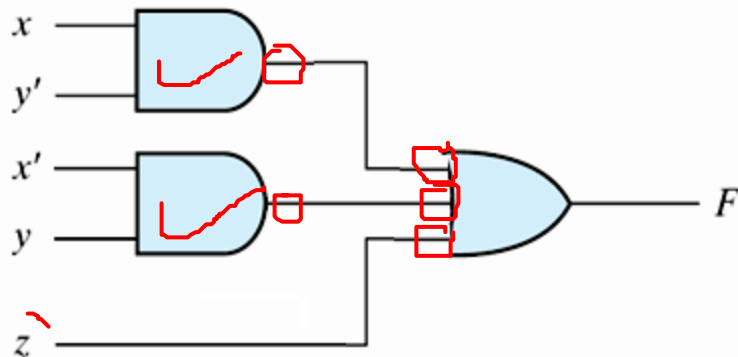

(b)

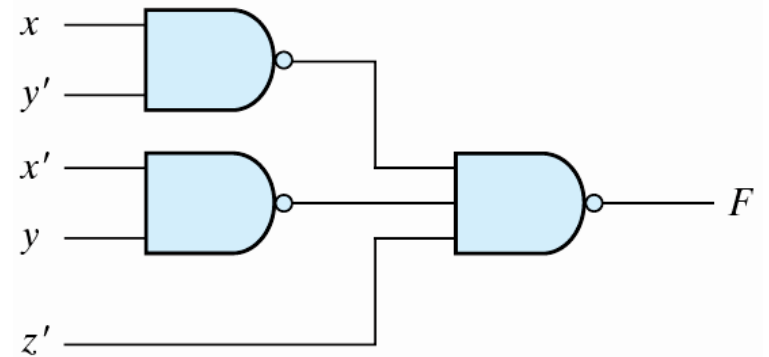

(c)



Two-level NAND-Only Implementation


▶ The procedure

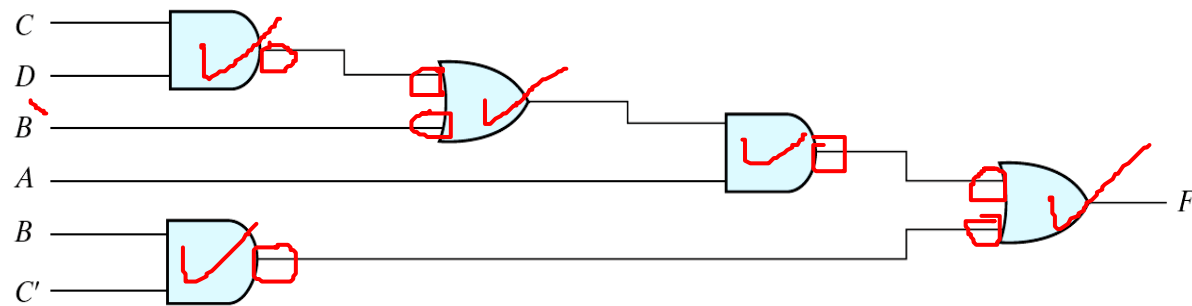1. Simplified in the form of **sum of products;**
2. A NAND gate for each product term; the inputs to each NAND gate are the literals of the term (the first level);
3. A single NAND gate for the second sum term (the second level);
4. A term with a single literal requires an inverter in the first level.




Multilevel NAND Circuits

- ▶ Boolean function implementation
 - ▶ AND-OR logic → NAND-NAND logic
 - ▶ AND → NAND + inverter
 - ▶ OR: inverter + OR = NAND



(a) AND-OR gates

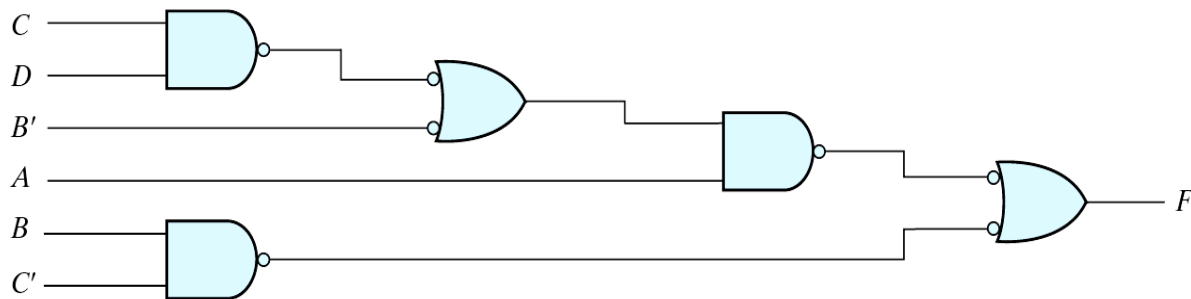


(b) NAND gates


Figure 3.22 Implementing $F = A(CD + B) + BC'$



NAND-Only Implementation

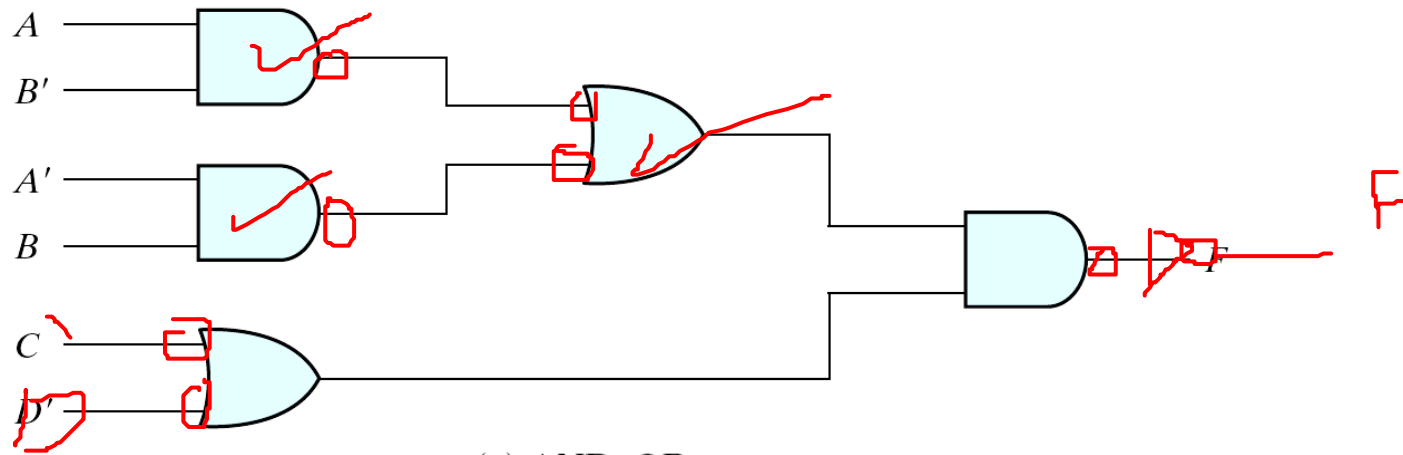

(a) AND-OR gates

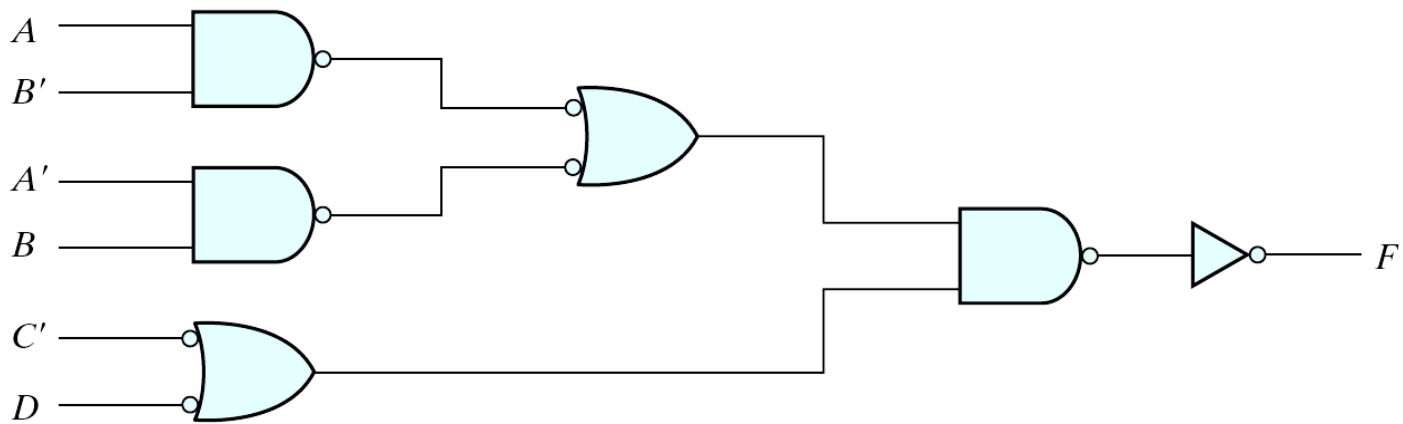

(b) NAND gates


Figure 3.23 Implementing $F = (AB' + A'B)(C + D')$



NOR-Only Implementation

- ▶ **NOR gate is a universal gate**
 - ▶ Can implement any digital system using NOR gate only

NOR

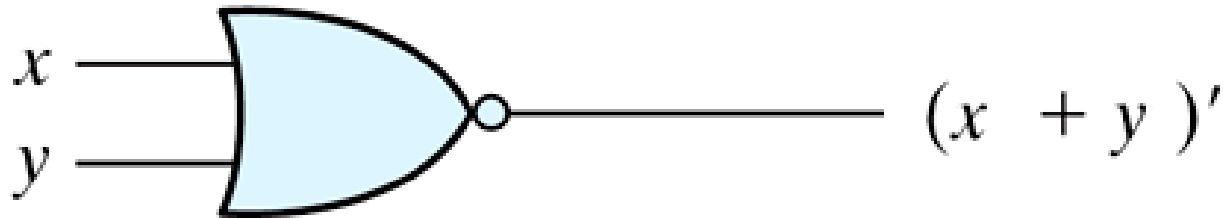


- ▶ **Universal gate** : we can implement all logic Operations with NOR Gates **ONLY**



NOR-Only Implementation

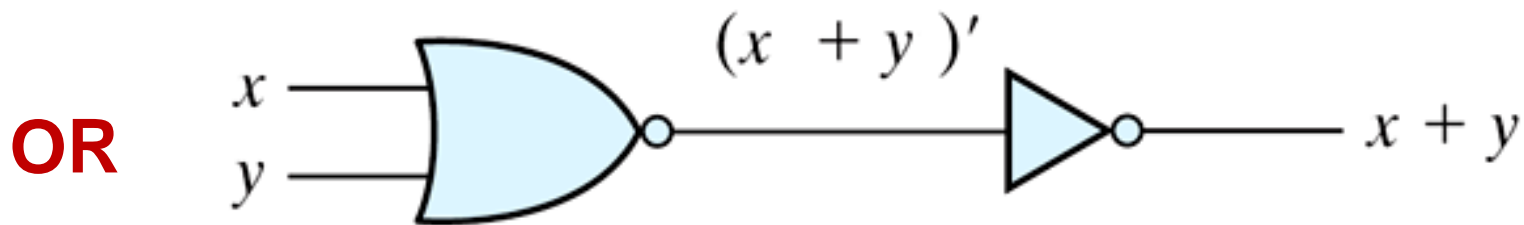- ▶ **NOR gate is a universal gate**
 - ▶ Can implement any digital system using NOR gate only




- ▶ **Universal gate** : we can implement all logic Operations with NOR Gates **ONLY**



NOR-Only Implementation

- ▶ **NOR gate is a universal gate**

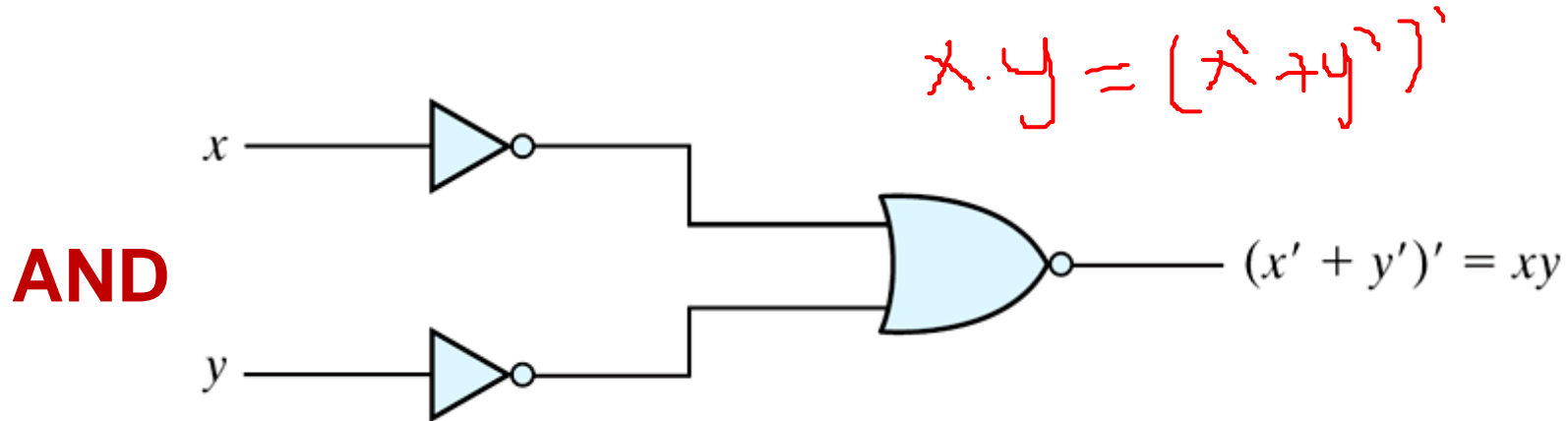- ▶ Can implement any digital system using NOR gate only




- ▶ **Universal gate** : we can implement all logic Operations with NOR Gates **ONLY**



NOR-Only Implementation

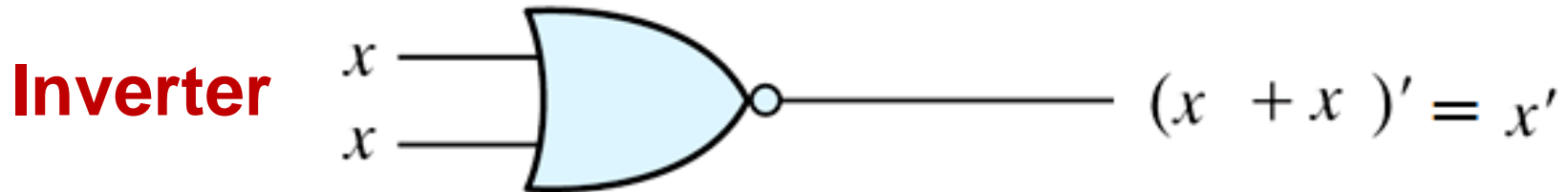- ▶ **NOR gate is a universal gate**
 - ▶ Can implement any digital system using NOR gate only




- ▶ **Universal gate** : we can implement all logic Operations with NOR Gates **ONLY**



NOR-Only Implementation

- ▶ **NOR gate is a universal gate**

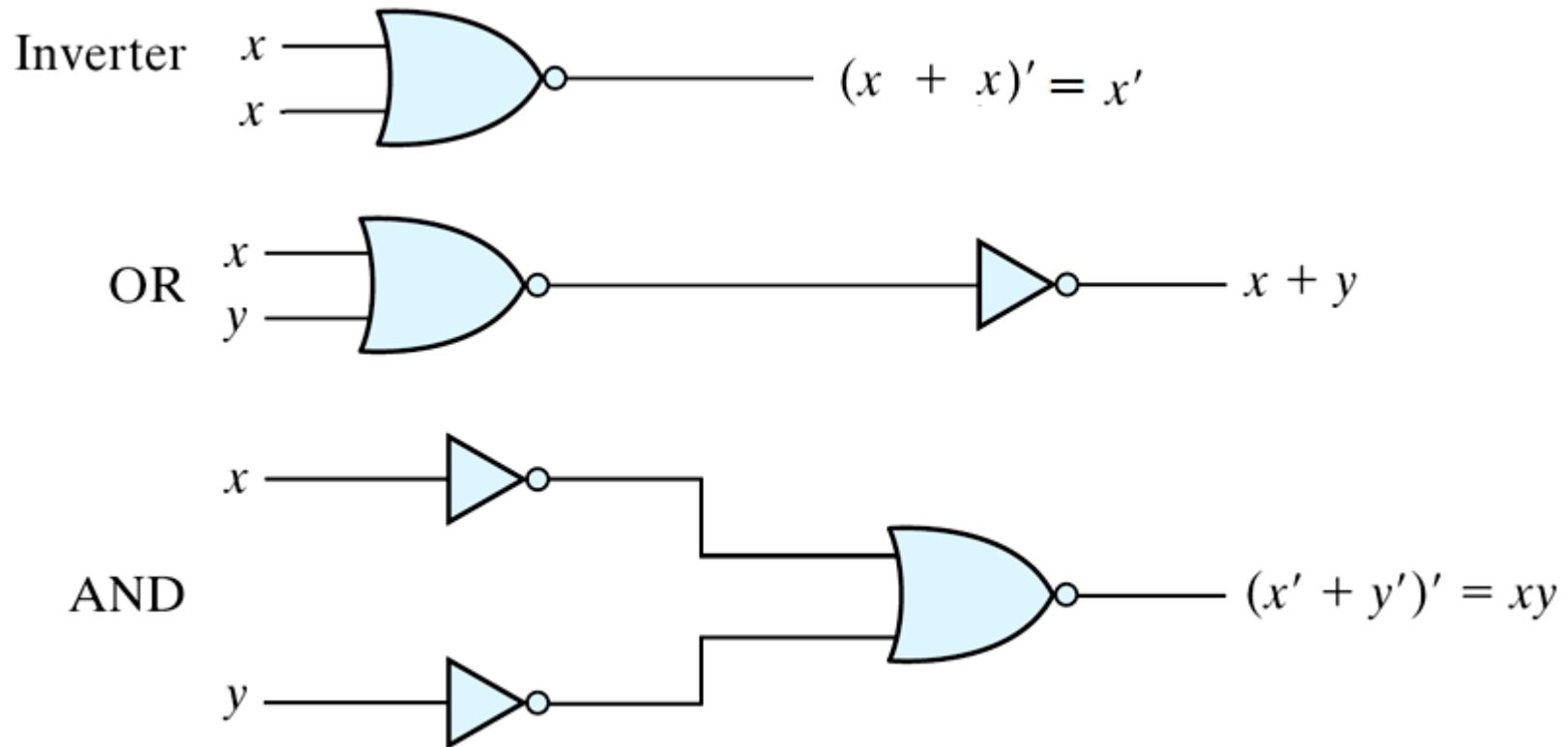


▶ Figure 3.24 Logic Operation with NOR Gates




NOR-Only Implementation

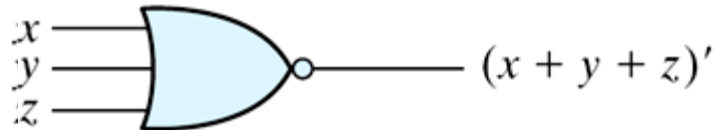- ▶ Two graphic symbols for a **NOR** gate



(a) OR-invert

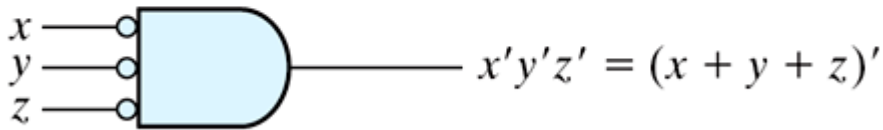

(b) Invert-AND

$$(x+y+z)' = x'y'z'$$

By applying
DeMorgan's Theorem



Figure 3.25 Two Graphic Symbols for NOR Gate



NOR-Only Implementation

- ▶ Two graphic symbols for a **NOR** gate

Example: $F = (A + B)(C + D)E$

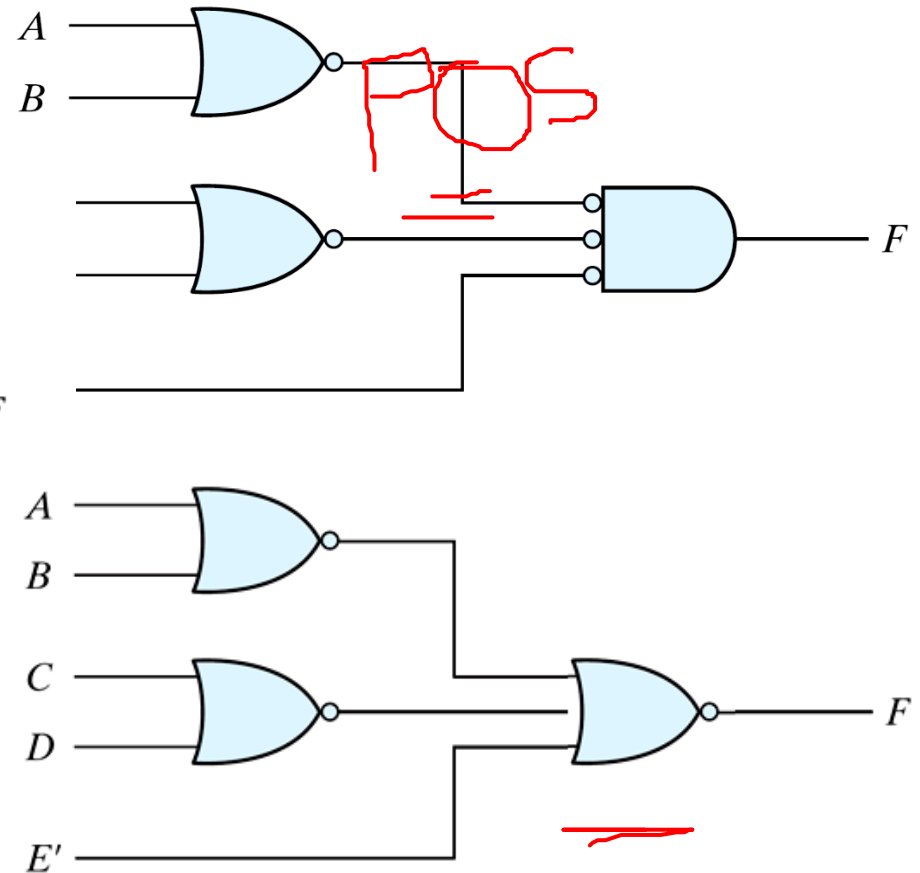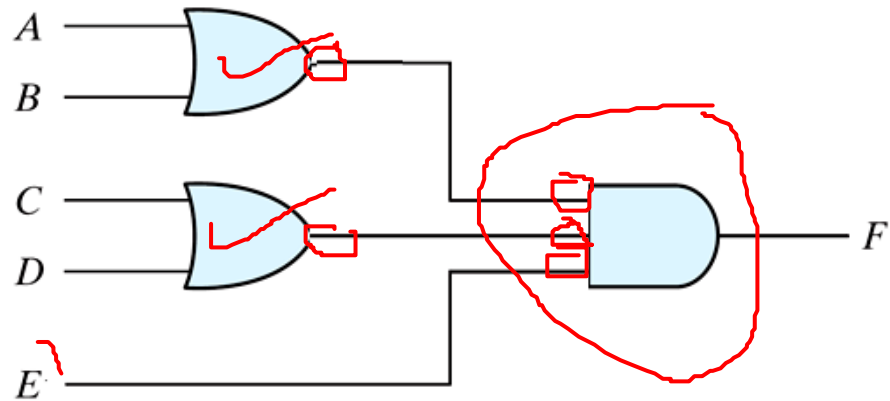

▶ Figure 3.26 Implementing $F = (A + B)(C + D)E$



NOR-Only Implementation

Example: $F = (AB' + A'B)(C + D)'$

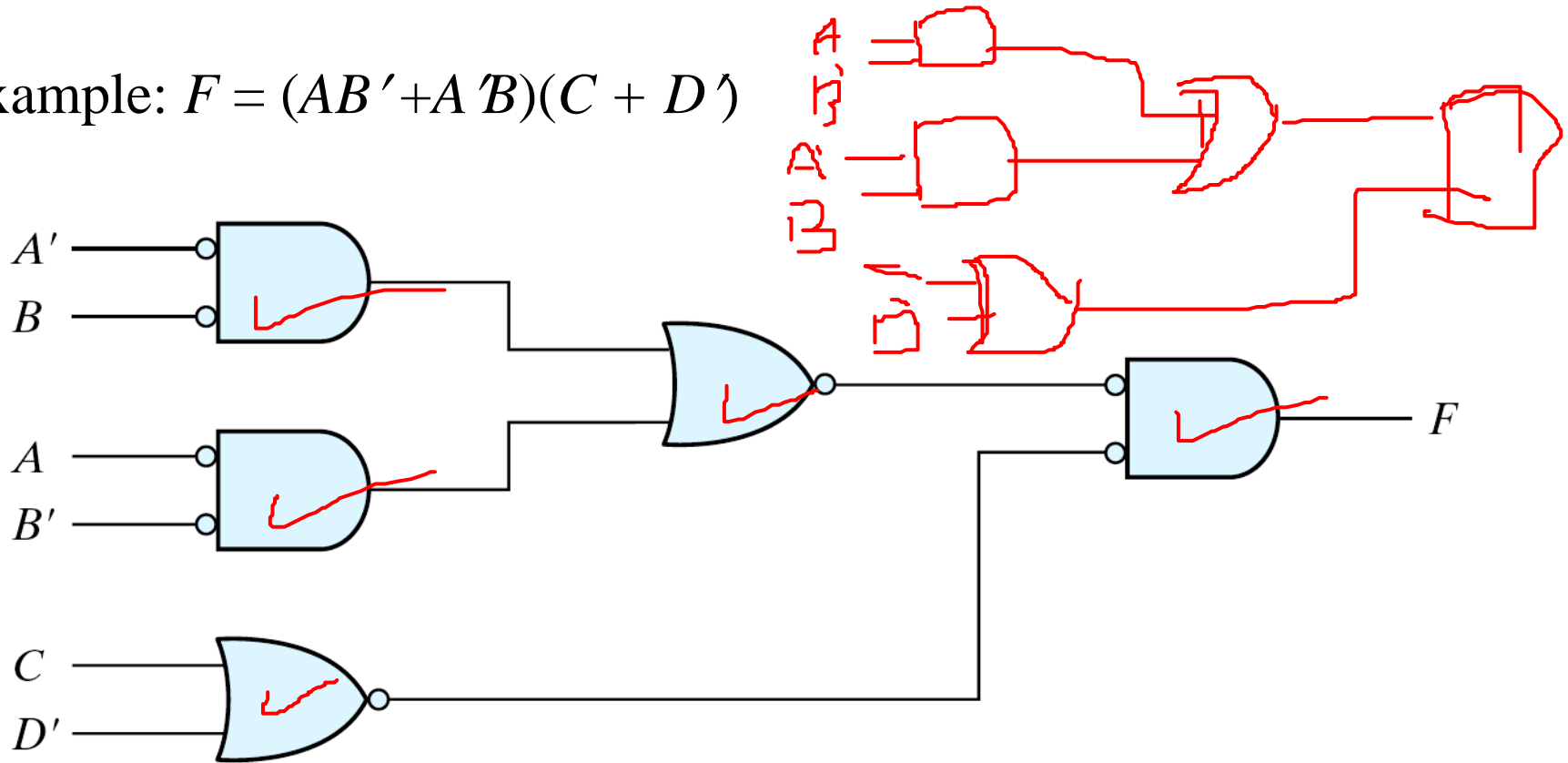


Figure 3.27 Implementing $F = (AB' + A'B)(C + D)'$ with NOR gates



Exclusive-OR Function


Exclusive-OR (XOR)	$x \oplus y = xy' + x'y$
Exclusive-NOR (XNOR)	$(x \oplus y)' = (x \odot y) = xy + x'y'$
Some identities	$x \oplus 0 = x$ $x \oplus 1 = x'$ $x \oplus x = 0$ $x \oplus x' = 1$ $x \oplus y' = (x \oplus y)'$ $x' \oplus y = (x \oplus y)'$
Commutative	$A \oplus B = B \oplus A$
Associative	$(A \oplus B) \oplus C = A \oplus (B \oplus C) = A \oplus B \oplus C$



Exclusive-OR Implementations


▶ Implementations

▶ $x \oplus y = xy' + x'y$

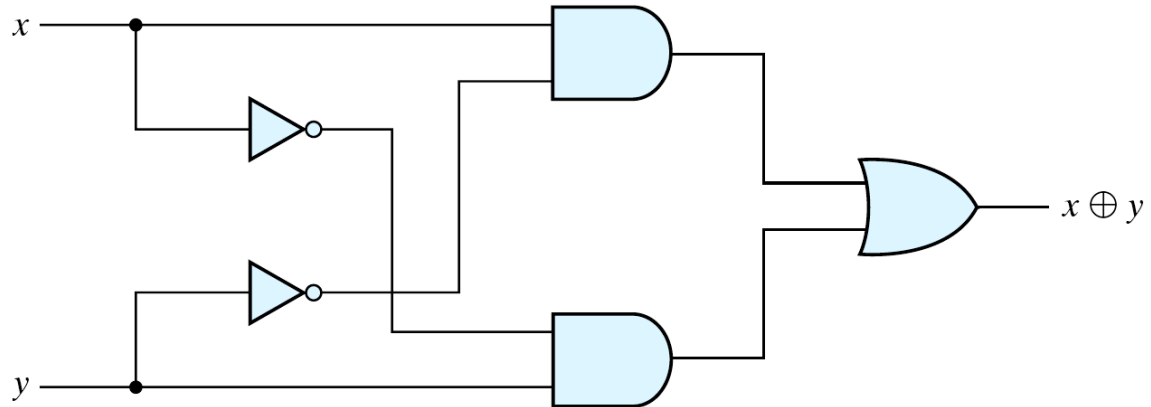

(a) With AND-OR-NOT gates

▶ $x \oplus y = (x' + y')x + (x' + y')y$

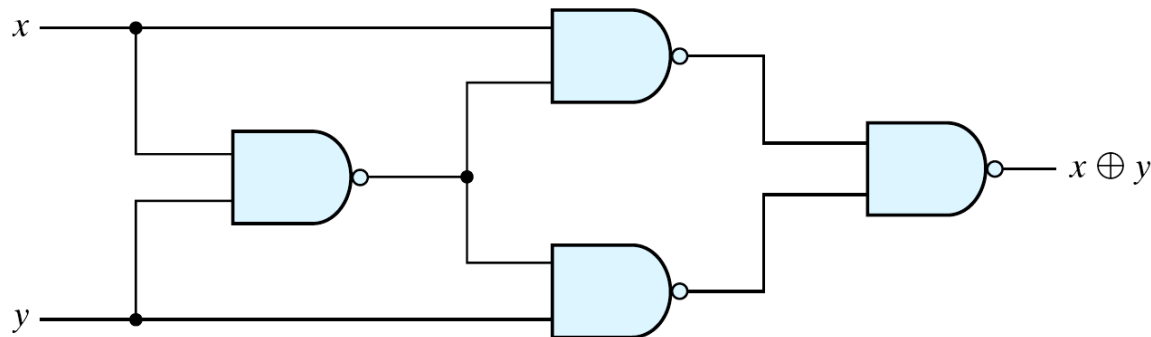


(b) With NAND gates




Odd Function

$$A \oplus B \oplus C = (AB' + A'B)C' + (AB + A'B')C$$
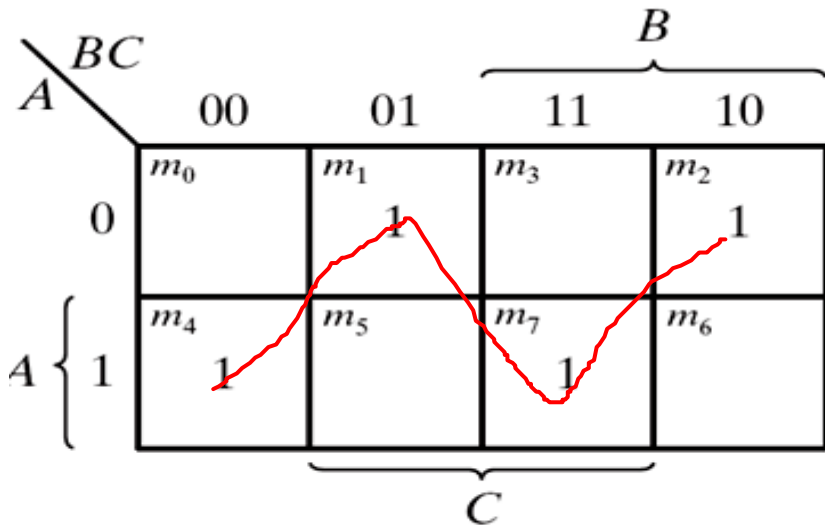
$$= AB'C' + A'BC' + ABC + A'B'C = \Sigma(1, 2, 4, 7)$$



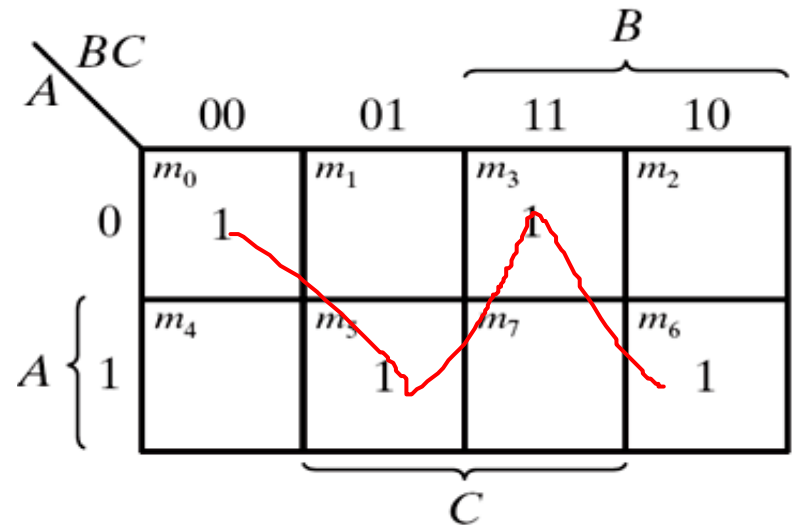(a) Odd function $F = A \oplus B \oplus C$



(b) Even function $F = (A \oplus B \oplus C)'$

XOR is a odd function

→ an odd number of 1's,
then $F = 1$.


XNOR is a even function

→ an even
number of 1's, then $F = 1$.




XOR and XNOR

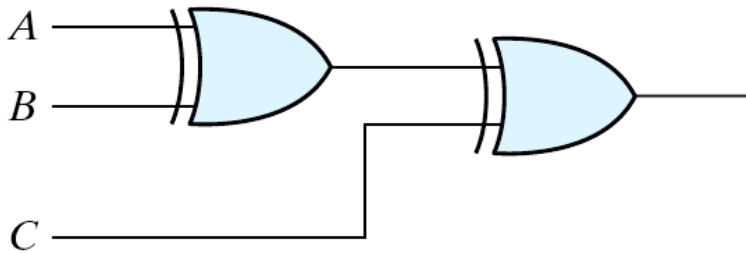- ▶ Logic diagram of odd and even functions



(a) 3-input odd function

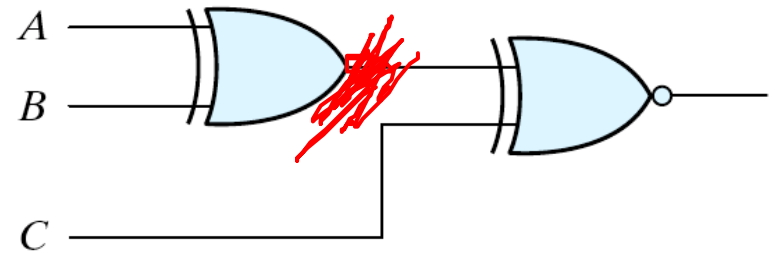

(b) 3-input even function


Logic Diagram of Odd and Even Functions




Four-variable Exclusive-OR function

▶ Four-variable Exclusive-OR function
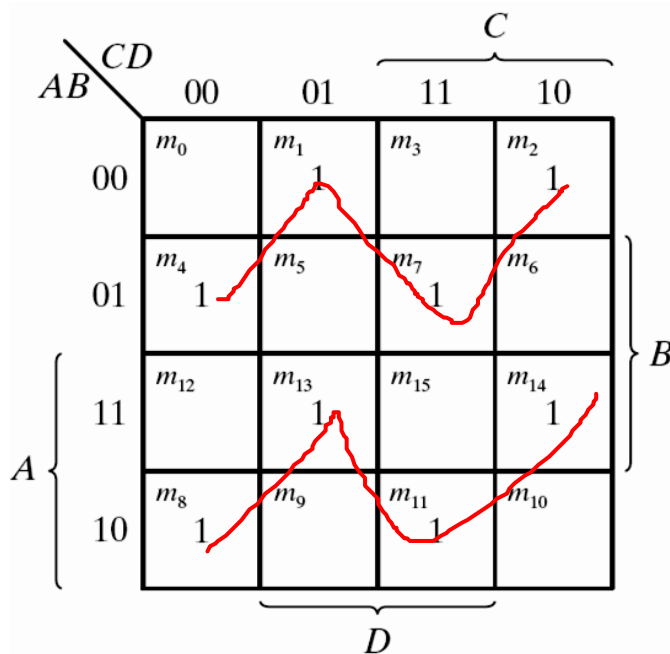
$$\begin{aligned} \blacktriangleright A \oplus B \oplus C \oplus D &= (AB' + A'B) \oplus (CD' + C'D) = \\ &= (AB' + A'B)(CD + C'D') + (AB + A'B')(CD' + C'D) \end{aligned}$$



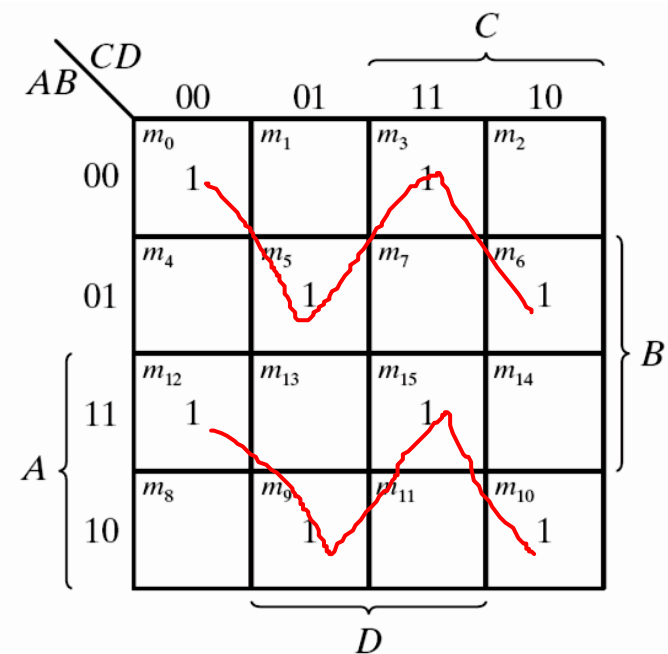(a) Odd function $F = A \oplus B \oplus C \oplus D$




(b) Even function $F = (A \oplus B \oplus C \oplus D)'$



Exclusive-OR Function Example

One Common Application of XOR is

Parity Generation and Checking

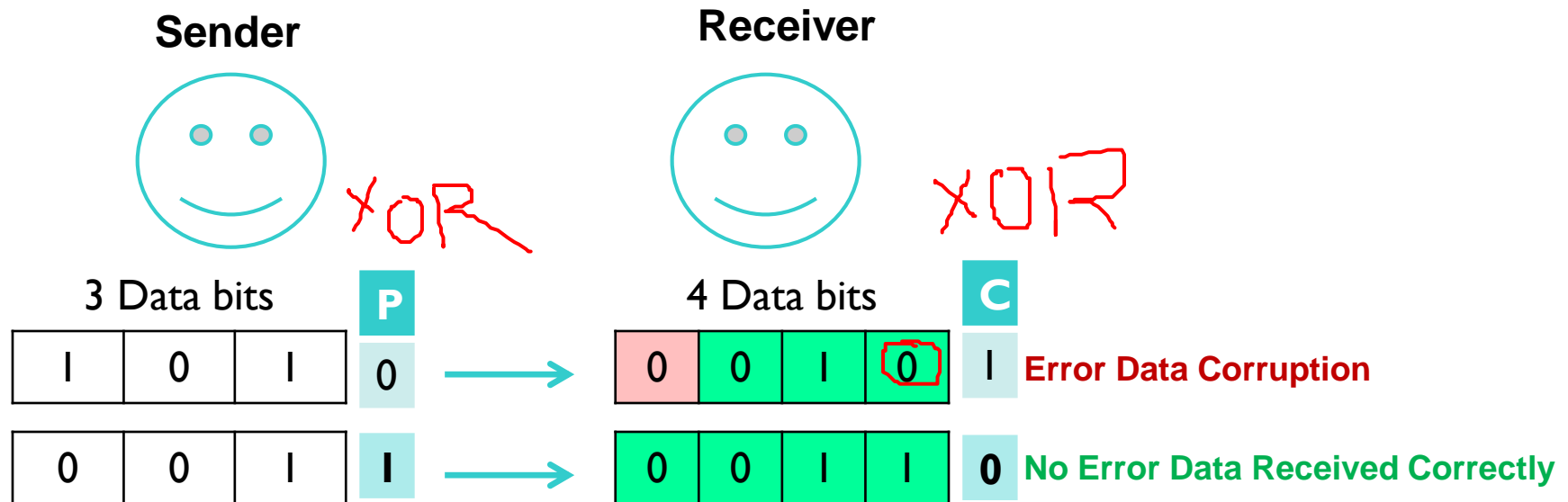

Even Parity Generator


Even Parity Checking



Exclusive-OR Function Example

One Common Application of XOR is

Parity Generation and Checking

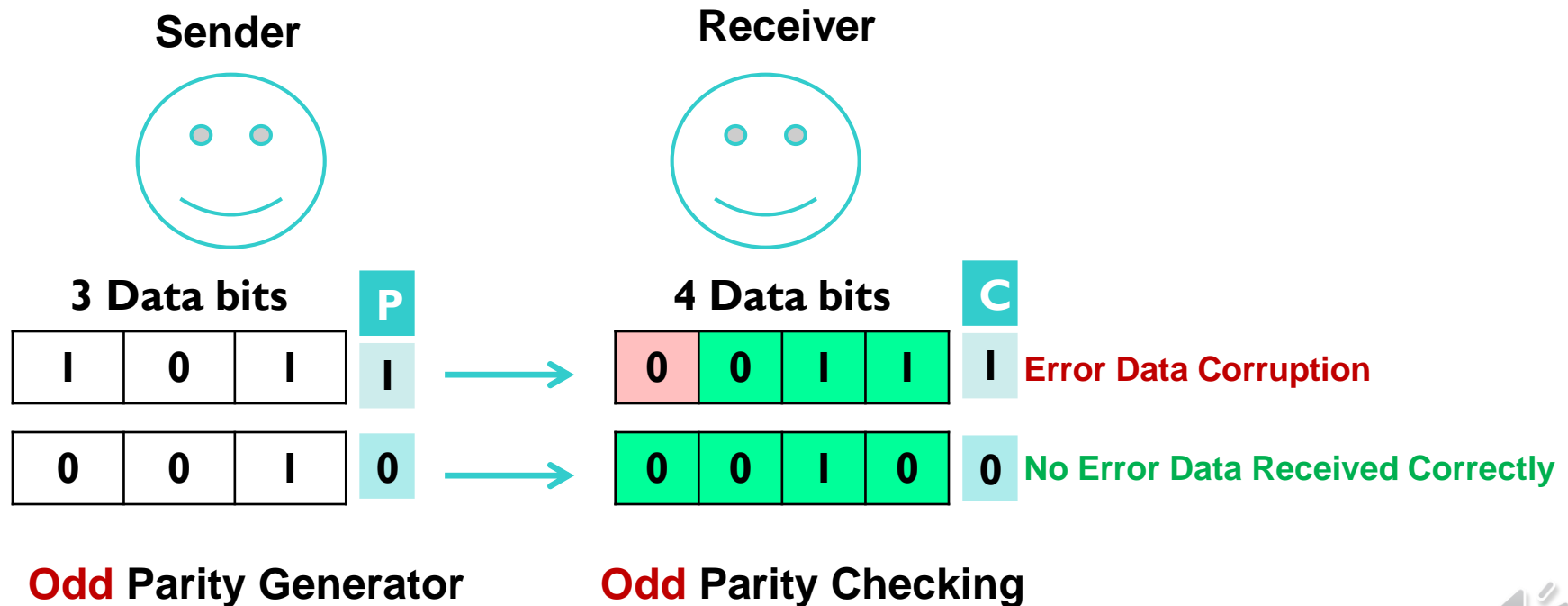

Even Parity Generation and Checking

▶ Parity Generation and Checking

▶ A parity bit: $P = x \oplus y \oplus z$

▶ Parity check: $C = x \oplus y \oplus z \oplus P$

▶ $C=1$: one bit error or an odd number of data bit error

▶ $C=0$: correct or an even # of data bit error

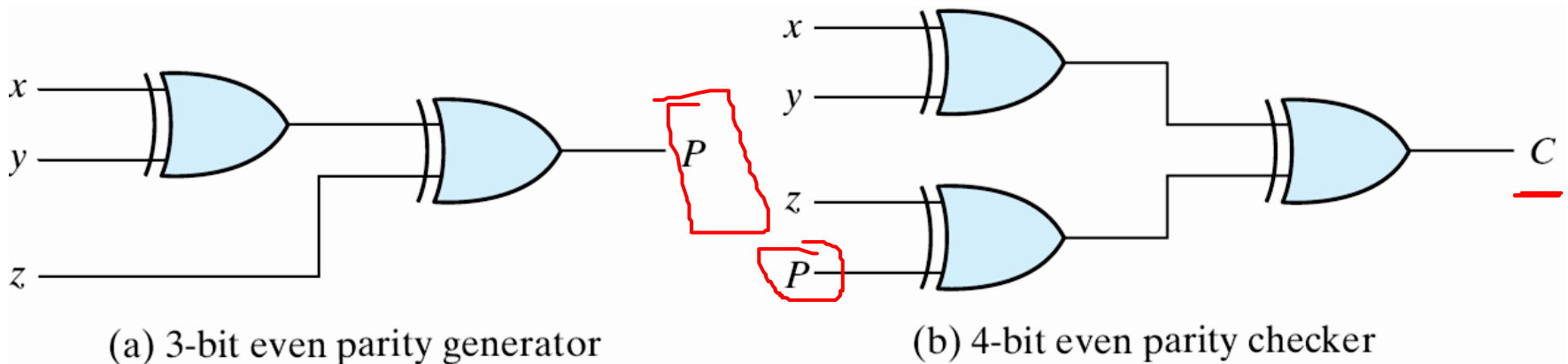


Figure 3.36 Logic Diagram of a Parity Generator and Checker



Parity Generation and Checking

Table 3.4

Even-Parity-Generator Truth Table

Three-Bit Message			Parity Bit
<i>x</i>	<i>y</i>	<i>z</i>	<i>P</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1



Parity Generation and Checking

Table 3.5
Even-Parity-Checker Truth Table

Four Bits Received				Parity Error Check
x	y	z	P	C
0	0	0	0	0
0	0	0	1	<u>1</u>
0	0	1	<u>0</u>	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0



Combinational Logic

- ▶ **Logic circuits** for digital systems may be **combinational** or **sequential**.
- ▶ A **combinational circuit** consists of input variables, logic gates, and output variables.

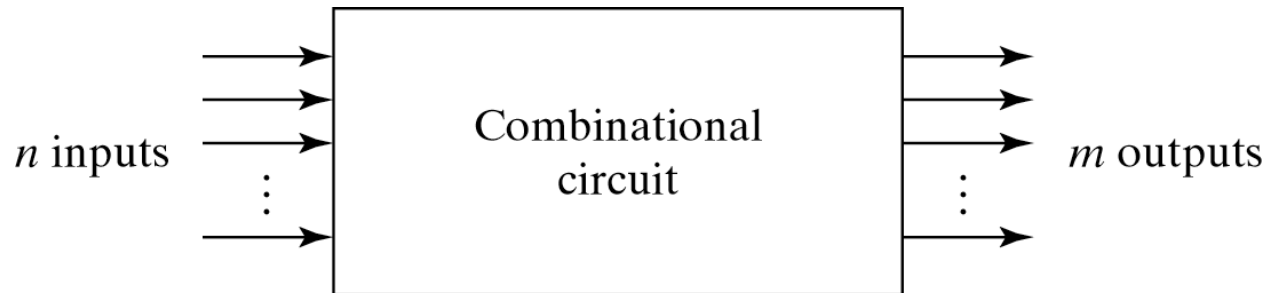


Fig. 4-1 Block Diagram of Combinational Circuit



Combinational Logic

- ▶ Combinational circuits:

- ▶ Consist of logic gates only
- ▶ Outputs are determined from the present values of inputs

- ▶ Sequential circuits:

- ▶ Consist of logic gates and storage elements
- ▶ Outputs are a function of the inputs and the state of the storage elements
 - ▶ Depend not only on present inputs, but also on past values



Combinational Logic

- ▶ A combinational circuit consists of:
 - ▶ Input variables
 - ▶ Logic gates
 - ▶ Output variables
- ▶ Transform binary information from the given input data to a required output data.

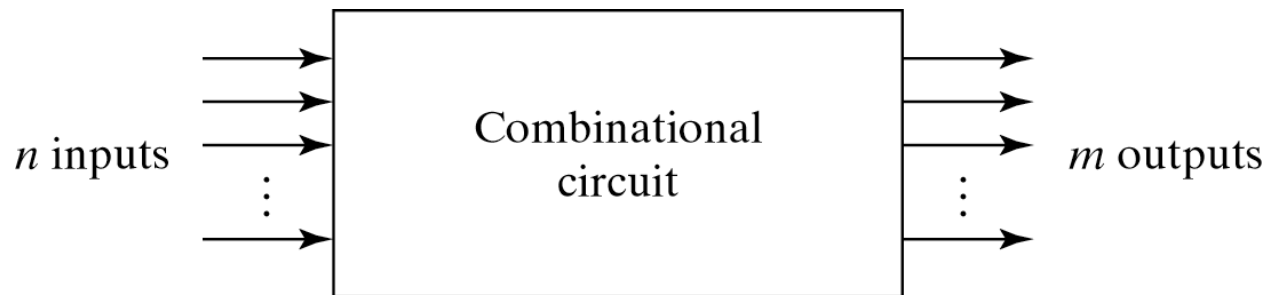


Fig. 4-1 Block Diagram of Combinational Circuit



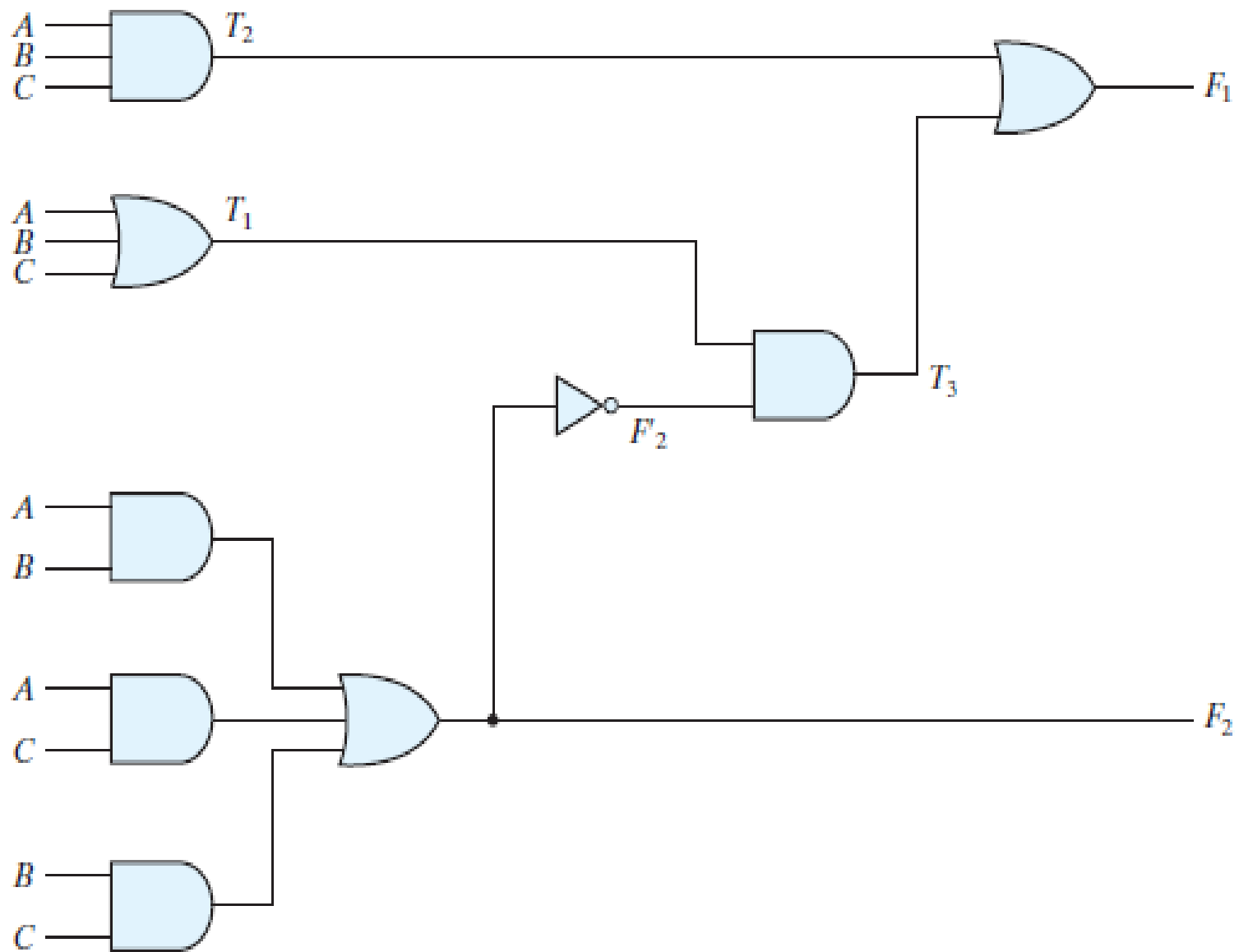


FIGURE 4.2

Logic diagram for analysis example



Combinational Logic

- ▶ There are 2^n possible binary input combinations for n input variable
- ▶ Only one possible output value for each possible input combination
 - ▶ Can be specified with a truth table, m Boolean functions, one for each output variable, Each output function is expressed in terms of n input variables

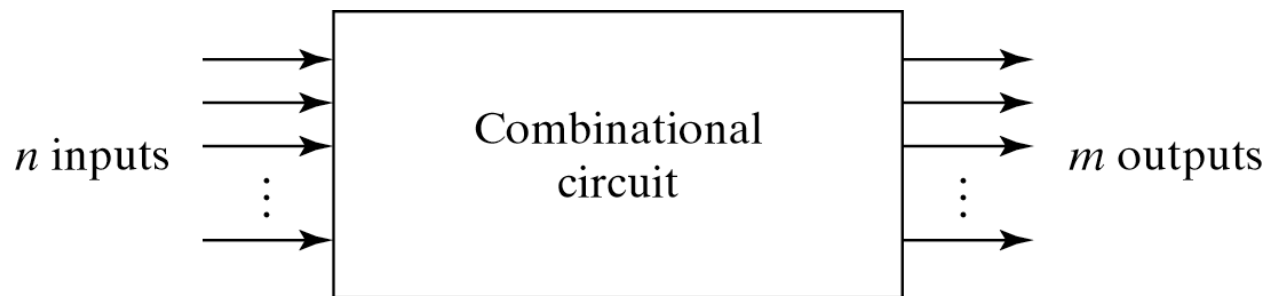


Fig. 4-1 Block Diagram of Combinational Circuit




Analysis Procedure

- ▶ **The “analysis” is the reverse of “design”.**
- ▶ Analysis: determine the function that the circuit implements
 - ▶ Often start with a given logic diagram
- ▶ **First step:** make sure that circuit is combinational and not sequential.
 - ▶ Without feedback paths or memory elements
- ▶ **Second step:** obtain the output Boolean functions or the truth table



Analysis Procedure

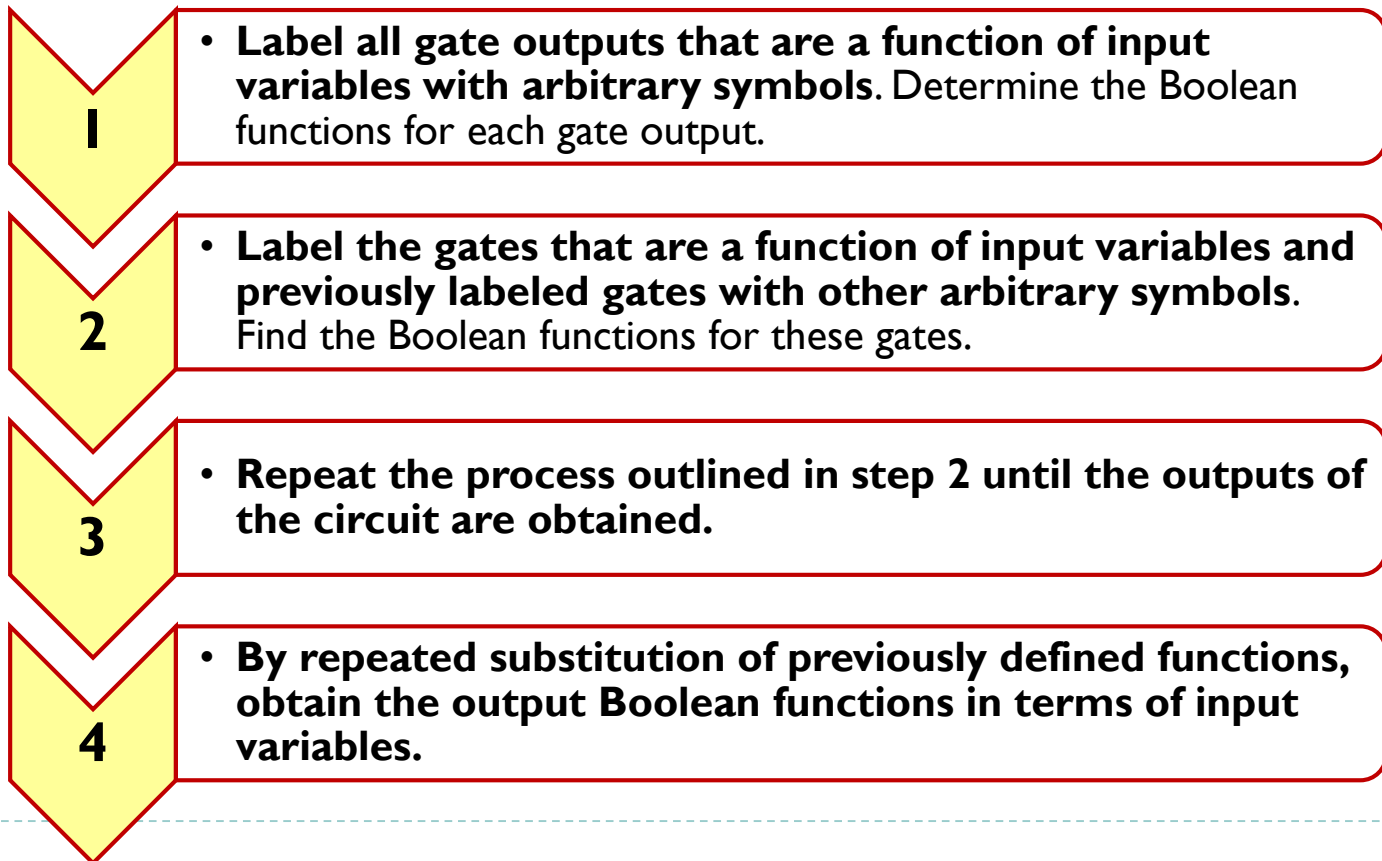- ▶ To obtain the output Boolean functions from a logic diagram, proceed as follows: (**do it backward**)



Analysis Procedure - Example

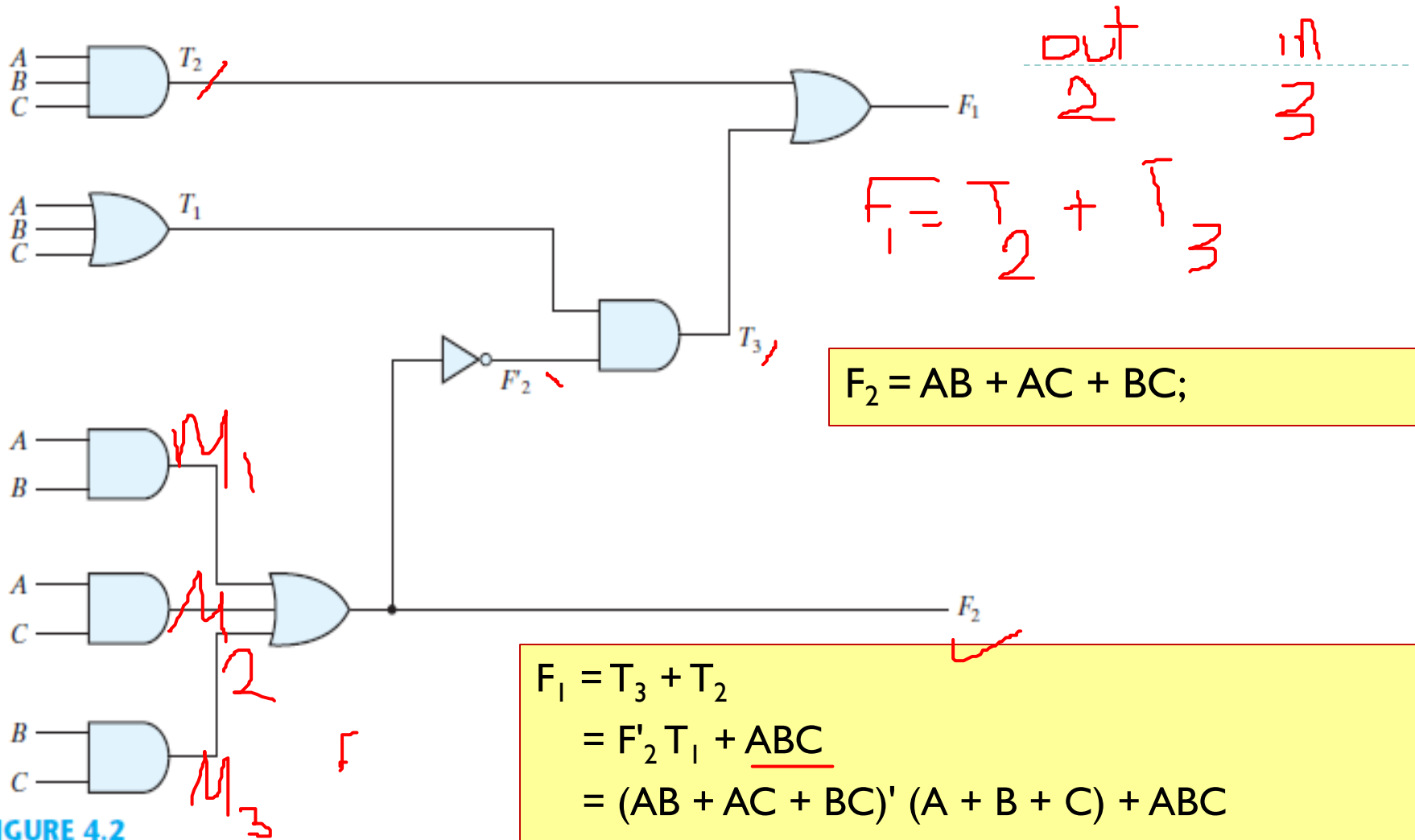


FIGURE 4.2
Logic diagram for analysis example

$$\begin{aligned}
 F_1 &= T_3 + T_2 \\
 &= F_2' T_1 + \underline{ABC} \\
 &= (AB + AC + BC)' (A + B + C) + ABC \\
 &= (A' + B')(A' + C')(B' + C')(A + B + C) + ABC \\
 &= (A' + B' C')(AB' + AC' + BC' + B' C) + ABC \\
 &= A' BC' + A' B' C + AB' C' + ABC
 \end{aligned}$$



Analysis procedure - Example

- ▶ **Truth Table:** We can derive the truth table by using the logic gate diagram

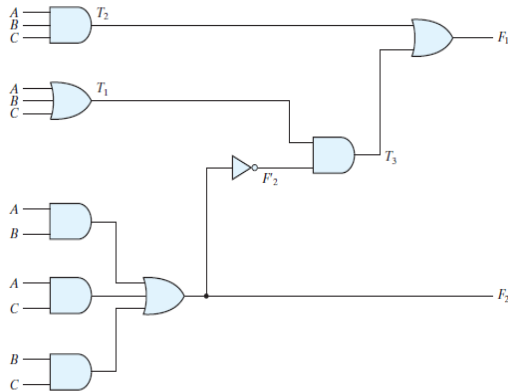


FIGURE 4.2
Logic diagram for analysis example

Table 4.1

Truth Table for the Logic Diagram of Fig. 4.2

A	B	C	F_2	F_2'	T_1	T_2	T_3	F_1
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1




Analysis procedure - Example

- ▶ **Truth Table:** We can derive the truth table by using the logic gate diagram
- ▶ To obtain the truth table from the logic diagram:
 1. Determine the number of input variables
 - ▶ For n inputs:
 - ▶ 2^n possible combinations
 - ▶ List the binary numbers from 0 to $2^n - 1$ in a table
 2. Label the outputs of selected gates
 3. Obtain the truth table for the outputs of those gates that are a function of the input variables only
 4. Obtain the truth table for those gates that are a function of previously defined variables at step 3
 - ▶ Repeatedly until all outputs are determined



Design Procedure

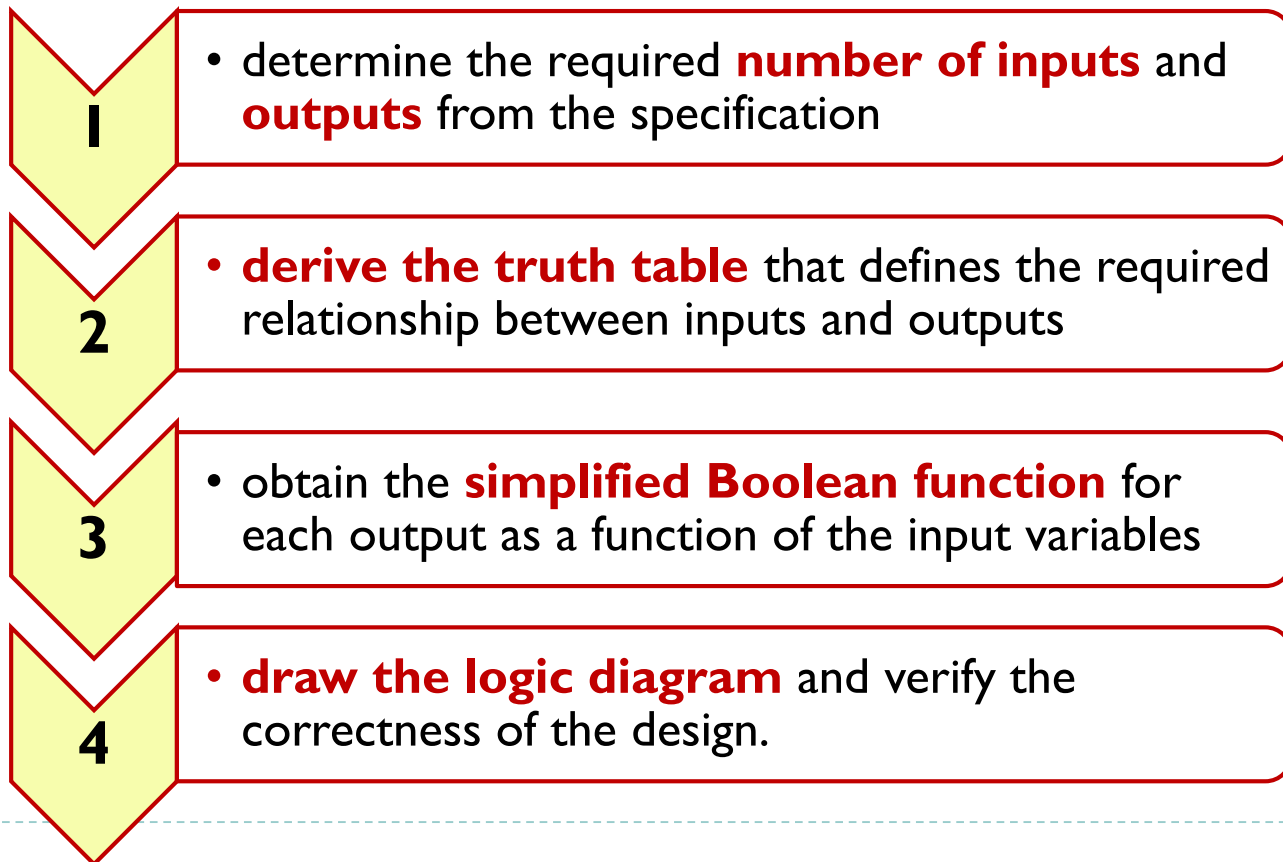- ▶ **Input:** the specification of the problem.
- ▶ **Output:** the logic circuit diagram or Boolean functions.



Code Conversion Design Problems

- ▶ It is sometimes necessary to use the output of one system as the input to another.
 - ▶ A conversion circuit must be inserted between the two system if each uses different codes for the same information.
 - ▶ Thus, a code converter is a circuit that makes the two systems compatible even though each uses a different binary code.
 - ▶ To convert from binary code A to binary code B, the input lines must supply the bit combination of elements as specified by code A and the output lines must generate the corresponding bit combination of code B.



Code Conversion Example

▶ BCD to Excess-3 Code Converter

2

1


- ▶ Input BCD
- ▶ 4 – Variables Input
- ▶ Output Excess-3
- ▶ 4 – Variables output

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0



Code Converter

▶ BCD to Excess-3 Code Converter

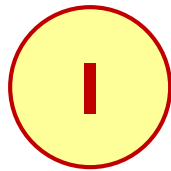

- ▶ Input BCD
- ▶ 4 – Variables Input
- ▶ Output Excess-3
- ▶ 4 – Variables output

Input BCD- Code				Output Excess -3 Code			
A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x



Code Conversion Example

3

- ▶ **Boolean Expression :**
- ▶ The six don't care minterms (10~15) are marked with X.
- ▶ Each of four maps represents one of the four outputs of this circuit as a function of the four input variables.

		CD		C	
		00	01	11	10
A	00		1	1	1
	01	1			
	11	X	X	X	X
	10		1	X	X

D

$$X = B'C + B'D + BC'D'$$

		CD		C	
		00	01	11	10
A	00				
	01		1	1	1
	11	X	X	X	X
	10	1	1	X	X

D

$$w = A + BC + BD$$



Code Conversion Example

▶ Boolean Expression : **3**

		<i>CD</i>		<i>C</i>	
		00	01	11	10
<i>A</i>	00	1			1
	01	1			1
	11	X	X	X	X
	10	1		X	X

$z = D'$

		<i>CD</i>		<i>C</i>	
		00	01	11	10
<i>A</i>	00	1		1	
	01	1		1	
	11	X	X	X	X
	10	1		X	X

$y = CD + C'D'$



Code Conversion Example

- ▶ **Logic Diagram:** Reduce the number of gates used.

4

$$z = D'$$

$$\begin{aligned}x &= B'C + B'D + BC'D' \\ &= B'(C + D) + BC'D' \\ &= B'(C + D) + B(C + D)'\end{aligned}$$

$$\begin{aligned}y &= CD + C'D' \\ &= CD + (C + D)'\end{aligned}$$


$$\begin{aligned}w &= A + BC + BD \\ &= A + B(C + D)\end{aligned}$$

- ▶ C + D is used to implement the three outputs.



Code Conversion Example

4

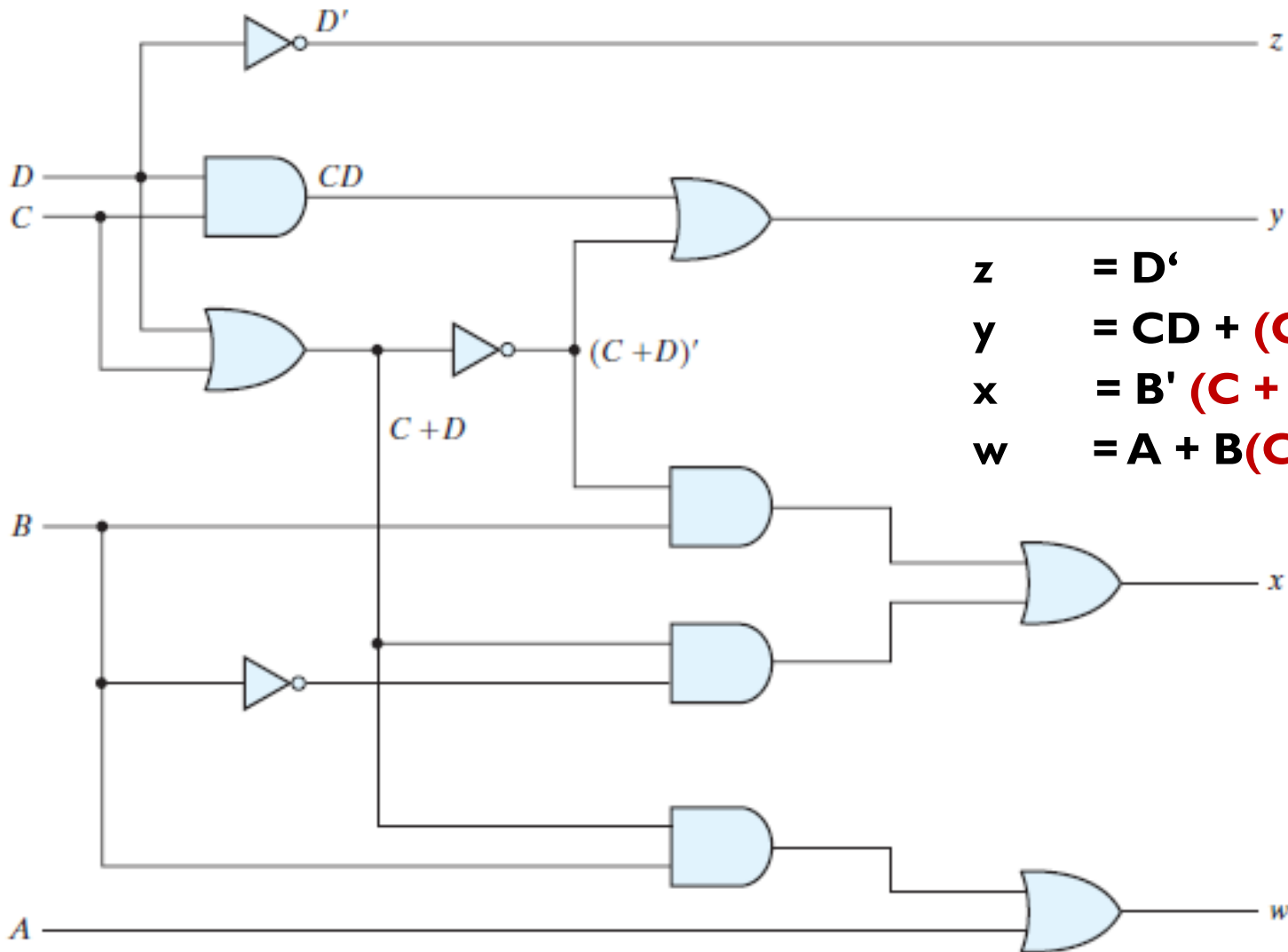

$$\begin{aligned} z &= D' \\ y &= CD + (C + D)' \\ x &= B' (C + D) + B(C + D)' \\ w &= A + B(C + D) \end{aligned}$$



Thank You!

