


Digital Design

Lecture of week 8

Dr Manal Tantawi

Chapter 5

Sequential Circuits

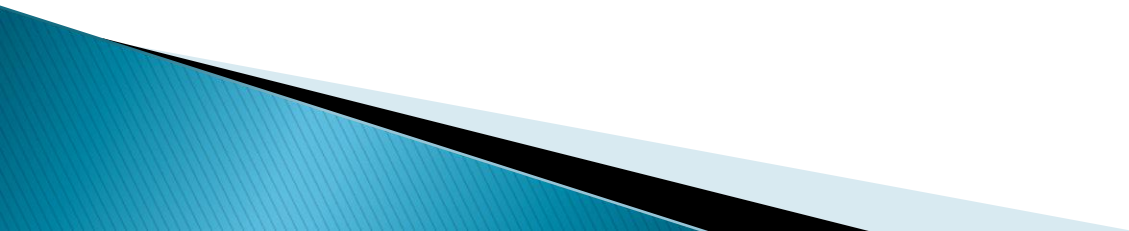


Synchronous Sequential Circuits

Combinational circuits Vs Sequential Circuits

Combinational Circuits

❖ Gates

❖ No feedback

 


❖ Time independent

Sequential Circuits


❖ Gates + memory units

❖ Feedback

 

❖ Time dependent
(Clock)

Clock

 

Level Trigger



(a) Response to positive level

Positive Edge Trigger



(b) Positive-edge response


Negative Edge Trigger



(c) Negative-edge response

Flip flops

Clock continued..

 


$$T = 1 / \text{Frequency (F)}$$

For example $T = 0.5 \text{ sec}$ $F = 2 \text{ HZ}$
 $T = 0.25 \text{ sec}$ $F = 4 \text{ HZ}$

Latches & Flip Flops

▶ RS Flipflop

R	S	Q _n	Q _{n+1}
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	undeterm
1	1	1	

 


Characteristic table

R	S	Q _{n+1}
0	0	No change Q _n
0	1	set 1
1	0	reset 0
1	1	Indeterminate

Latches & Flip Flops

▶ RS Latch

R	S	Q _n	Q _{n+1}
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	undeterm
1	1	1	

 


Characteristic table

CLK	R	S	Q _{n+1}
0	X	X	No change
1	0	0	No change
1	0	1	set
1	1	0	reset
1	1	1	Indeterminate

Latches & Flip Flops

▶ RS Flip Flop

R	S	Q _n	Q _{n+1}
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	undeterm
1	1	1	

 


Characteristic table

R	S	Q _{n+1}
0	0	No change Q _n
0	1	set 1
1	0	reset 0
1	1	Indeterminate


Flip flops

► D Flip Flop

D	Q _n	Q _{n+1}
0	0	0
0	1	0
1	0	1
1	1	1

 

Characteristic table

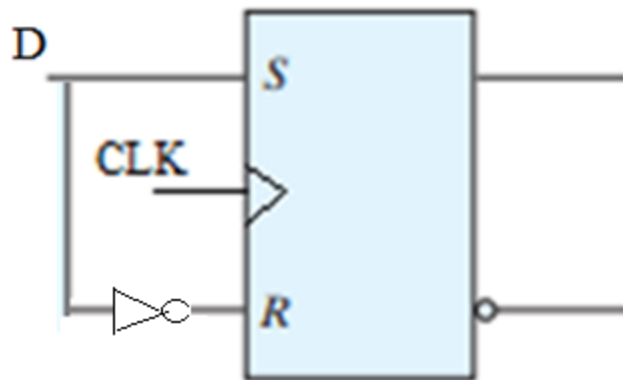


D Flip-Flop

D	Q_(n + 1)	
0	0	Reset
1	1	Set

Flip Flops

▶ JK Flip Flop

J	K	Q _n	Q _{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

 



Characteristic table

JK Flip-Flop			
J	K	Q(n + 1)	
0	0	Q(n)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(n)	Complement

Flip flops

▶ T Flip Flop

T	Q _n	Q _{n+1}
0	0	0
0	1	1
1	0	1
1	1	0

 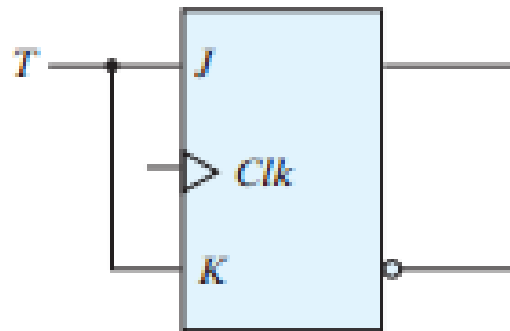


Characteristic table


T Flip-Flop

T	Q(n + 1)	
0	Q(n)	No change
1	Q'(n)	Complement

Synchronous Sequential Circuits

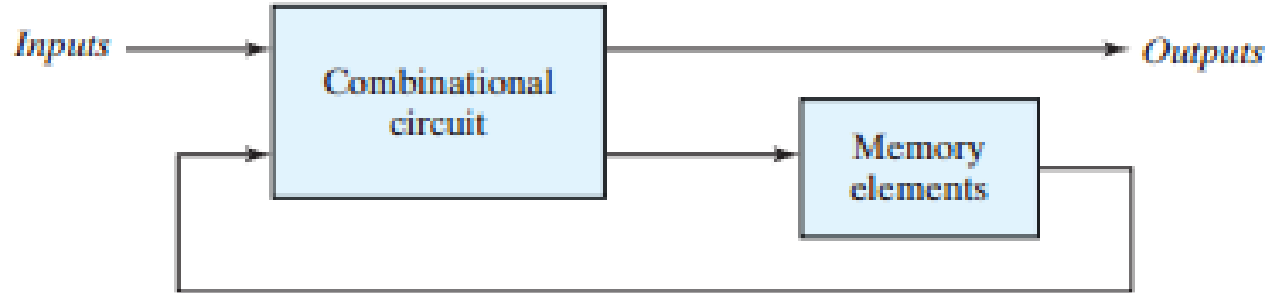


Synchronous Sequential Circuits

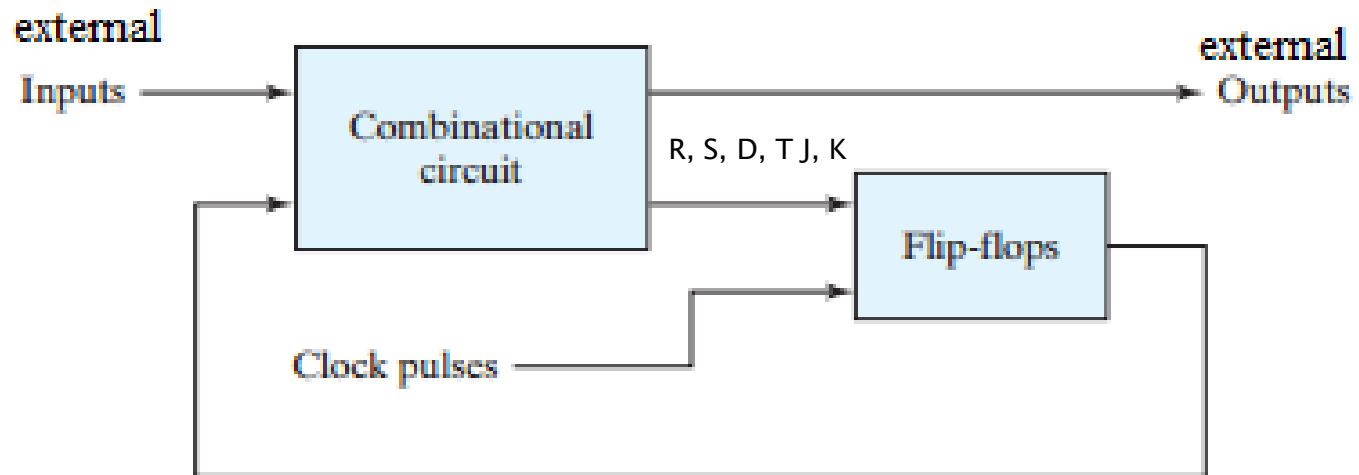


Synchronous Sequential Circuits

Design Procedure

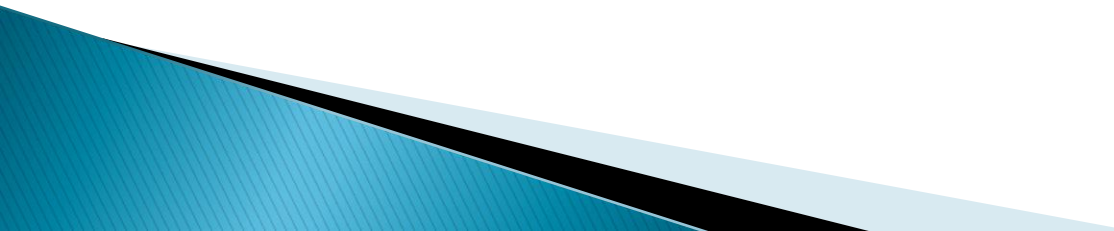 - 1) State Diagram
 - 2) Number of ex. Inputs and outputs and number of flipflops
 - 3) State Table
 - 4) Simplified expressions using Kmap for external outputs and inputs of flipflops
 - 5) Logic diagram
- 


Synchronous Sequential Circuits

Design a sequential circuit that follows the following state diagram using D flip flops



2) Two flip flops , one ex. Input & one ex. output

3) state table

 


Present outputs


next outputs

A_n	B_n	X	A_{n+1}	B_{n+1}	D_A	D_B	Y
0	0	0	0	0			0
0	0	1	0	1			0
0	1	0	0	0			0
0	1	1	1	0			0
1	0	0	0	0			0
1	0	1	1	1			0
1	1	0	0	0			1
1	1	1	1	1			1

 
4) Kmaps for ex. Output and flip flops inputs



$$D_A = Ax + Bx$$

 


$$D_B = Ax + B'x$$

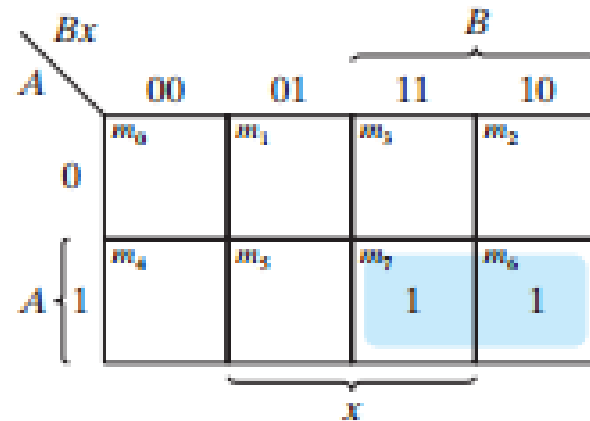


$$y = AB$$

► Logic diagram

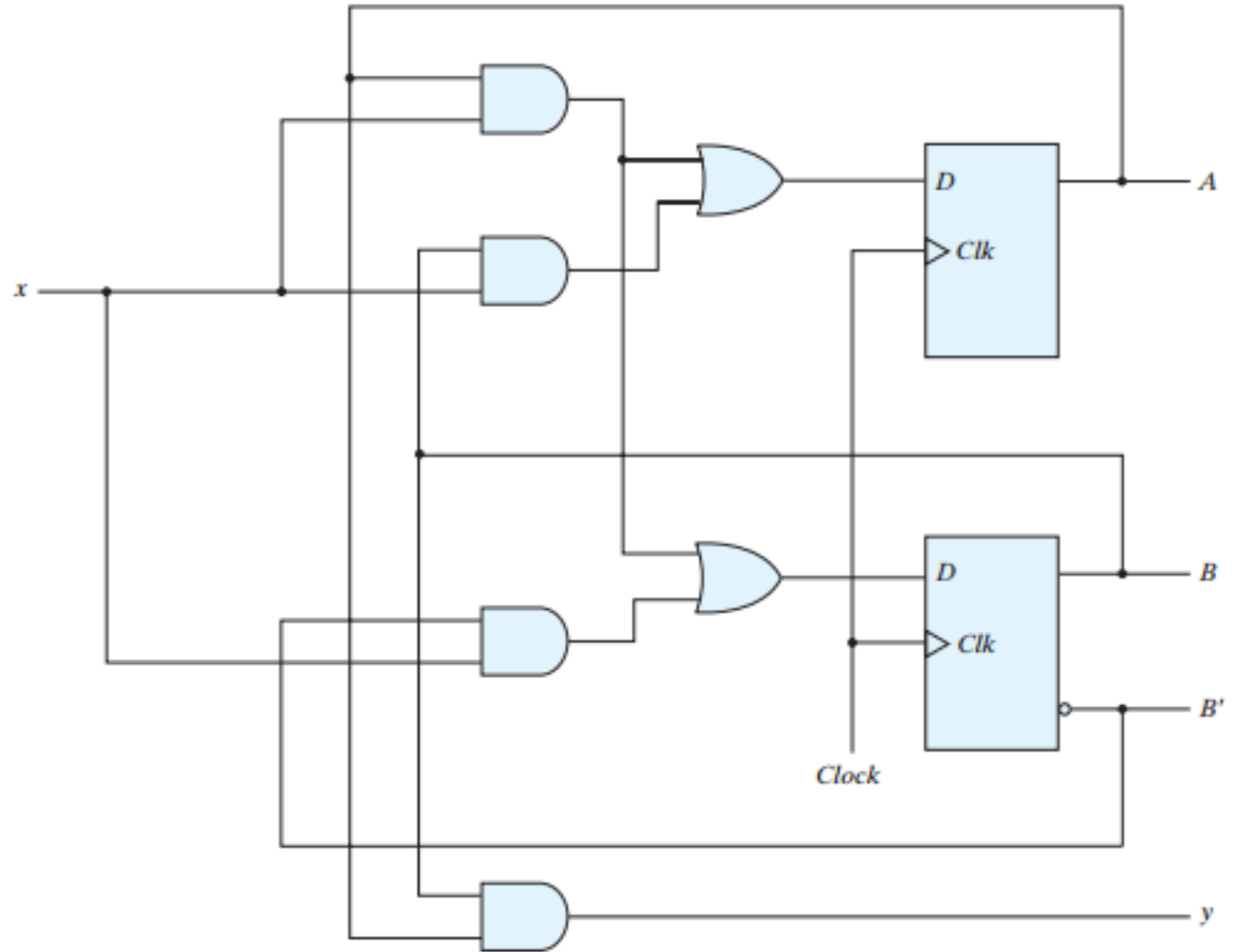

 
Design a sequential circuit that follows the following state diagram using T flip flops



2) 3 flip flops , no ex. Input & no ex. output

T Flip-Flop


T	$Q(n + 1)$
0	$Q(n)$ No change
1	$Q'(n)$ Complement

 

A_{2n}	A_{1n}	A_{0n}	A_{2n+1}	A_{1n+1}	A_{0n+1}	T_{a2}	T_{a1}	T_{a0}
0	0	0	0	0	1	0		
0	0	1	0	1	0	0		
0	1	0	0	1	1	0		
0	1	1	1	0	0	1		
1	0	0	1	0	1	0		
1	0	1	1	1	0	0		
1	1	0	1	1	1	0		
1	1	1	0	0	0	1		

T Flip-Flop


T	$Q(n+1)$	
0	$Q(n)$	No change
1	$Q'(n)$	Complement

 

A_{2n}	A_{1n}	A_{0n}	A_{2n+1}	A_{1n+1}	A_{0n+1}	T_{a2}	T_{a1}	T_{a0}
0	0	0	0	0	1	0	0	
0	0	1	0	1	0	0	1	
0	1	0	0	1	1	0	0	
0	1	1	1	0	0	1	1	
1	0	0	1	0	1	0	0	
1	0	1	1	1	0	0	1	
1	1	0	1	1	1	0	0	
1	1	1	0	0	0	1	1	

T Flip-Flop

T	$Q(n + 1)$
0	$Q(n)$ No change
1	$Q'(n)$ Complement

 

A_{2n}	A_{1n}	A_{0n}	A_{2n+1}	A_{1n+1}	A_{0n+1}	T_{a2}	T_{a1}	T_{a0}
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

4) Kmaps for flip flops inputs

		A_1A_0			
		00	01	A_1 11 10	
A_2	0	m_0	m_1	m_3 1	m_2
	1	m_4	m_5	m_7 1	m_6
		A_0			

$$T_{A_2} = A_1A_0$$


		A_1A_0			
		00	01	A_1 11 10	
A_2	0	m_0	m_1 1	m_3 1	m_2
	1	m_4	m_5 1	m_7 1	m_6
		A_0			

$$T_{A_1} = A_0$$

		A_1A_0			
		00	01	A_1 11 10	
A_2	0	m_0 1	m_1 1	m_3 1	m_2 1
	1	m_4 1	m_5 1	m_7 1	m_6 1
		x			

$$T_{A_0} = 1$$

► Logic diagram

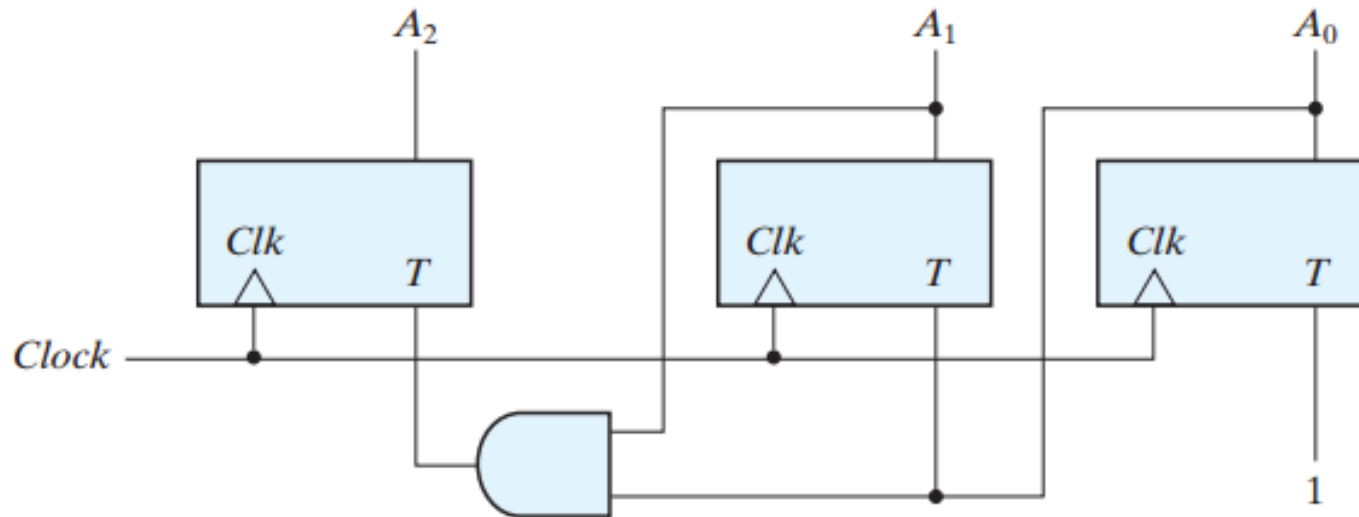

**Next Lecture we will continue
chapter 5 thank you**

