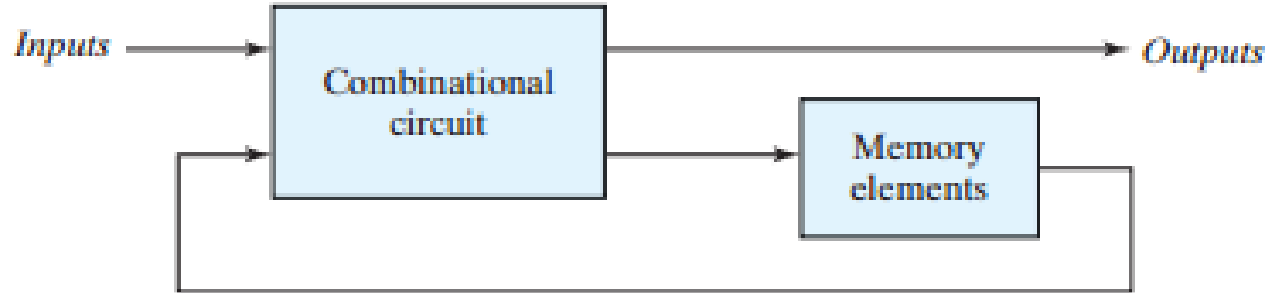


Digital Design


Lecture of week 10

Dr Manal Tantawi

Recap: Synchronous Sequential Circuits




Recap: Synchronous Sequential Circuits

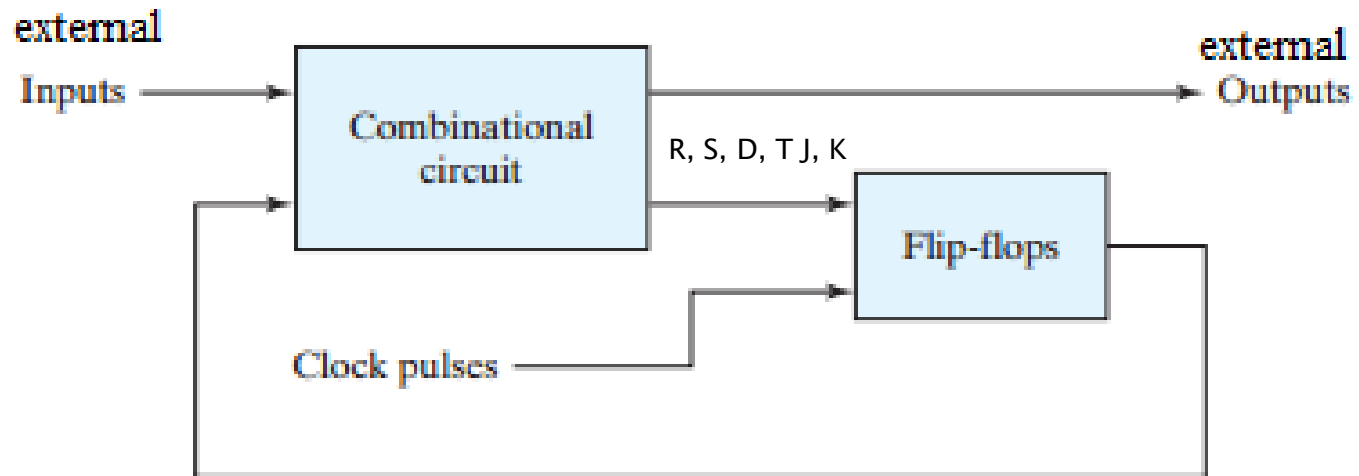

Recap: Synchronous Sequential Circuits

Design Procedure

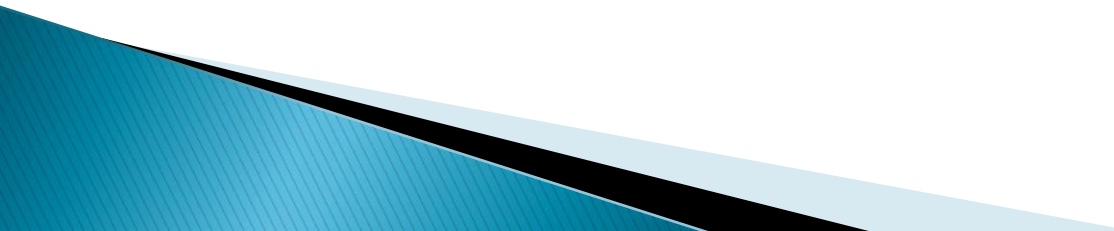- 1) State Diagram
 - 2) Number of ex. Inputs and outputs and number of flipflops
 - 3) State Table
 - 4) Simplified expressions using Kmap for external outputs and inputs of flipflops
 - 5) Logic diagram
- 

Designing using JK flip flops (deriving Excitation Table)

1) $Q_n = 0 \rightarrow Q_{n+1} = 0$

0 \rightarrow 0

J K

0 0

0 1

0 X

JK Flip-Flop			
J	K	Q(n + 1)	
0	0	Q(n)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(n)	Complement

2) $Q_n = 0 \rightarrow Q_{n+1} = 1$

0 \rightarrow 1

J K

1 0

1 1

1 X

3) $Q_n = 1 \rightarrow Q_{n+1} = 0$ 4) $Q_n = 1 \rightarrow Q_{n+1} = 1$

1 \rightarrow 0

J K

0 1

1 1

X 1

1 \rightarrow 1

J K

0 0

1 0


X 0


Designing using JK flip flops (deriving Excitation Table) continued..

Q(n)	Q(n + 1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

JK Flip-Flop

 Design a sequential circuit with input x that follows the following state diagram using JK flip flops



 

$Q(n)$	$Q(n + 1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

JK Flip-Flop

Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	J_A	K_A	J_B	K_B
0	0	0	0	0	X	0	X	
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

3)


		B			
		Bx	00	01	11
A	0	m_0	m_1	m_3	m_2 1
	1	m_4 X	m_5 X	m_7 X	m_6 X
		x			
		$J_A = Bx'$			

		B			
		Bx	00	01	11
A	0	m_0 X	m_1 X	m_3 X	m_2 X
	1	m_4	m_5	m_7 1	m_6
		x			
		$K_A = Bx$			



		B			
		Bx	00	01	11
A	0	m_0	m_1 1	m_3 X	m_2 X
	1	m_4	m_5 1	m_7 X	m_6 X
		x			
		$J_B = x$			

		B			
		Bx	00	01	11
A	0	m_0 X	m_1 X	m_3	m_2 1
	1	m_4 X	m_5 X	m_7 1	m_6
		x			
		$K_B = (A \oplus x)'$			

4)

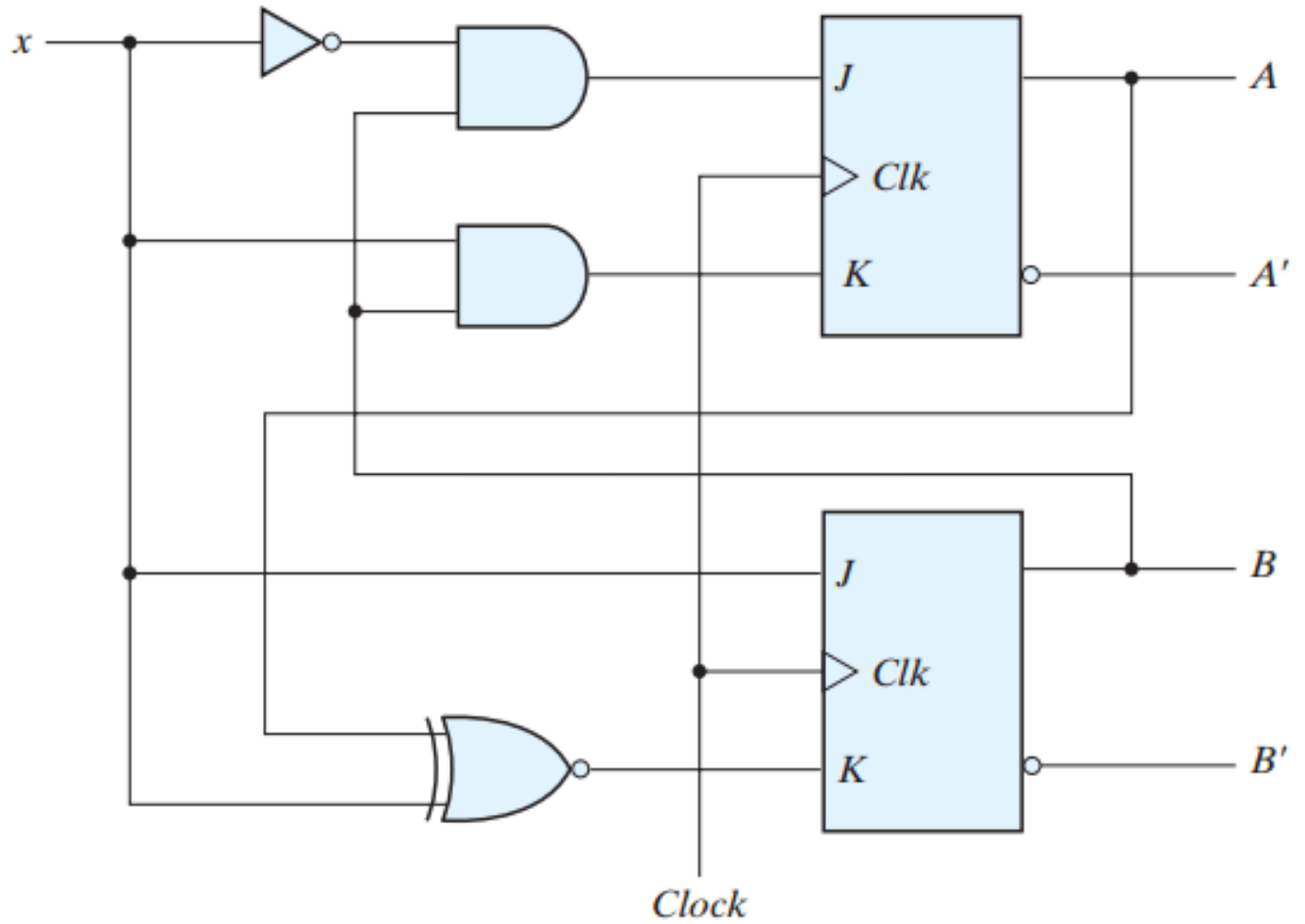

Counters

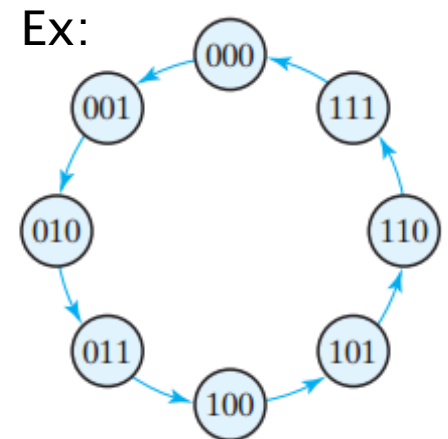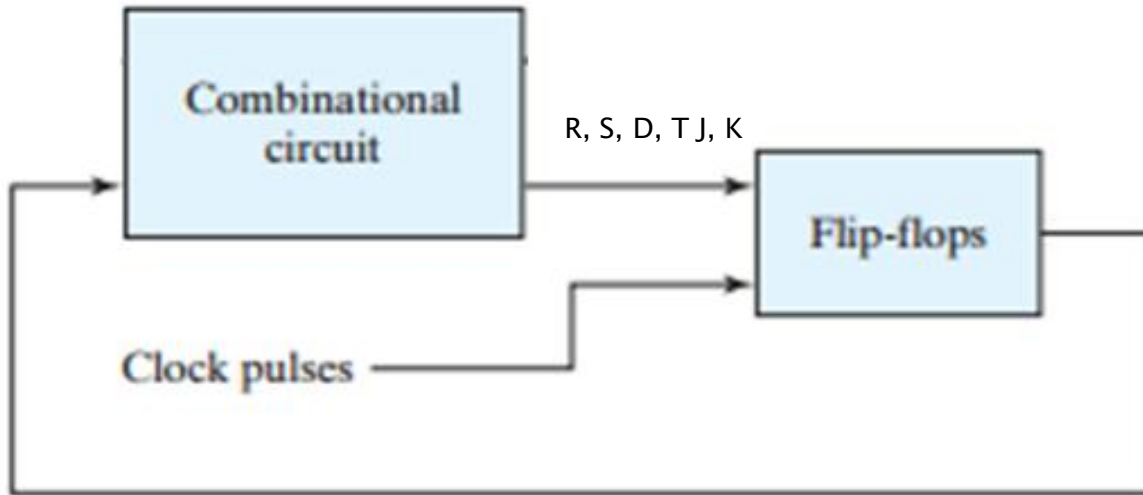

Design a 2 bit counter using JK flip flops


$Q(n)$	$Q(n + 1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

JK Flip-Flop

A_n	B_n	A_{n+1}	B_{n+1}	J_A	K_A	J_B	K_B
0	0	0	1	0	X	1	X
0	1	1	0	1	X	X	1
1	0	1	1	X	0	1	X
1	1	0	0	X	1	X	1

3) $J_A = K_A = B$
 $J_B = K_B = 1$

4)

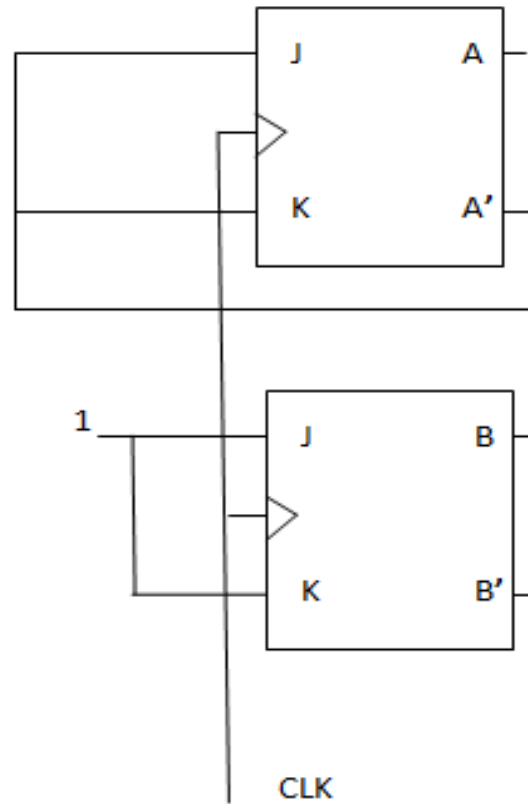



Design a counter that counts the following sequence 1, 6, 7, 3, 2 using T flipflops. Check if it self correcting or not

A_n	B_n	C_n	A_{n+1}	B_{n+1}	C_{n+1}	T_A	T_B	T_C
0	0	0	X	X	X			
0	0	1	1	1	0			
0	1	0	0	0	1			
0	1	1	0	1	0			
1	0	0	X	X	X			
1	0	1	X	X	X			
1	1	0	1	1	1			
1	1	1	0	1	1			

Design a counter that counts the following sequence 1, 6, 7, 3, 2 using T flipflops. Check if it self correcting or not

T Flip-Flop

T	Q(n + 1)
0	Q(n)
1	Q'(n)

	A_n	B_n	C_n		A_{n+1}	B_{n+1}	C_{n+1}	T_A	T_B	T_C
	0	0	0		X	X	X	X		
	0	0	1		1	1	0	1		
	0	1	0		0	0	1	0		
	0	1	1		0	1	0	0		
	1	0	0		X	X	X	X		
	1	0	1		X	X	X	X		
	1	1	0		1	1	1	0		
	1	1	1		0	1	1	1		

Design a counter that counts the following sequence 1, 6, 7, 3, 2 using T flipflops. Check if it self correcting or not

T Flip-Flop

T	Q(n + 1)
0	Q(n)
1	Q'(n)

A_n	B_n	C_n	A_{n+1}	B_{n+1}	C_{n+1}	T_A	T_B	T_C
0	0	0	X	X	X	X	X	
0	0	1	1	1	0	1	1	
0	1	0	0	0	1	0	1	
0	1	1	0	1	0	0	0	
1	0	0	X	X	X	X	X	
1	0	1	X	X	X	X	X	
1	1	0	1	1	1	0	0	
1	1	1	0	1	1	1	0	

Design a counter that counts the following sequence 1, 6, 7, 3, 2 using T flipflops. Check if it self correcting or not

T Flip-Flop

T	Q(n + 1)
0	Q(n)
1	Q'(n)

A_n	B_n	C_n	A_{n+1}	B_{n+1}	C_{n+1}	T_A	T_B	T_C
0	0	0	X	X	X	X	X	X
0	0	1	1	1	0	1	1	1
0	1	0	0	0	1	0	1	1
0	1	1	0	1	0	0	0	1
1	0	0	X	X	X	X	X	X
1	0	1	X	X	X	X	X	X
1	1	0	1	1	1	0	0	1
1	1	1	0	1	1	1	0	0

TA

Bn

	0 X	1 1	3	2
An	4 X	5 X	7 1	6

Cn

$$TA = Bn' + An Cn$$

TB

Bn

	0 X	1 1	3	2 1
An	4 X	5 X	7	6

Cn

$$TB = Bn' + An' Cn'$$

	Tc			Bn				
	0	X	1	1	3	1	2	1
An	4	X	5	X	7		6	1
								Cn





$$TC = An' + Cn' = (An Cn)'$$

4) Draw logic diagram

The unused states of this counter are 0
, 4 and 5
Is it self-correcting ??

    Examples for self-correcting

- ▶ If the unused states are 2, 4 and 6 for example. Let us consider some cases for checking the designed counter



Now what about our counter

$$T_A = B_n' + A_n C_n$$

$$T_B = B_n' + A_n' C_n'$$

$$T_C = A_n' + C_n' = (A_n C_n)'$$

Unused states

Unused state A B C	Ta Tb Tc	Its next state A B C
0 0 0	1 1 1	1 1 1 ✓
1 0 0		
1 0 1		

Now what about our counter

$$T_A = B_n' + A_n C_n$$

$$T_B = B_n' + A_n' C_n'$$

$$T_C = A_n' + C_n' = (A_n C_n)'$$

Unused states

Unused state A B C	Ta Tb Tc	Its next state A B C
0 0 0	1 1 1	1 1 1 ✓
1 0 0	1 1 1	0 1 1 ✓
1 0 1		

Now what about our counter

$$T_A = B_n' + A_n C_n$$

$$T_B = B_n' + A_n' C_n'$$


$$T_C = A_n' + C_n' = (A_n C_n)'$$

Unused states

Unused state A B C	Ta Tb Tc	Its next state A B C
0 0 0	1 1 1	1 1 1 ✓
1 0 0	1 1 1	0 1 1 ✓
1 0 1	1 1 0	0 1 1 ✓


Counter is self correcting

What if

 

A_n	B_n	C_n	A_{n+1}	B_{n+1}	C_{n+1}	T_A	T_B	T_C
0	0	0	X	X	X	X	X	X
0	0	1	1	1	0	1	1	1
0	1	0	0	0	1	0	1	1
0	1	1	0	1	0	0	0	1
1	0	0	X	X	X	X	X	X
1	0	1	0 X	1 X	0 X	1 X	1 X	1 X
1	1	0	1	1	1	0	0	1
1	1	1	0	1	1	1	0	0

What we can do ??

 

Break the loop, update the table and redesign (repeat the maps)

**Next Lecture we will explain
analysis of sequential circuits
thank you**

